 


# EE230 : Analog Circuits Lab

Mayur Ware | 19D070070, **Section 6**  
Experiment 5 : NMOS Output Characteristics

August 29, 2021

## NMOS Output Characteristics



Mayur Ware | 19D070070

### \*NMOS Output Characteristics

```
.model NXYAA5U nmos Level=1 Vto=0.7 KP=80u w=14.8u L=1u  
+ Gamma=0 Phi=0.65 Lambda=0.0
```

### \*Voltage Sources

```
V1 B D 0
```

```
V2 A GND 1
```

```
VGS G GND 2
```

### \*NMOS

```
M1 D G GND GND NXYAA5U
```

### \*Resistor

```
RD A B 2.2k
```

### \*Control Commands

```
.control
```

```
dc V2 0 50 0.2 VGS 2 5 1
```

```
run
```

```
plot i(V1)
```


```
.endc
```

```
.end
```

## Simulation Results :

For different values of  $V_{GS}$ , we get different values of  $I_{DS}$

 
- 1) For  $V_{GS} = 2V$ ,  $I_{DS} = 1.02mA$
- 2) For  $V_{GS} = 3V$ ,  $I_{DS} = 3.12mA$
- 3) For  $V_{GS} = 4V$ ,  $I_{DS} = 6.51mA$
- 4) For  $V_{GS} = 5V$ ,  $I_{DS} = 10.98mA$



I learned variation of  $I_{DS}$  with  $V_{GS}$  and  $V_{DS}$

## NMOS Common-Source Amplifier (Bias Circuit)

### Biasing Analysis

 

As given,

$$I_D = 1\text{mA}$$

$$V_G = V_{DD} \times \frac{R_2}{(R_1 + R_2)} = 3.44\text{V}$$

$$V_D = V_{DD} - I_D R_D = 8.71\text{V}$$

$$V_S = I_D R_S = 1\text{V}$$

Mayur Ware | 19D070070

\*Common Source Amplifier

.model NXYAA5U nmos Level =1 Vto =1 KP =100 u w=10u L=1u

+ Gamma =0 Phi =0.65 Lambda =0.01

\*Voltage Sources

VDD DD 0 dc 12V

VDS Out D dc 0V

Vin In 0 sin (0 50m 1k 0 0)

\*Resistances

R1 DD G 8.2k

R2 G 0 3.3k

Rd DD Out 3.3k

Rs S 0 1k

\*Capacitors

C1 G In 10u

Cs S 0 100u

\*NMOS

M1 D G S 0 NXYAA5U

.tran 0.1u 3m

.control

run

set color0 = white

set color1 = black

set color2 = blue

set color3 = red

print i(VDS) V(G) V(S) V(D)

.endc

.end

**Simulation Results :**  $i(VDS) = 1.011256\text{mA}$


$V(G) = 3.442654\text{V}$

$V(S) = 1.011256\text{V}$

$V(D) = 8.643329\text{V}$

## NMOS Common-Source Amplifier (Bias Circuit)

### Gain Analysis

 

Assuming,  
 $I_D = 1\text{mA}$   
 $V_A = 100\text{V}$   
 So,  

$$g_m = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right) I_D} = 1.414\text{mS}$$

$$r_o = \frac{V_A}{I_D} = 100\text{k}\Omega$$

$$A_{v_{mid}} = -g_m (R_D \parallel r_o) = -4.52$$

Mayur Ware | 19D070070

\*Common Source Amplifier

.model NXYAA5U nmos Level =1 Vto =1 KP =100 u w=10u L=1u

+ Gamma =0 Phi =0.65 Lambda =0.01

\*Voltage Sources

VDD DD 0 dc 12V

VDS Out D dc 0V

Vin In 0 sin (0 50m 1k 0 0)

\*Resistances

R1 DD G 8.2k

R2 G 0 3.3k

Rd DD Out 3.3k

Rs S 0 1k

\*Capacitors

C1 G In 10u

Cs S 0 100u

\*NMOS

M1 D G S 0 NXYAA5U

.tran 0.1u 3m

.control

run

meas tran a pp v(Out)


meas tran b pp v(In)

gain = -1\*a/b

print gain


.endc

.end

 

I learned about how to calculate the biasing conditions of a common source amplifier and how to do the small signal analysis for the same.
 
## NMOS Current Mirror based Current Source



Mayur Ware | 19D070070

\*NMOS Current Mirror

.model NXYAA5U nmos Level =1 Vto =1 KP =100 u w=10u L=1u

+ Gamma =0 Phi =0.65 Lambda =0.01

\*Voltage Sources

VDD DD 0 dc 12V

VO D 0 dc 1V

\*Resistances

R DD G 8.2k

\*NMOS

M1 G G 0 0 NXYAA5U

M2 D G 0 0 NXYAA5U

.dc Vo 1V 5V 0.2V

.control


run

print i(VDD) i(VO)

plot i(VO)

.endc

.end

 

I learned how a current mirror is created using NMOS

### References

- 1) Lecture Slides
- 2) Sedra-Smith
- 3) WEL Resources for NGSpice