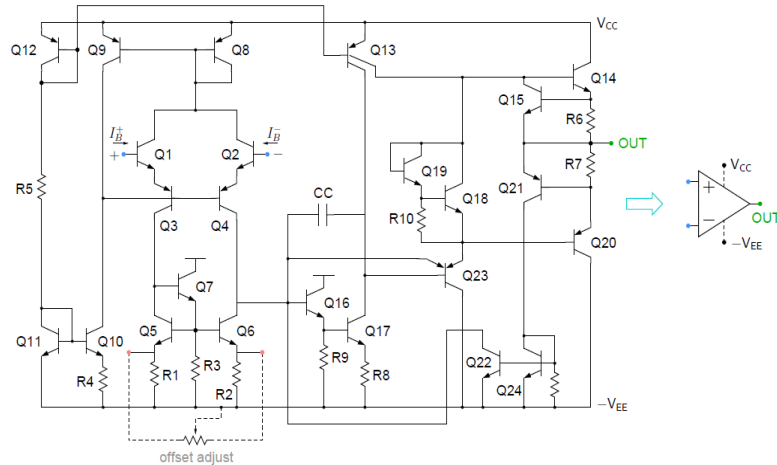


EE230 : Analog Circuits Lab


Mayur Ware | 19D070070, **Section 6**
Experiment 9 : Measurement of Opamp DC Parameters

October 9, 2021



Internal Circuit of OpAmp 741

Input offset voltage

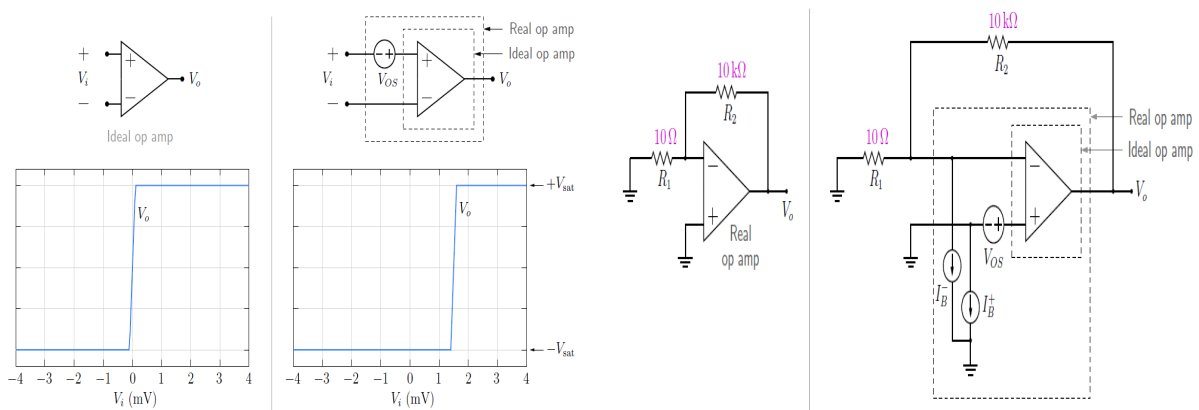

In reality, there are always some small differences between the transistors.

As a result of this mismatch, the V_o versus V_i relationship of a real OpAmp exhibits a shift along the V_i axis.

For Op Amp 741, the offset voltage is typically in the range -5mV to +5mV.

$$V_{OS} = \frac{V_o}{1 + R_2/R_1} = \frac{V_o}{R_2/R_1}$$

Input bias currents

The transistors of the input stage of OpAmp 741 draw small but non-zero base currents I_{B+} and I_{B-} . Due to mismatches, I_{B+} and I_{B-} are not the same.


The average of the two currents is called the input bias current I_B , and the difference between the two is called the input offset current I_{OS}

$$I_B = \frac{I_{B+} + I_{B-}}{2} \quad I_{OS} = |I_{B+} - I_{B-}|$$

For Op Amp 741, I_B is typically 100 nA, and I_{OS} is 10 nA at 25 °C.


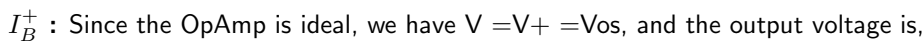
$$\Rightarrow I_B^- \approx V_o/R \quad \text{For large values of } R$$



$$\Rightarrow I_B^+ \approx V_o/R \quad \text{For large values of } R$$

$$\frac{R_2}{R_2 + R_3}(V_o^B - V_o^A) * A_{OL} = -V'$$

Comparison

Following is a table comparing the Input offset voltage (V_{OS}), Input bias current (I_B), Input offset current (I_{OS}) and the DC open loop gain (A_{OL}) of UA741, TL084 and LM324.

Values in the table are the typical values at $25^{\circ}C$

Parameter	UA741	TL084	LM324
V_{OS}	1mV	3mV	3mV
I_B	80nA	20pA	20nA
I_{OS}	20nA	5pA	2nA
A_{OL}	200V/mV	200V/mV	100V/mV

References

- 1) Lecture Slides
- 2) Sedra-Smith