

Expt 5 – NMOS Output Characteristics, CS Amplifier, and Current Mirror

EE 230 Analog Circuits Lab


Joseph John

2021-22/I

Summary

- Quiz 4, Question 6 – Diff Pair - Large Signal response
- Expt 5
 - Part A - NMOS Output Characteristics
 - Part B - CS Amplifier
 - Part C - Current Mirror based Current Source

Quiz 4, Ques.6

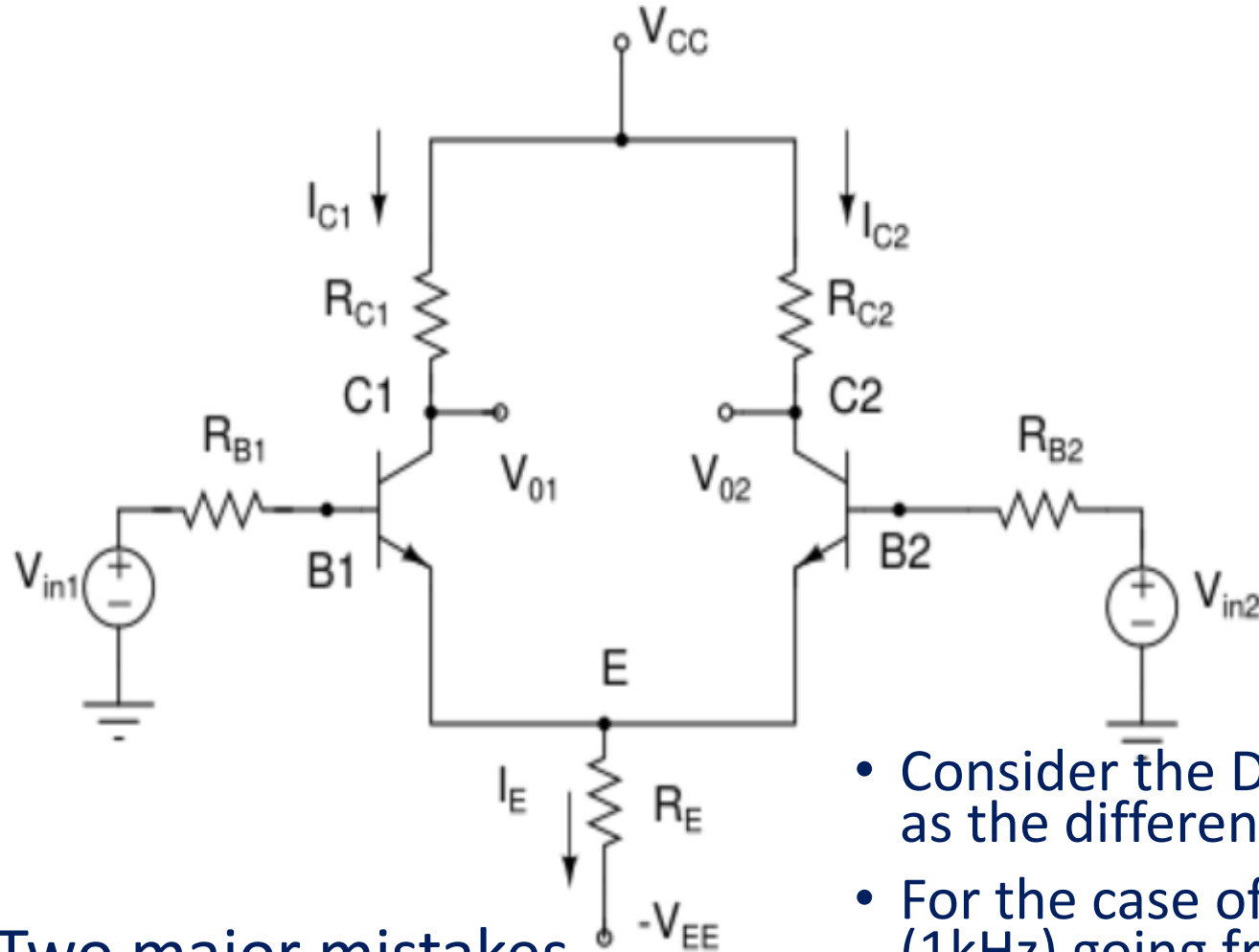

- Two major mistakes

- Large signal vs small signal
- Max Vout?

- Circuit values and parameters:


- $V_{CC} = +10\text{ V}$,
- $-V_{EE} = -10\text{ V}$,
- $R_{C1} = R_{C2} = 2\text{ k}\Omega$,
- $R_{B1} = R_{B2} = 1\text{ k}\Omega$,
- $R_E = 5\text{ k}\Omega$.

- Consider the Differential pair circuit of Expt 4 (same as the differential pair shown in Question 3).
- For the case of $V_{in2} = 0$ and V_{in1} a pulse waveform (1kHz) going from -2 V to $+2\text{ V}$, sketch the V_{O2} output.
- Your sketch should show both V_{in1} and V_{O2} and also the voltage levels.

BJT Capacitances

- C_π and C_μ – parasitic capacitances or internal capacitances?
- **C_π and C_μ are internal capacitances (Ref Sedra & Smith – Microelectronic Circuits)**

Table 5.1 Regions of Operation of the Enhancement NMOS Transistor

 

- $v_{GS} < V_{tn}$: no channel; transistor in cut-off; $i_D = 0$
- $v_{GS} = V_{tn} + v_{OV}$: a channel is induced; transistor operates in the triode region or the saturation region depending on whether the channel is continuous or pinched-off at the drain end;

Triode Region

Continuous channel, obtained by:

$$v_{GD} > V_{tn}$$

or equivalently:

$$v_{DS} < v_{OV}$$

Then,

$$i_D = k'_n \left(\frac{W}{L}\right) \left[(v_{GS} - V_{tn}) v_{DS} - \frac{1}{2} v_{DS}^2 \right]$$

or equivalently,

$$i_D = k'_n \left(\frac{W}{L}\right) \left(v_{OV} - \frac{1}{2} v_{DS} \right) v_{DS}$$

Saturation Region

Pinched-off channel, obtained by:

$$v_{GD} \leq V_{tn}$$

or equivalently:


$$v_{DS} \geq v_{OV}$$

Then


$$i_D = \frac{1}{2} k'_n \left(\frac{W}{L}\right) (v_{GS} - V_{tn})^2$$

or equivalently,
 
$$i_D = \frac{1}{2} k'_n \left(\frac{W}{L}\right) v_{OV}^2$$





 Source: Sedra & Smith –
Microelectronic Circuits, 6ed.,
Chap 5




Source: Sedra & Smith –
Microelectronic Circuits,
6ed., Chap 5

Part A - NMOS Output Characteristics

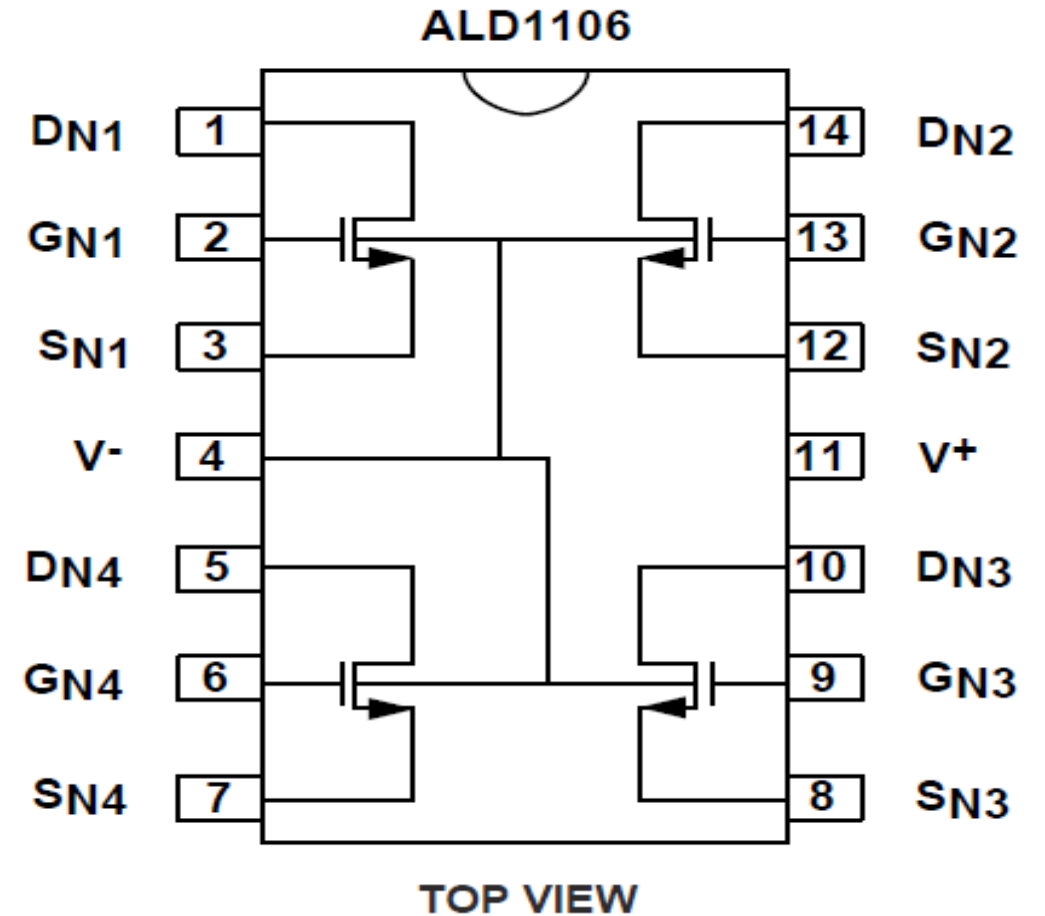 


I_D vs V_{DS} plots: Measured Results

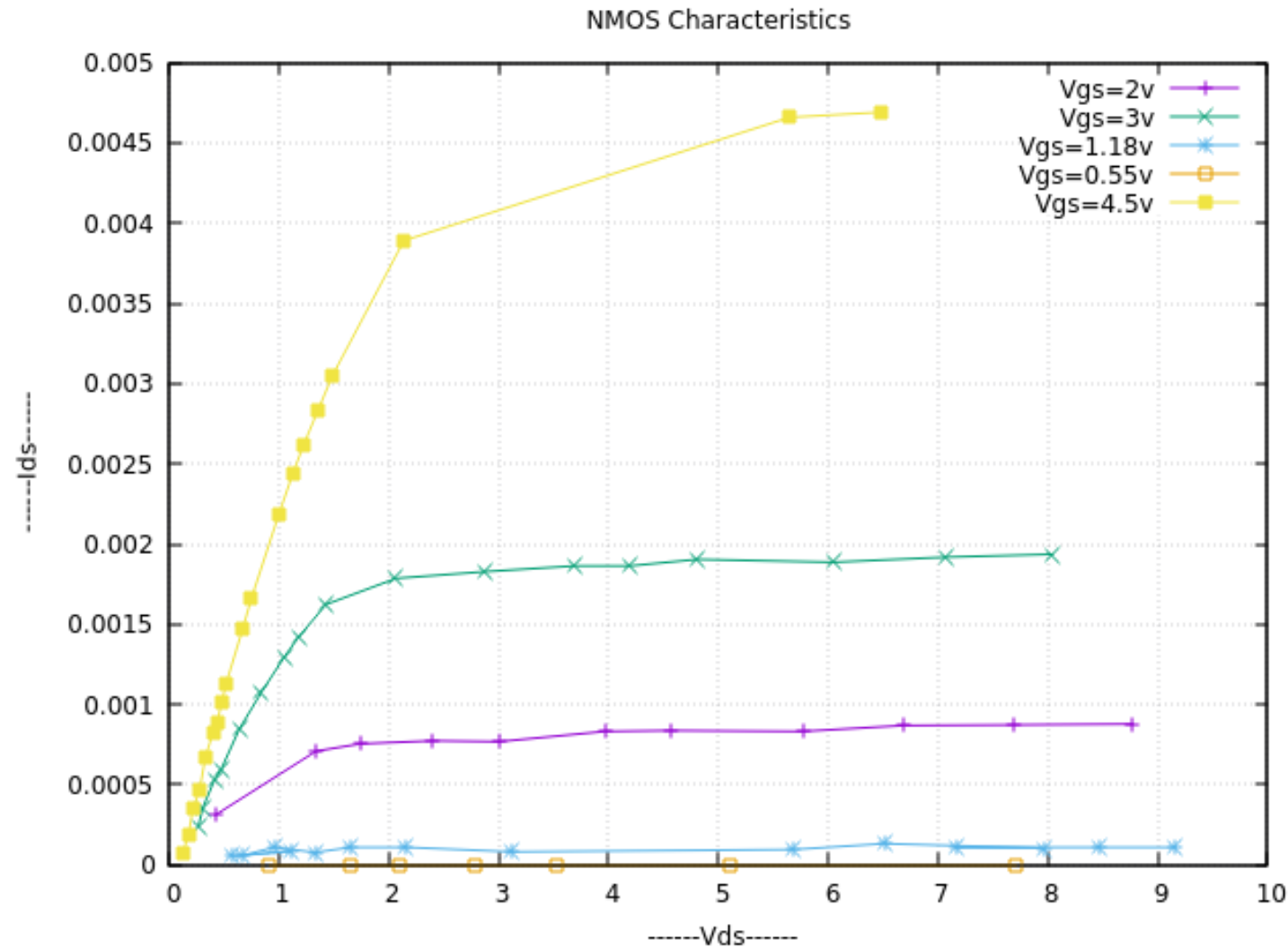

 
Part B - CS Amplifier

Features

- High input resistance
 - Limited only by the bias Ckt
- Low Voltage gain
 - Due to low g_m values
- Discrete CS Amplifiers seldom used




Part B - CS Amplifier – Bias Circuit

 

- $V_{DD} = 12 \text{ V}$
- $R_1 = 8.2 \text{ k}\Omega$
- $R_2 = 3.3 \text{ k}\Omega$
- $R_S = 1 \text{ k}\Omega$
- $R_D = 3.3 \text{ k}\Omega$
- Design values
 - $V_{GS} \approx 2 \text{ V}$
 - $V_G = 3.44 \text{ V}$


- Choice of R_1 , R_2 , R_S and R_D
- Decide on I_D
- Choose V_{GS}
 - From the I_D vs V_{DS} Characteristics
- Measured Voltages
 - $V_G = 3.4 \text{ V}$
 - $V_S = 0.98 \text{ V}$
 - $V_D = 8.72 \text{ V}$
 - $V_{GS} = 2.42 \text{ V}$
 - $I_D (= [(V_{DD} - V_D)/R_D]) = 0.99 \text{ mA}$

CS Amplifier

 


- $C_1 = 10 \mu\text{F}$
- $C_S = 100 \mu\text{F}$
- $V_{DD} = 12 \text{ V}$
- $R_1 = 8.2 \text{ k}\Omega$
- $R_2 = 3.3 \text{ k}\Omega$
- $R_S = 1 \text{ k}\Omega$
- $R_D = 3.3 \text{ k}\Omega$

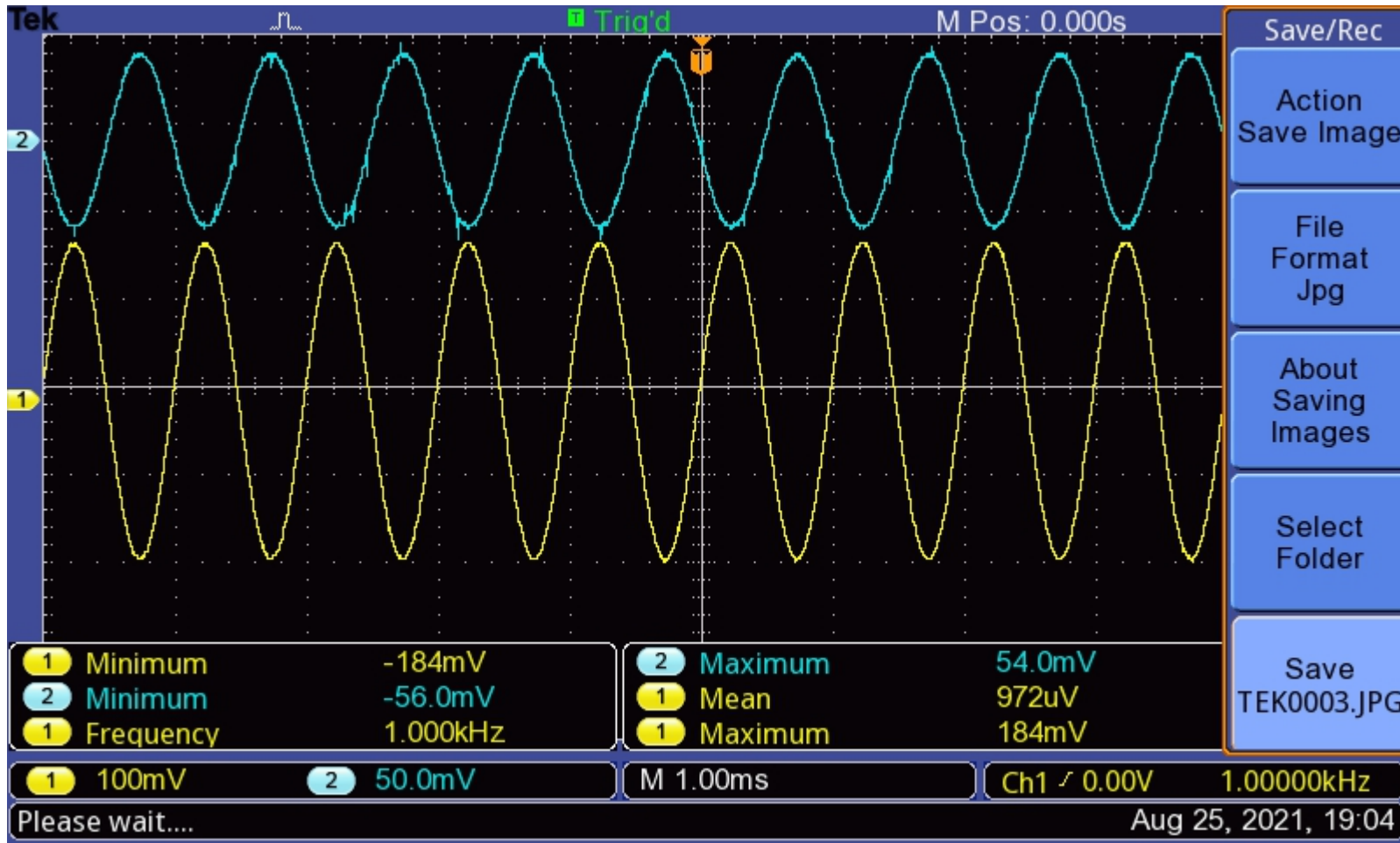CS Amplifier ($C_1 = 10 \mu\text{F}$; $C_S = 100 \mu\text{F}$)



- $V_{in} = 50 \sin \omega t$ (1 kHz)
 - V_{in} (p-to-p) = 100 mV
- V_{out} : 368 mV p-to-p
- Voltage gain = 3.68 V/V
 - ($R_D = 3.3 \text{ k}\Omega$, R_L – open)
- NGSPICE Simulation
 - $V_{out} = 465 \text{ mV}$ (p-p)
 - $(W/L)=10$; $KP= 100u$
 - $V_{to} = 1$

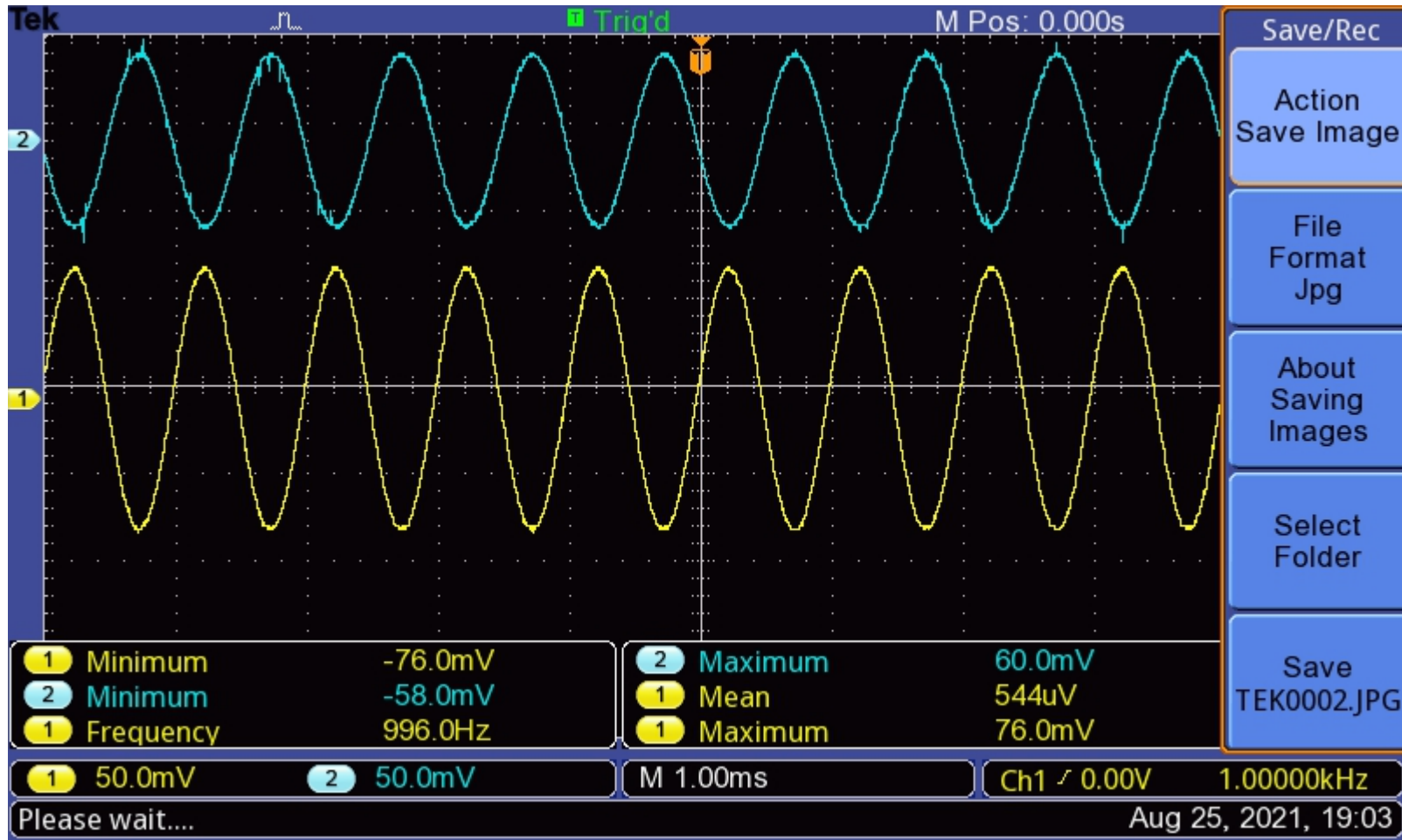CS Amplifier ($C_1 = 10 \mu\text{F}$; No C_S)




- $V_{in} = 50 \sin \omega t$ (1 kHz)
 - V_{in} (p-to-p) = 100 mV
- V_{out} : 120 mV p-to-p
- Voltage gain = 1.2 V/V
- NGSPICE Simulation
 - $V_{out} = 190$ mV (p-p)
 - $(W/L)=10$; $KP= 100u$
 - $V_{to} = 1$

Summary of CS Amplifier Features

- Very high input resistance (due to zero gate current)
 - Input resistance of the CS amp limited primarily due to the biasing circuit.
 - Solution - choose large resistor values at the input side for biasing
- Very low g_m
- Expression for g_m :
$$g_m = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right) I_D}$$
- Observation regarding g_m dependence:
 - Proportional to $\sqrt{I_D}$
 - Proportional to $\sqrt{\frac{W}{L}}$
 - Proportional to $\sqrt{\mu_n C_{ox}}$
 - Depends on both biasing current and on the process

 Part C - Current Mirror based Current Source



- $V_{DD} = 12\text{ V}$
- $R = 8.2\text{ k}\Omega$
- NGSPICE Simulation
 - $V_{GS} = 2.5\text{ V}$
 - $I_{REF} = 1.158\text{ mA}$
 - $I_O = 1.186\text{ mA}$ @ $V_O = 5\text{ V}$
 - $(W/L)=10$; $KP= 100\mu$
 - $V_{to} = 1$
 - $\text{Lambda} = 0.01$

Current Mirror - Measurements

```
1 #####
2 #   Current Mirror Experiment   #
3 #   Rout = 1k , biasing resistor = 8.2k #
4 #           Vgs=2.08V(measured)   #
5 #####
6 # Vdd(V) | Vout(V) | Io(mA)
7 1       0.47    0.53
8 2       1.19    0.81
9 3       2.18    0.82
10 4       3.22    0.78
11 5       4.19    0.81
12 6       5.22    0.78
13
```

```
1 #####
2 #   Current Mirror Experiment   #
3 #   Rout = 1k , biasing resistor = 6.8k #
4 #           Vgs=2.25V(measured)   #
5 #####
6 # Vdd(V) | Vout(V) | Io(mA)
7 1       0.44    0.56
8 2       1.08    0.92
9 3       2.03    0.97
10 4       3.04    0.96
11 5       4.03    0.97
12 6       5.02    0.98
13
```

