

Experiment 1 - Familiarization with NGSPICE and Lab Equipment

Joseph John

EE230 Analog (Circuits) Lab

2021-22/I

NGSPICE Familiarization

- Why NGSPICE? Why not LTSPICE, PSpICE,...
- NGSPICE - for understanding basic concepts better
 - Effect of device parameters on the circuit performance
- Comparison – Analysis, Simulation, Experiment
- Which one to trust? Why?

Why Analysis and Simulation Differ with the Measured Results?

- Analysis
 - Uses models
 - Involves lots of approximations
 - If so, why to use analysis?
- Simulation
 - Uses models
 - Should use the right models
 - If so, why to use simulation?

Experiments

- If carefully done should match closely to analysis and simulations
- All components have manufacturing tolerances
 - Resistors – 5%, 10% (0.1% resistors also available)
- Capacitors – several types
 - Named as per the dielectric used
 - Ceramic and Electrolytic capacitors – most commonly used
 - Paper, Mica, Polyester, Nylon – used in precision or high voltage applications

Youtube Recordings – done for EE113-2020

- Expt 0 – Familiarization
- Expt 1 – DC Power Supply
- Expt 2 – Opamp circuits (Linear and Non-linear)


Expt 1 - Familiarization

- NGSPICE simulation – RC and RLC Circuits
- Lab Equipment


RC Switching Circuits

- RC Integrator
- RC Differentiator


RC Integrator

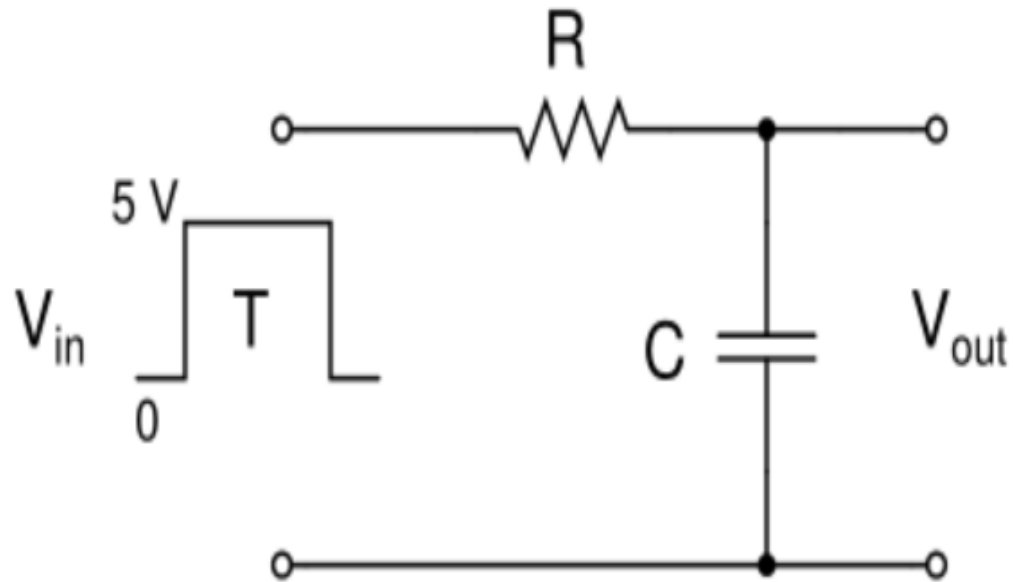

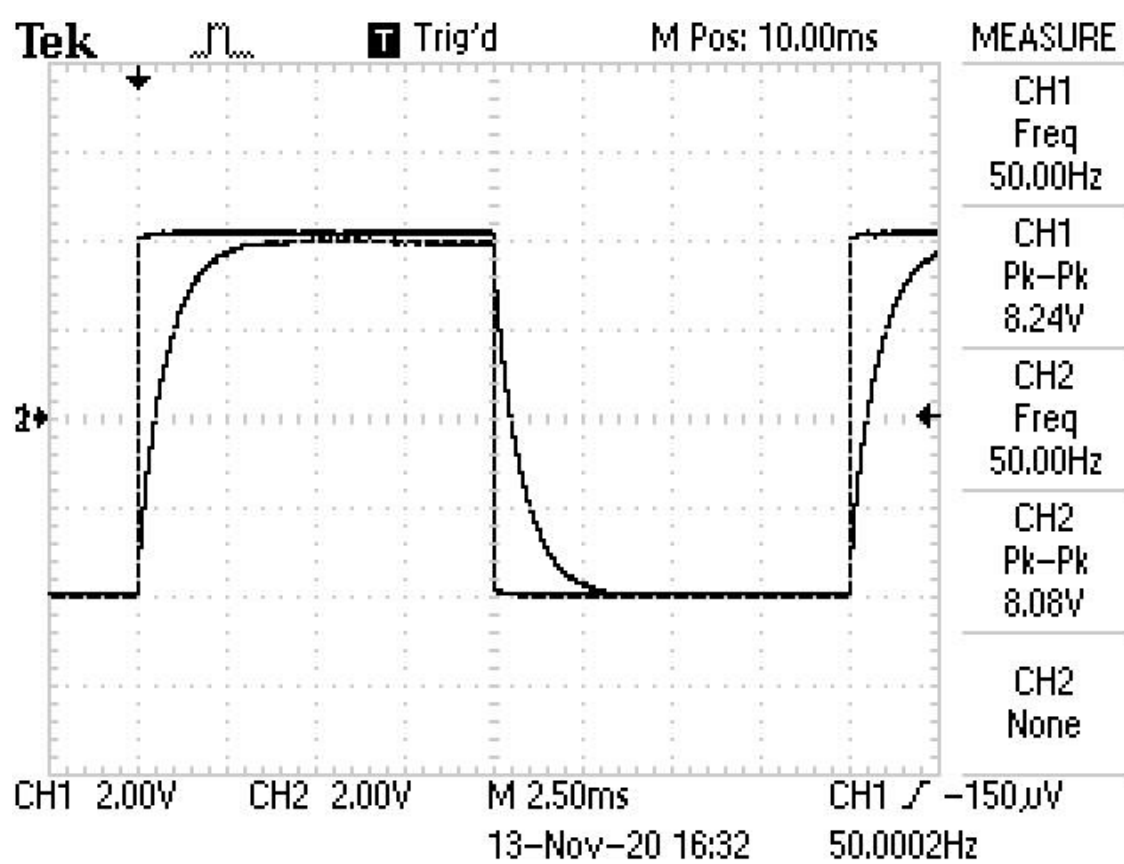
- $R = 10 \text{ k}\Omega$ and $C = 0.1 \text{ }\mu\text{F}$
- Cases:
 - i) $T = 10 \tau$;
 - ii) $T = 5 \tau$;
 - iii) $T = 1 \tau$;
 - iv) $T = 0.5 \tau$;
 - v) $T = 0.1 \tau$;
 - vi) $T = 0.05 \tau$




i) $T = 10 \tau$

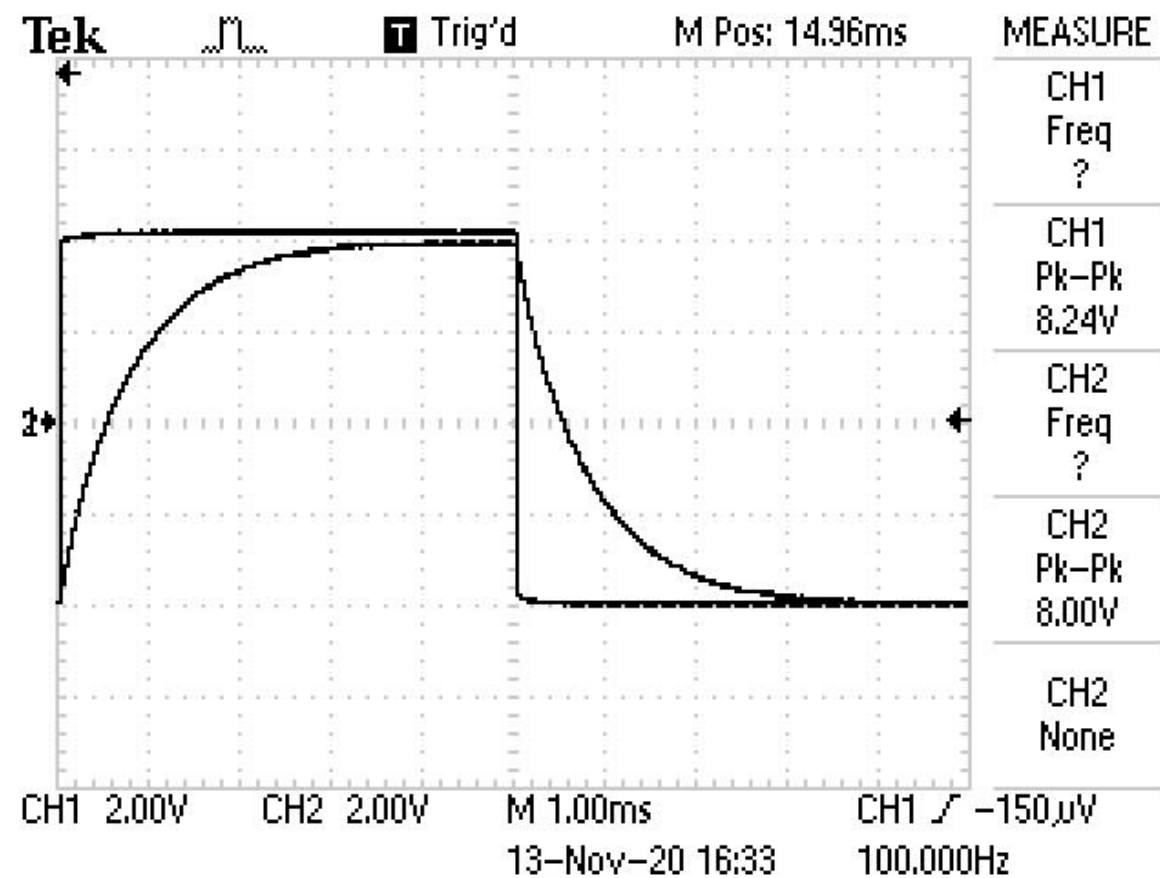


ii) $T = 5 \tau$

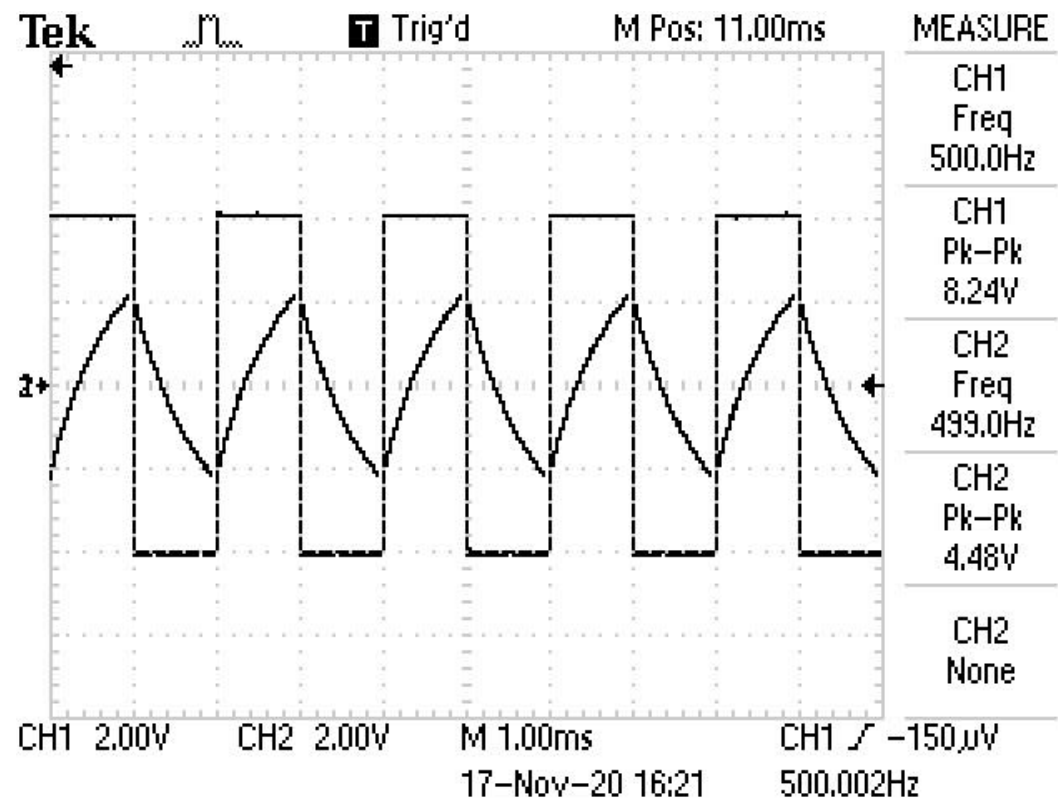

iii) $T = 1 \tau$

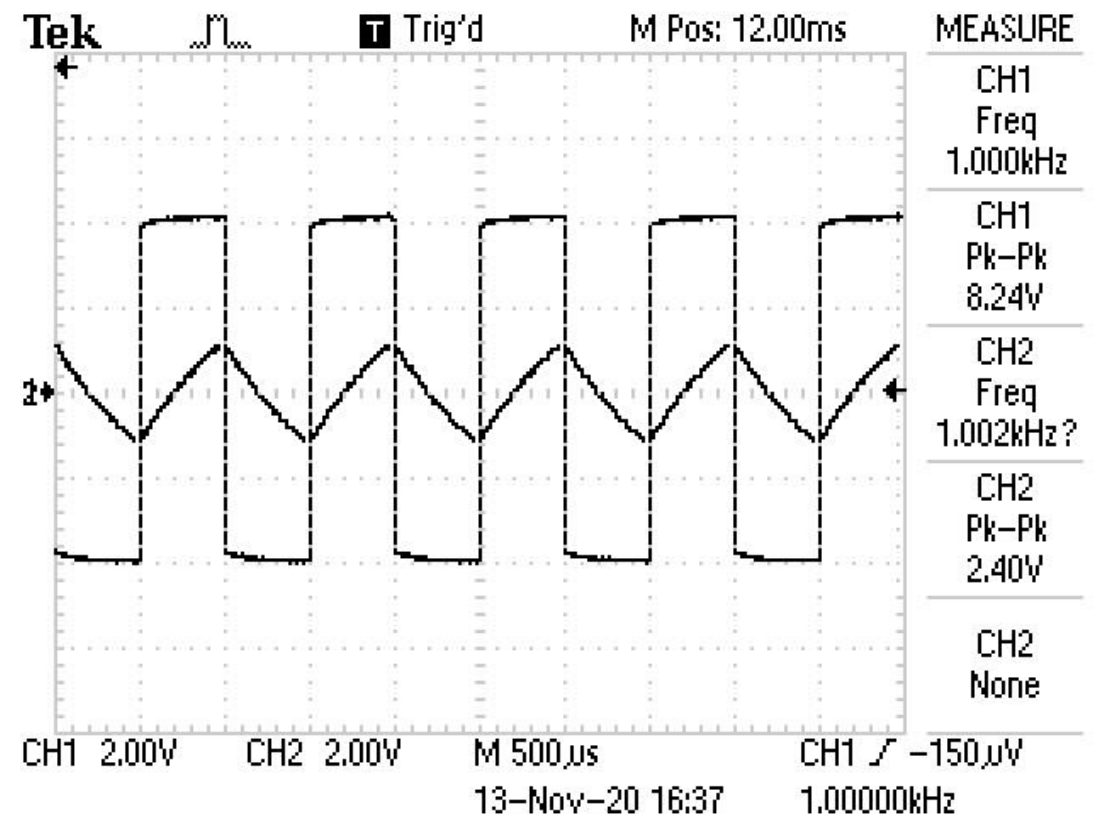


iv) $T = 0.5 \tau$

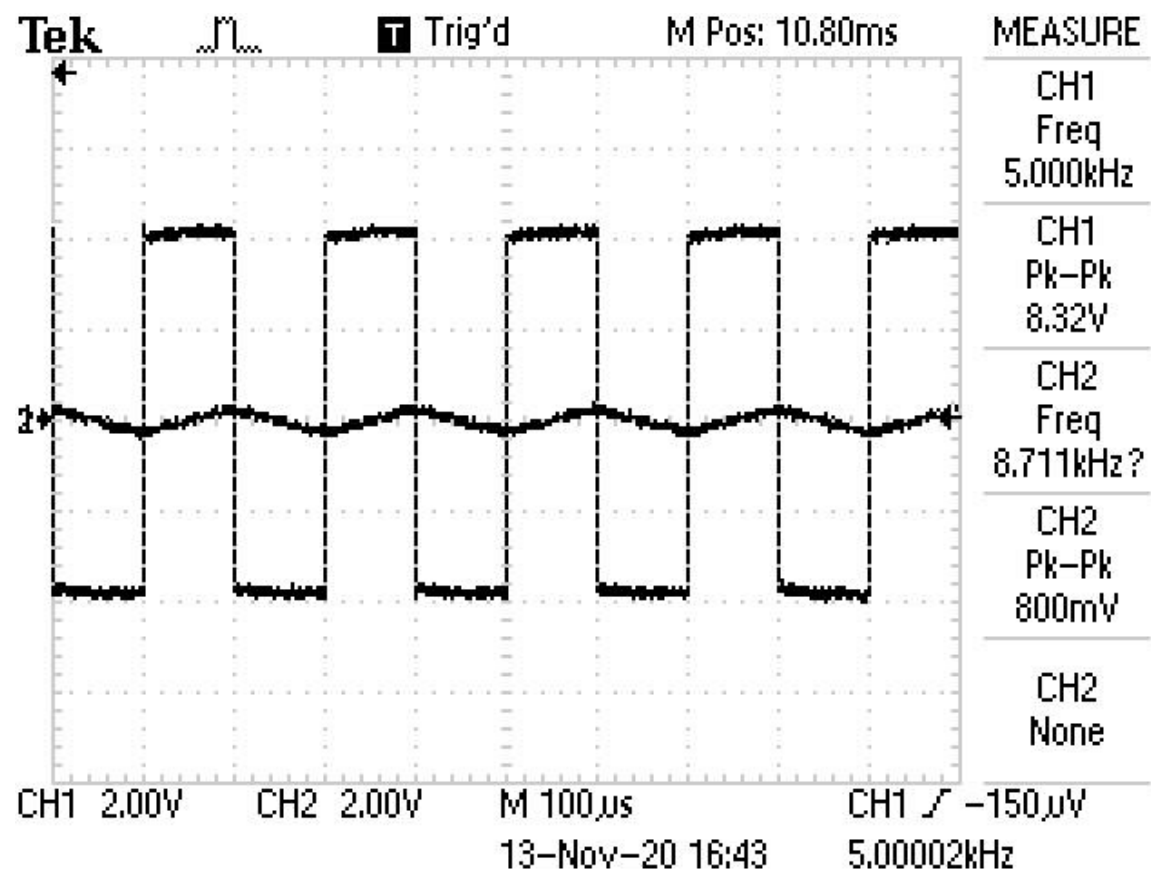

v) $T = 0.1 \tau$

RC Differentiator

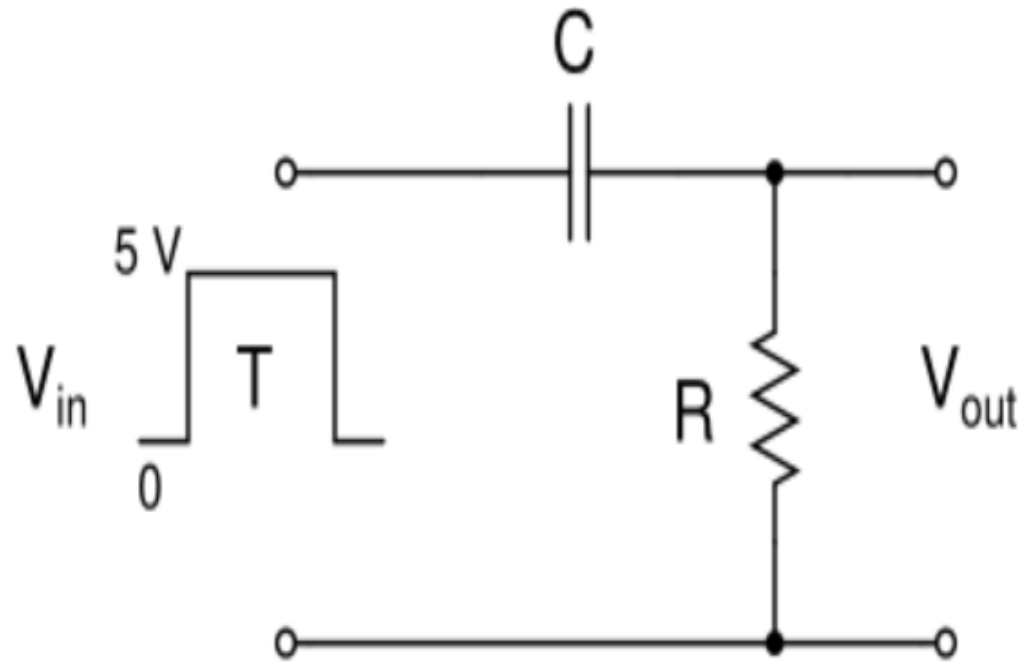

- $R = 10 \text{ k}\Omega$ and $C = 0.1 \text{ }\mu\text{F}$

- Cases:

- i) $T = 10 \tau$;


- ii) $T = 5 \tau$;

- iii) $T = 1 \tau$;


- iv) $T = 0.5 \tau$;

- v) $T = 0.1 \tau$;


- vi) $T = 0.05 \tau$

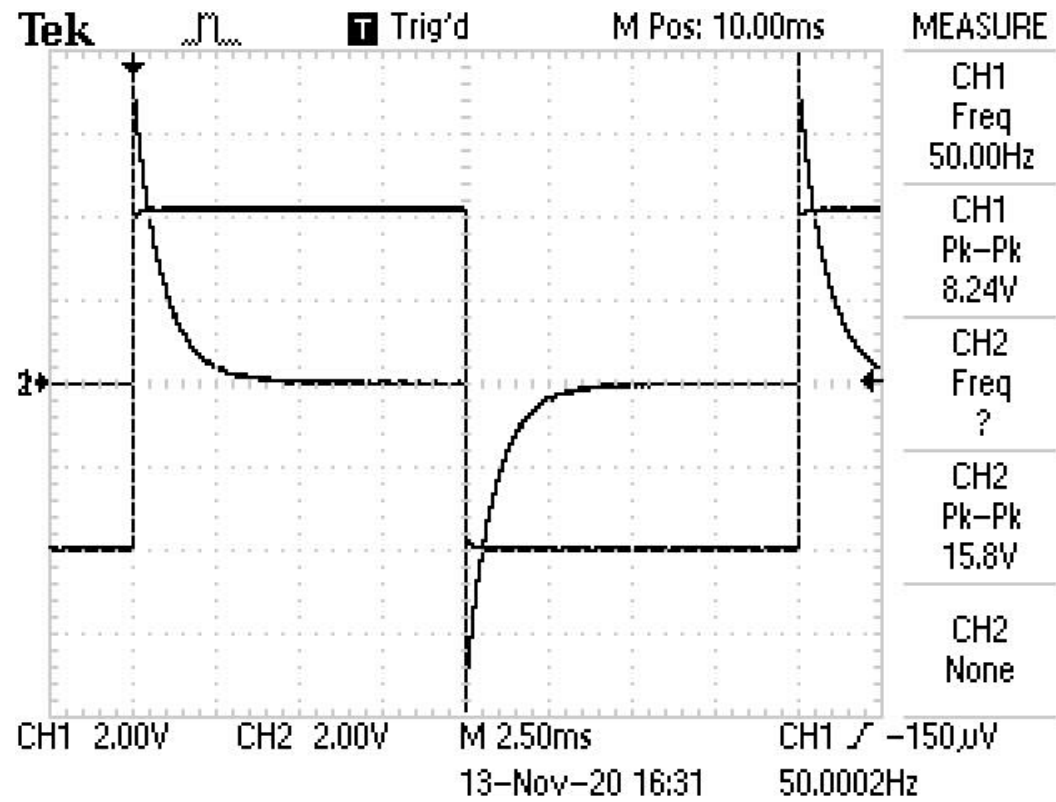

i) $T = 10 \tau$

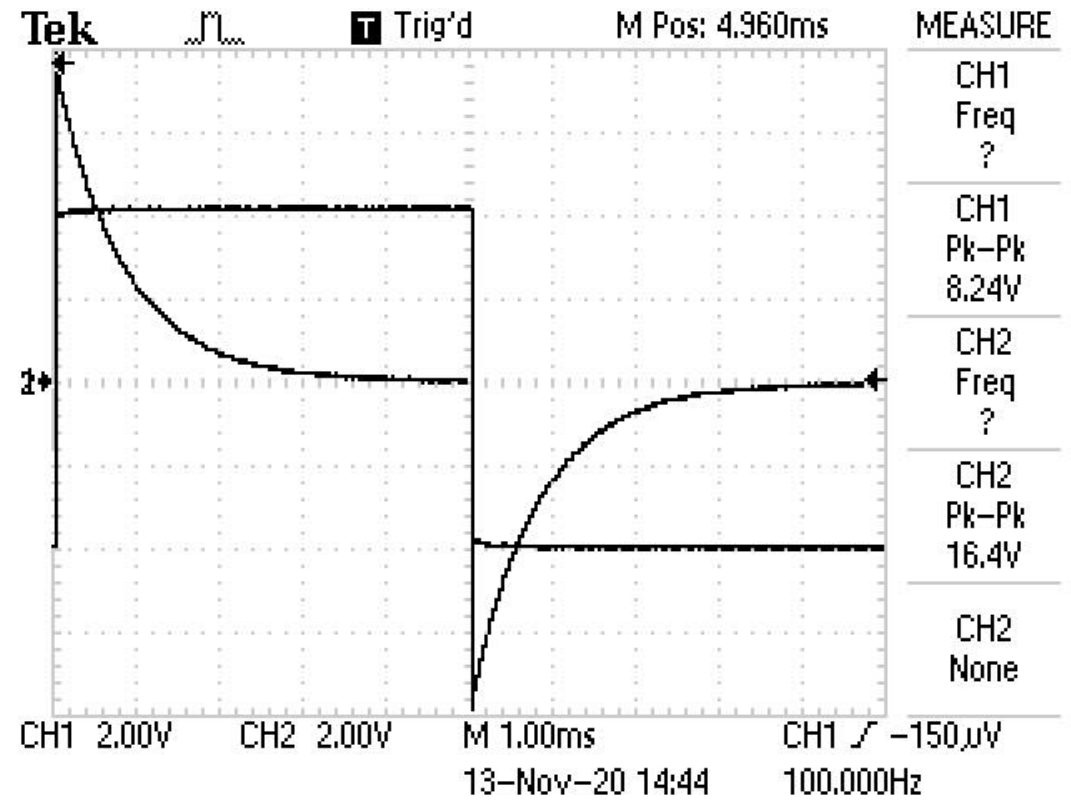

ii) $T = 5 \tau$

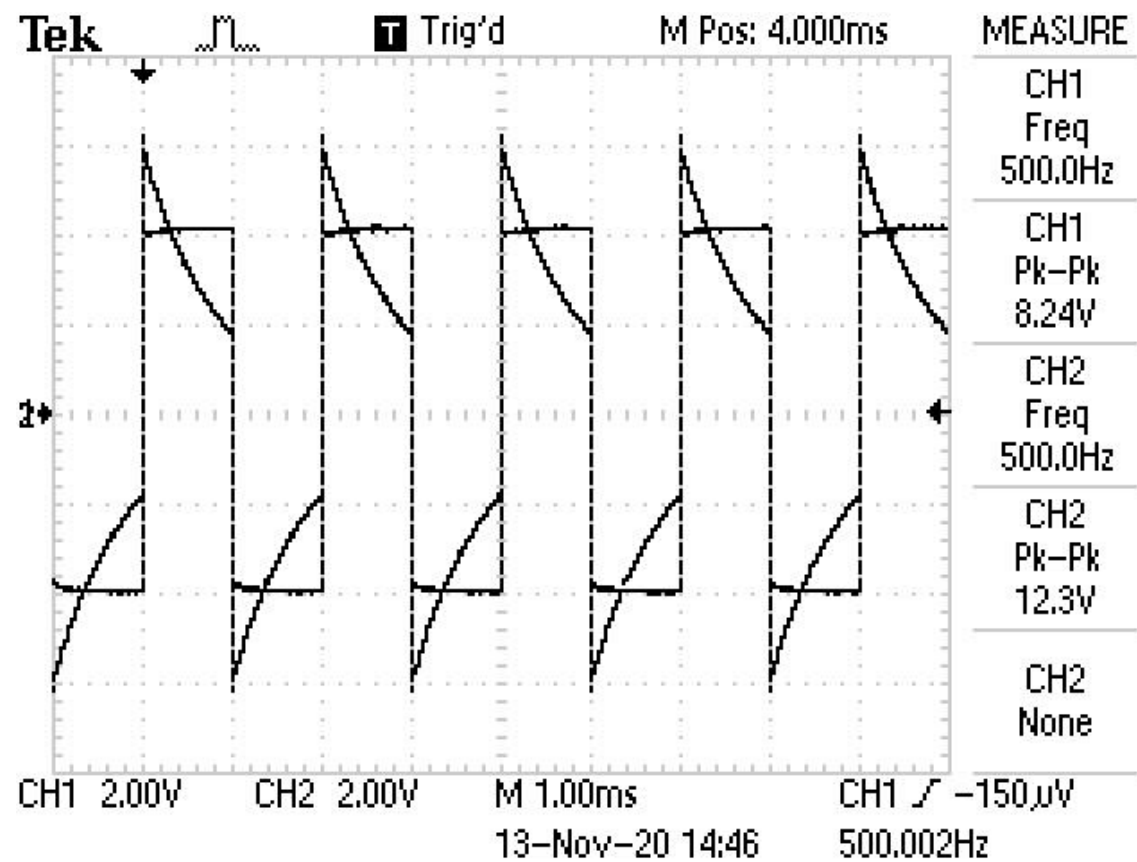


iii) $T = 1 \tau$

RC Filters


- RC Lowpass filter
- RC Highpass filter
- RC Bandpass filter

RC Filter Circuits

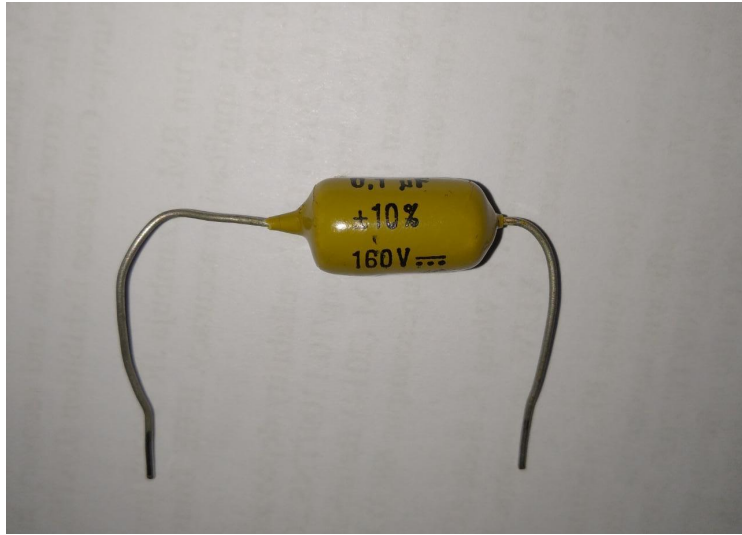- Easy to design and implement
- Not good for many applications
- Capacitors – several types
 - Named as per the dielectric used
 - Ceramic and Electrolytic capacitors – most commonly used
 - Paper, Mica, Polyester, Nylon – used in precision or high voltage applications



Paper Capacitor

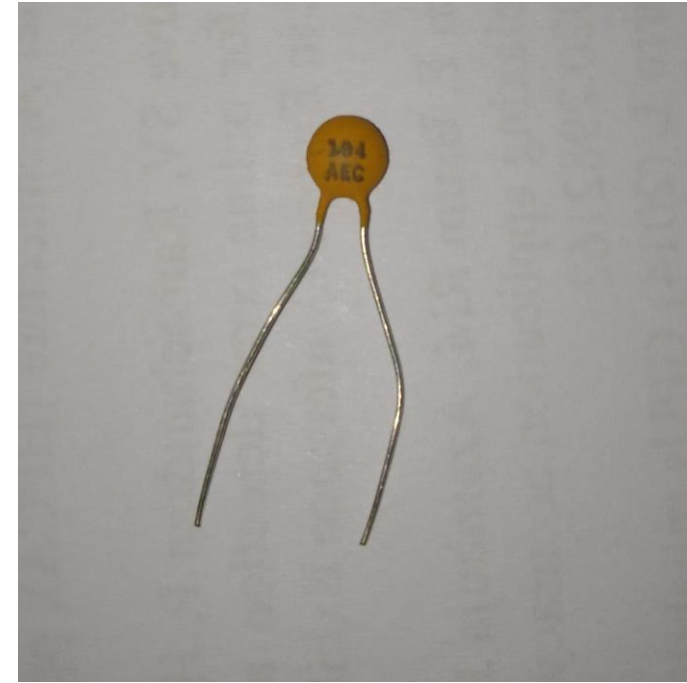

Ceramic Capacitor




Nylon/Polyster Capacitor




Paper
Capacitor

RC Lowpass Filter

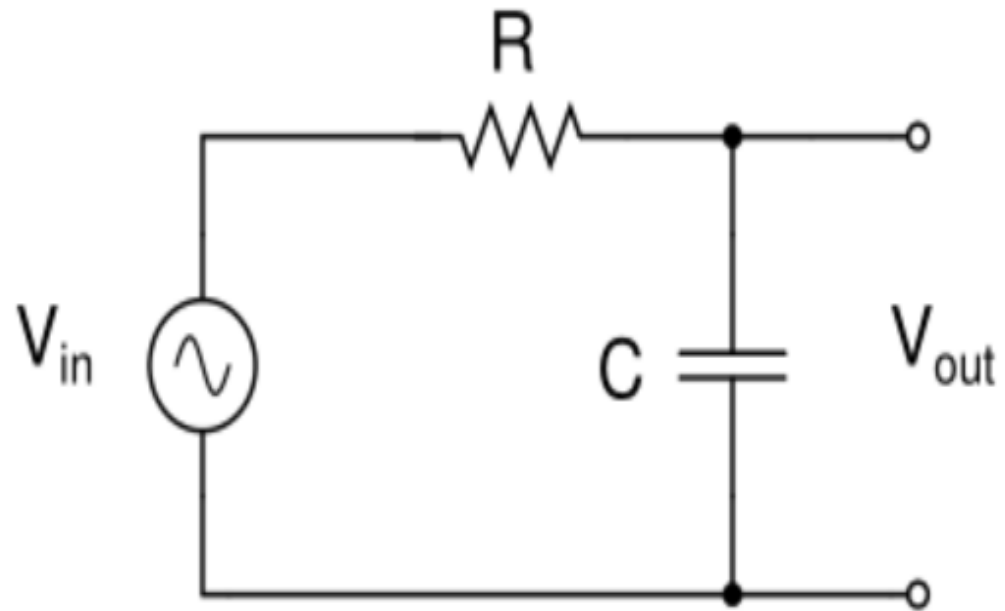

$$R = 10 \text{ k}\Omega, \quad C = 0.1 \text{ }\mu\text{F}.$$

Measured Results

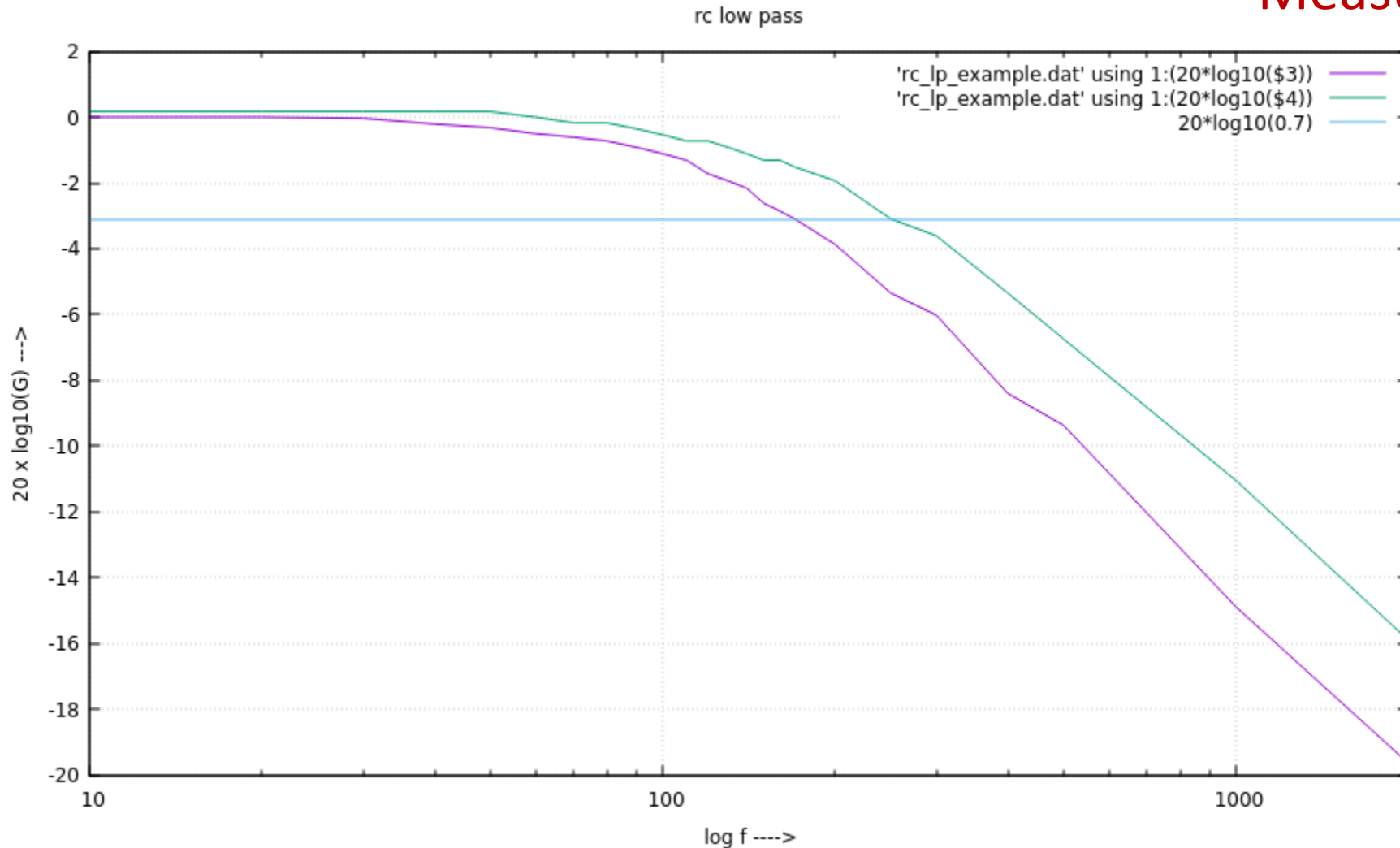

Nominal values:

$R = 10 \text{ k}\Omega$ and

$C = 0.1 \text{ }\mu\text{F}$

Actual:

$R = 9.7 \text{ k}\Omega$

$C = ??$

Green: Ceramic Capacitor

Light purple: Paper Capacitor (10% tolerance)

- Theory

$$f_c = 1/(2\pi RC)$$

(R = 10 kΩ, C = 0.1 μF)

- $f_c = 159.2 \text{ Hz}$


Note the
difference in
 $f_c \rightarrow$

RC LPF	Paper cap(10%)		Ceramic cap
freq	Vin(pk-pk)	Vout(pk-pk) V	Vout(pk-pk) V
10	1	1	1.02
20	1	1	1.02
30	1	0.996	1.02
40	1	0.976	1.02
50	1	0.964	1.02
60	1	0.944	1
70	1	0.932	0.98
80	1	0.92	0.98
90	1	0.9	0.96
100	1	0.88	0.94
110	1	0.86	0.92
120	1	0.82	0.92
130	1	0.8	0.9
140	1	0.78	0.88
150	1	0.74	0.86
160	1	0.72	0.86
170	1	0.7	0.84
200	1	0.64	0.8
250	1	0.54	0.7
300	1	0.5	0.66
400	1	0.38	0.54
500	1	0.34	0.46
1000	1	0.18	0.28
2000	1	0.104	0.16

RC Lowpass Filter


Measured values

RC Highpass Filter

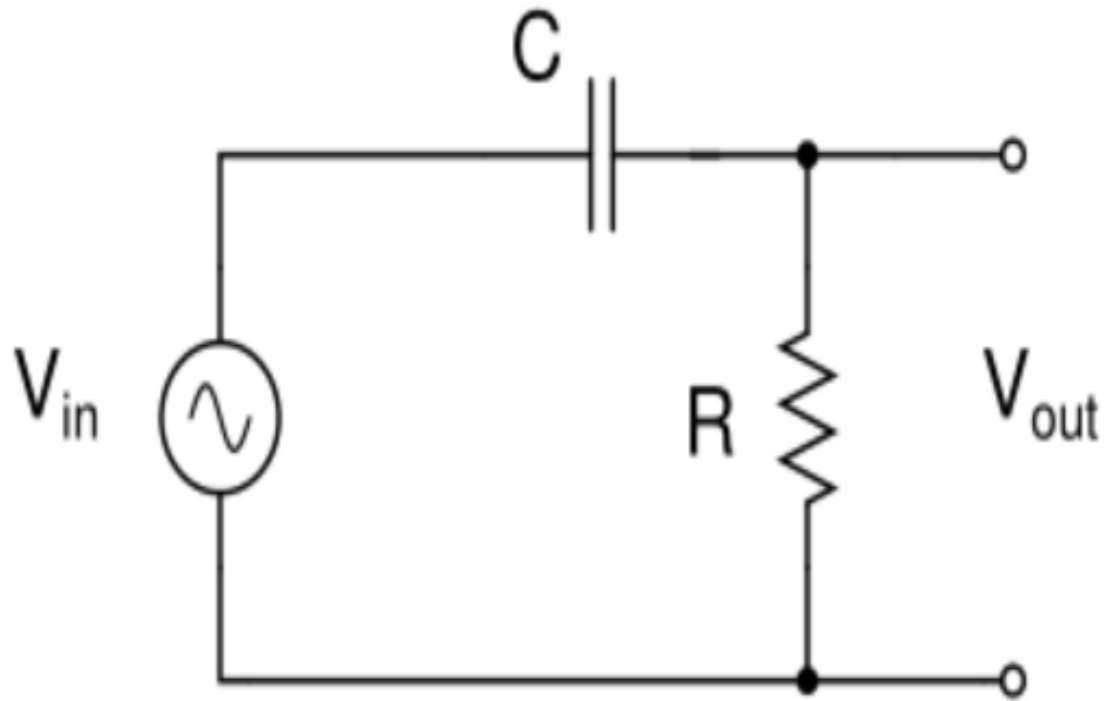

$R = 10\text{ k}\Omega$ and $C = 0.1\text{ }\mu\text{F}$

Measured Results

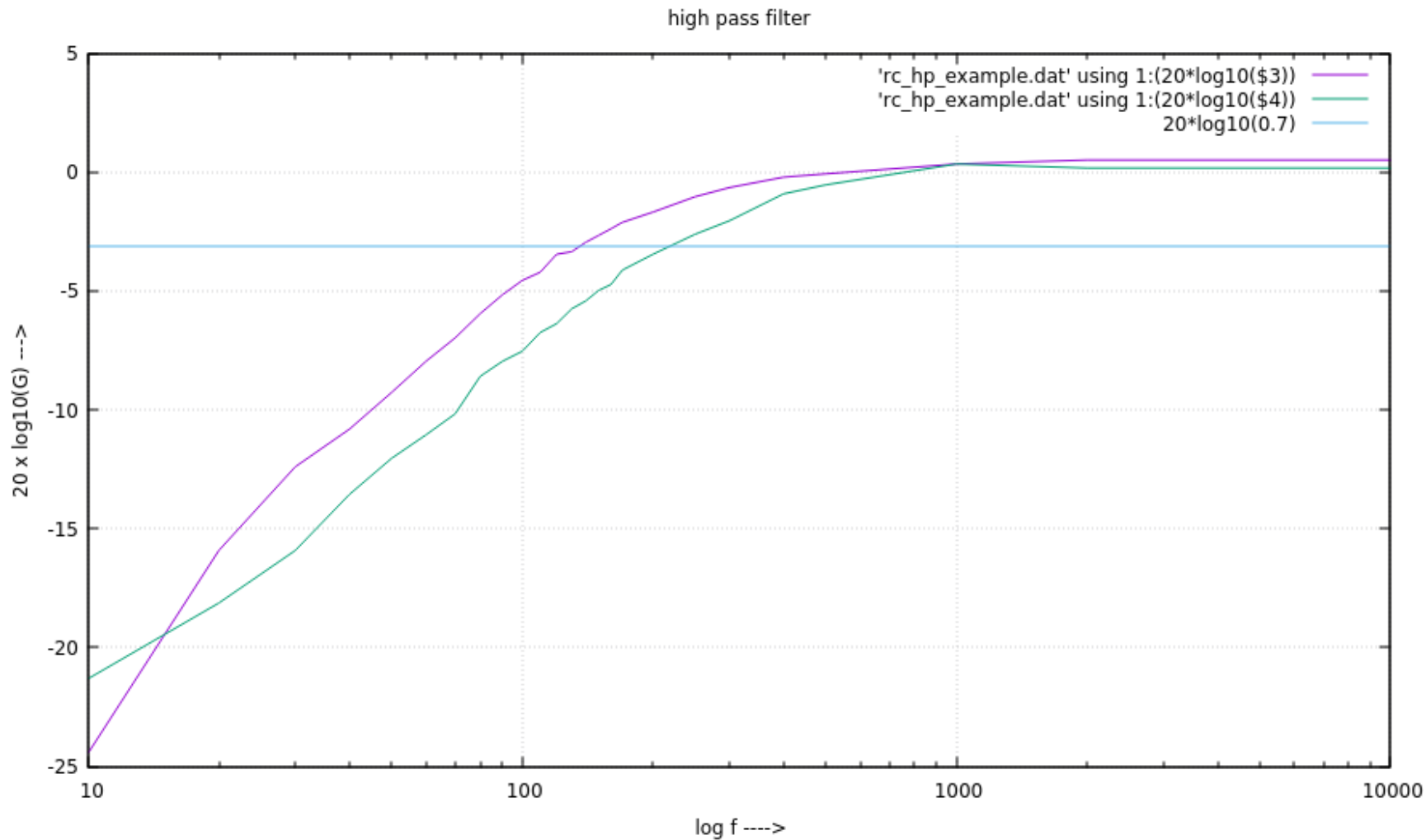

Nominal values:

$R = 10 \text{ k}\Omega$ and

$C = 0.1 \text{ }\mu\text{F}$

Actual:


$R = 9.7 \text{ k}\Omega$

$C = ??$

Green: Ceramic Capacitor


Light purple: Paper Capacitor (10% tolerance)

RC Bandpass Filter

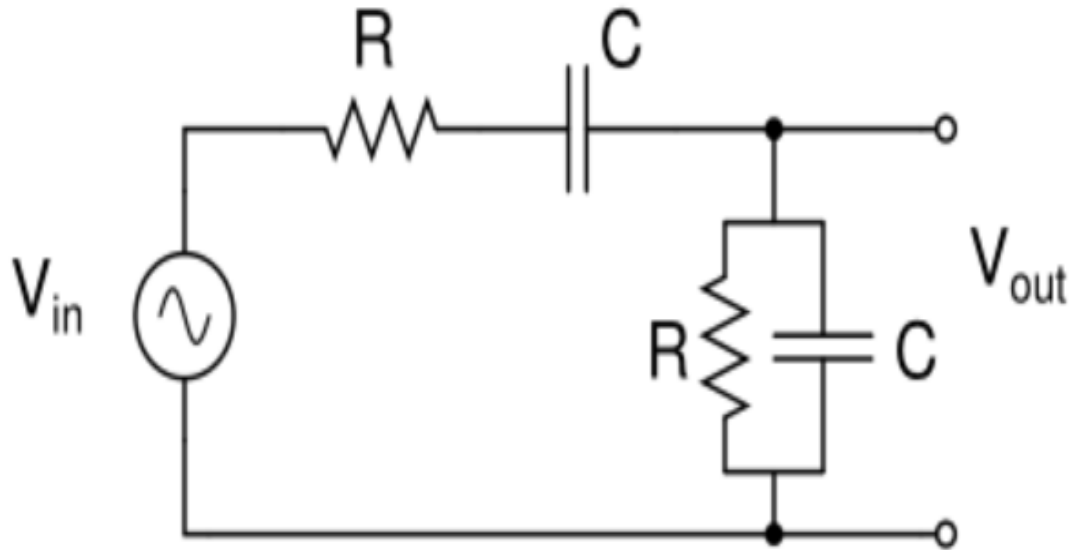

- $R = 10\text{ k}\Omega$ and $C = 0.1\text{ }\mu\text{F}$.
- Also called the 'Wien network'

Measured Results

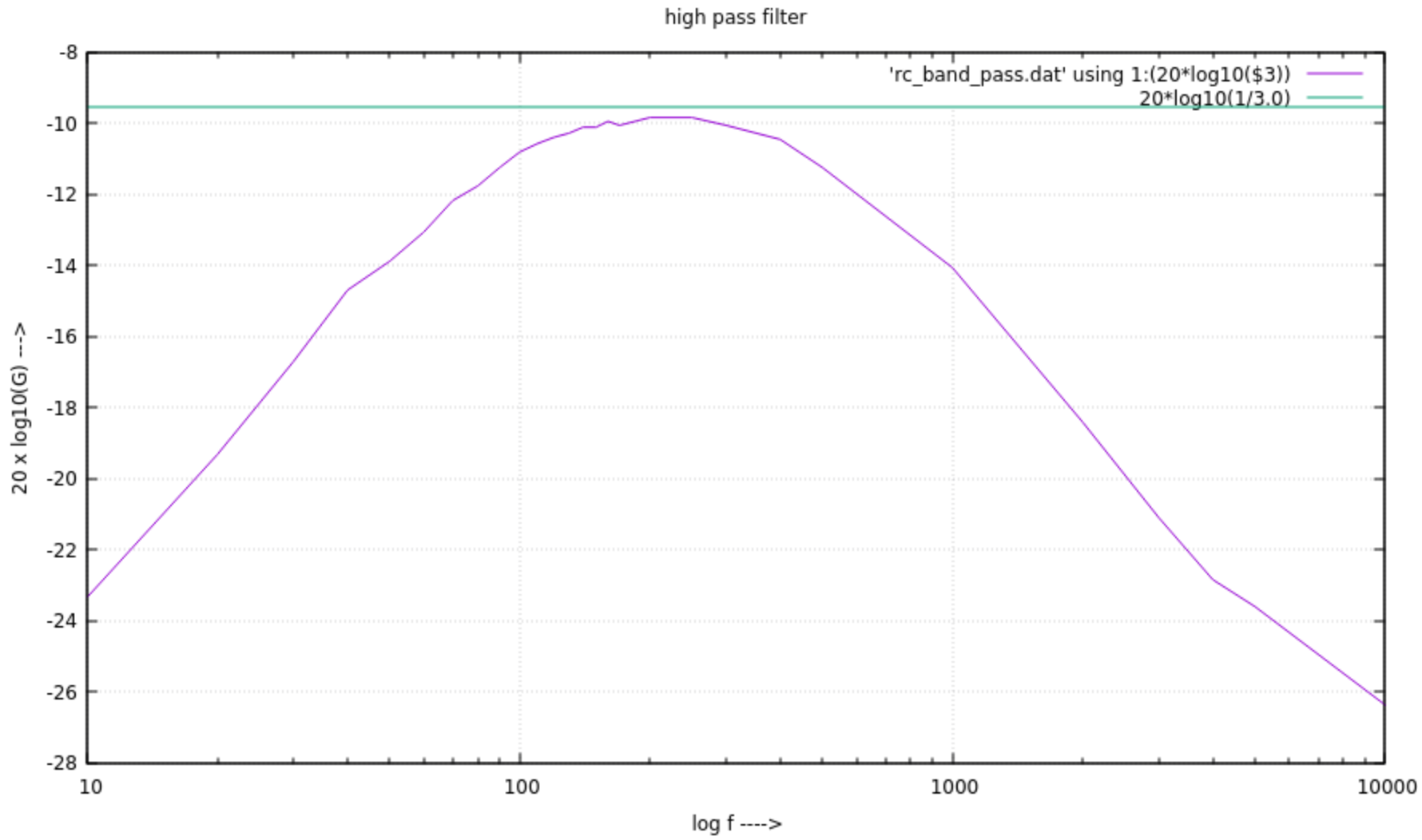

- Nominal values:
 $R = 10 \text{ k}\Omega$ and
 $C = 0.1 \text{ }\mu\text{F}$
- Actual:
 $R = 9.7 \text{ k}\Omega$
 $C = ??$
- Peak at $\omega = 1/RC$

- Theory

$$f_c = 1/(2\pi RC)$$

(R = 10 kΩ, C = 0.1 μF)


- $f_c = 159.2 \text{ Hz}$

Note the
difference in f_c



RC Band Pass		sine wave 1v(pk-pk)
		Ceramic cap
freq	Vin(pk-pk) V	Vout(pk-pk) V
10	1	0.068
20	1	0.108
30	1	0.146
40	1	0.184
50	1	0.202
60	1	0.222
70	1	0.246
80	1	0.258
90	1	0.274
100	1	0.288
110	1	0.296
120	1	0.302
130	1	0.306
140	1	0.312
150	1	0.312
160	1	0.318
170	1	0.314
200	1	0.322
250	1	0.322
300	1	0.314
400	1	0.3
500	1	0.274
1000	1	0.198
2000	1	0.12
3000	1	0.088
4000	1	0.072
5000	1	0.066
10000	1	0.048

RLC Bandpass Filter

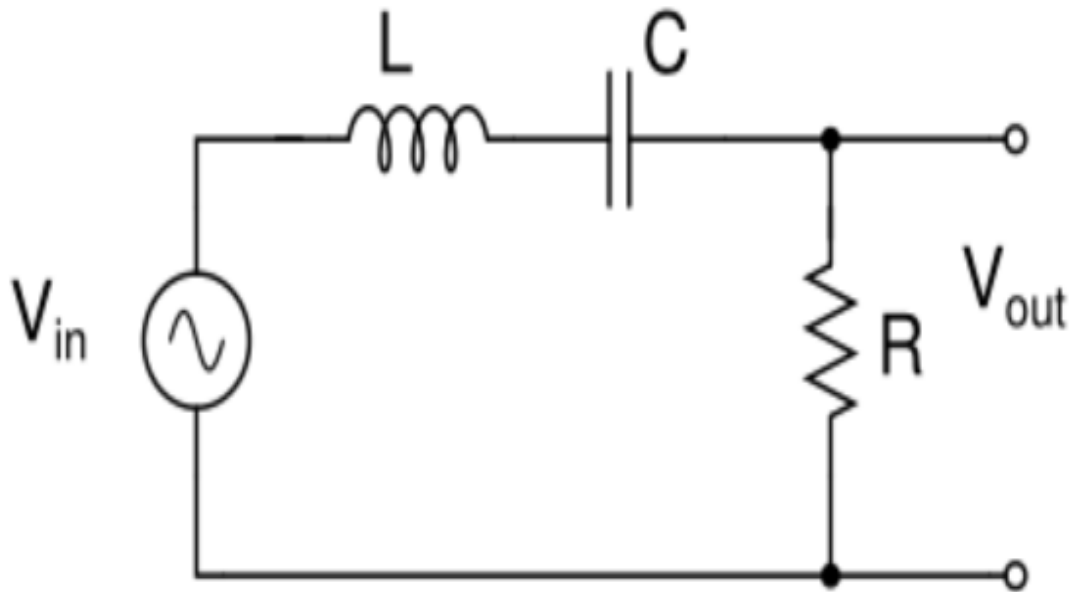

- $R = 1\text{ k}\Omega$, $L = 10\text{ mH}$ and $C = 0.1\text{ }\mu\text{F}$

- Will share the measured results later.

Lab Equipment


- DC Power Supply (Aplab)
- DMM (Aplab)
- DSO (Tektronix)
- AFG (Tektronix)

Aplab REGULATED DC POWER SUPPLY LQ 6324 S

W3-571




15.0 V

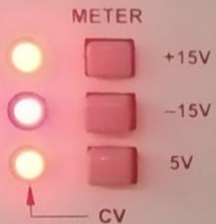

4.5 - 5.5V

12 - 15V

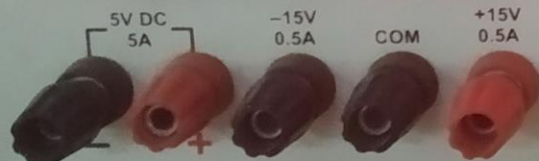

0.10 V


COARSE VOLTAGE FINE



SET O/V


0.00 A

COARSE CURRENT FINE

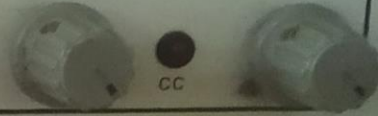

0 - 32V DC
0 - 2A

O/V

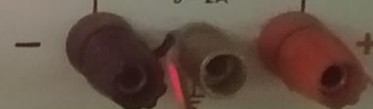


Aplab

0.17

W12-360

TRUE RMS DMM MODEL 1003

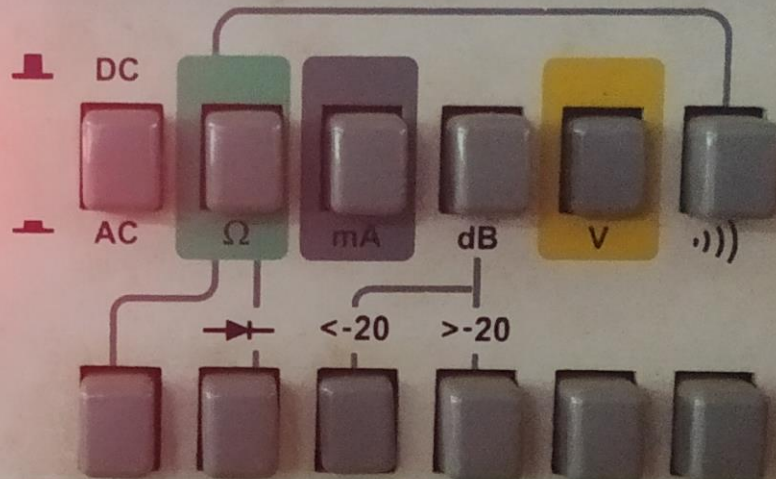

KΩ	200Ω	2	20	200	2M	20M
mA	200μA	2	20	200	1000	
V	200mV	2	20	200	1000	



Tektronix

TDS 1002B

TWO CHANNEL
DIGITAL STORAGE OSCILLOSCOPE

60 MHz
1 GS/s

Restart



USB
Flash Drive



CONTROL PANEL

FUNCTION KEYS: AUTORANGE, SAVE/RECALL, MEASURE, ACQUIRE, HELP, AUTOSET, RUN/STOP, REF MENU, UTILITY, CURSOR, DISPLAY, DEFAULT SETUP, SINGLE SEQ.

VERTICAL POSITION: Two rotary knobs for CH 1 and CH 2.

HORIZONTAL POSITION: One rotary knob.

TRIGGER LEVEL: One rotary knob.

MENUS: CH 1 MENU, MATH MENU, CH 2 MENU, HORIZ MENU, TRIG MENU.

SCALING: VOLTS/DIV (rotary knob), SEC/DIV (rotary knob).

SET POINTS: SET TO ZERO, SET TO 50%.

FORCED TRIGGER: FORCE TRIG, TRIG VIEW.

CH 1: BNC input connector.

CH 2: BNC input connector.

EXT TRIG: BNC input connector.


SAFETY: 300V CAT II warning symbol and ground symbol.

OTHER FEATURES: SAVE, PRINT, PROBE CHECK, PROBE COMP (~5V@1kHz).




- CRO Probes,
1X/10X facility
- Locate the
Adjustable
Capacitor
&
- 1X/10X switch

CRO Probes

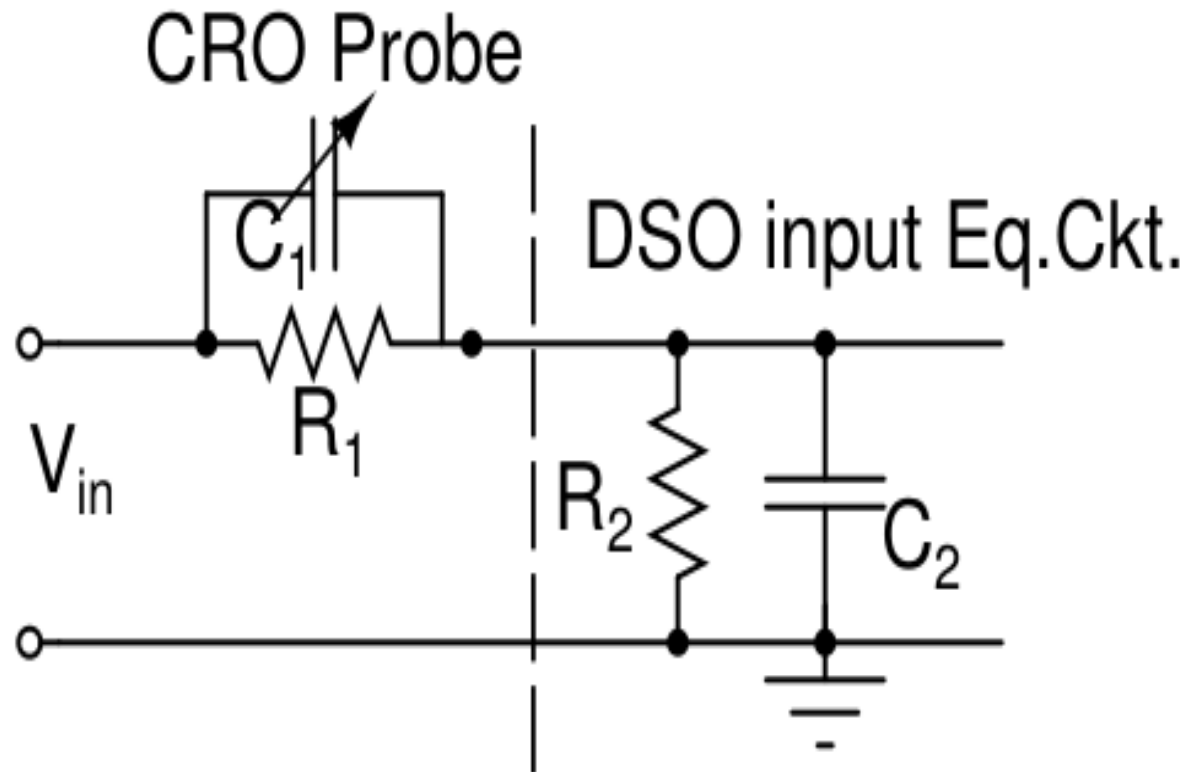

- CRO/DSO input resistance = 1 Mohm
- Input capacitance = 10 to 20 pF (typ)
- High RC time constant
 - Pulse Measurements can go very wrong
- CRO Probes ('Compensated Attenuators')
 - Cancel the input capacitance by adding and adjusting another capacitor in series

Arbitrary Function Generator

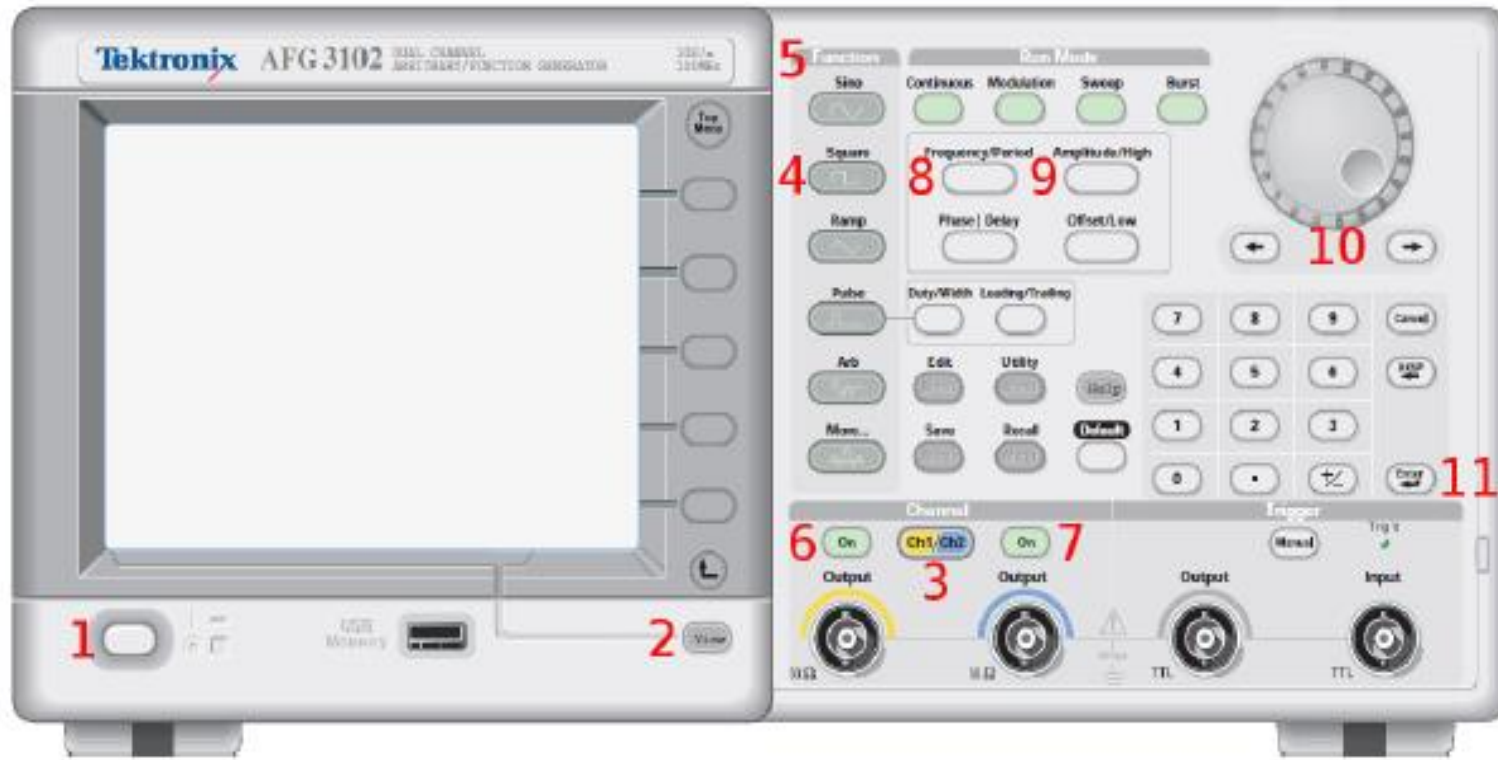

- All types of Waveforms
- Can set Amplitudes and offset
- Can choose output Load