

EE230 : Analog Circuits Lab


Mayur Ware | 19D070070, Section 6

Experiment 1: Familiarization with NGSPICE Circuit Simulator and Lab Equipment

July 31, 2021

NGSPICE Simulation of RC and RLC Circuits

RC Integrator

 

Integrator.CIR :

RC Integrator Circuit [Mayur Ware, 19D070070]

*Resistor connected between In and Out

R1 In Out 10k

*Capacitor connected between Out and GND

C1 Out GND 0.1u

*Voltage Source between In and GND

Vin In GND pulse(0 5 0 0 0 10m 20m)

.tran 0.1m 100m

*Control Commands

.control

run

set color0 = white

set color1 = black

set color2 = blue

set color3 = red


set xbrushwidth = 2

plot V(In) V(Out)


.endc

.end

Plots :

 


Case 1 : $T = 10 \tau$

 

Case 2 : $T = 0.05 \tau$

As, we can notice, V_{Out} is settling properly in Case 1, whereas it is not settling in Case 2 due to very low time period

RC Differentiator

 

Differentiator.CIR :

RC Differentiator Circuit [Mayur Ware, 19D070070]

*Capacitor connected between In and Out

C1 In Out 0.1u

*Resistor connected between Out and GND

R1 Out GND 10k

*Voltage Source between In and GND

Vin In GND pulse(0 5 0 0 0 10m 20m)

.tran 0.1m 100m

*Control Commands

.control

run

set color0 = white

set color1 = black

set color2 = blue

set color3 = red


set xbrushwidth = 2

plot V(In) V(Out)


.endc

.end

Plots :

 


Case 1 : $T = 10 \tau$

 

Case 2 : $T = 0.05 \tau$

As, we can notice, V_{Out} is settling properly in Case 1, whereas it is not settling in Case 2 due to very low time period

RC Lowpass Filter

 

RC_Low.CIR :

RC Lowpass Filter Circuit [Mayur Ware, 19D070070]

* Resistor connected between In and Out

R1 In Out 10k

* Capacitor connected between Out and GND

C1 Out GND 0.1u

* Voltage Source between In and GND

Vin In GND dc 0 ac 1

.ac DEC 10 1 10e6

* Control Commands

.control

run

set color0 = white

set color1 = black

set color2 = blue

set color3 = red


set xbrushwidth = 2

plot Vdb(In) Vdb(Out)


.endc

.end

Plots :

 


Case 1 : Frequency without log scale

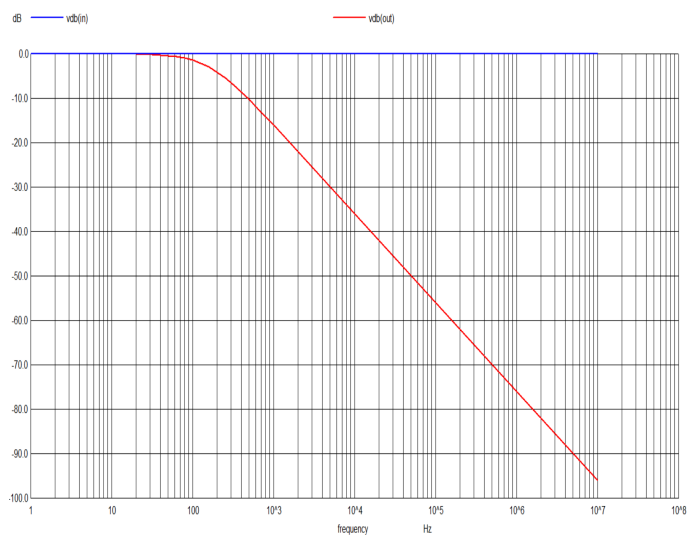

Case 2 : Frequency in log scale

RC Highpass Filter

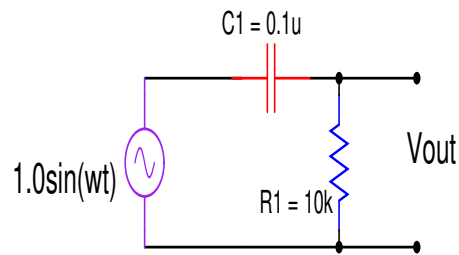

RC_High.CIR :

RC Highpass Filter Circuit [Mayur Ware, 19D070070]

*Capacitor connected between In and Out

C1 In Out 0.1u

*Resistor connected between Out and GND

R1 Out GND 10k

*Voltage Source between In and GND

Vin In GND dc 0 ac 1

.ac DEC 10 1 10e5

*Control Commands

.control

run

set color0 = white

set color1 = black

set color2 = blue

set color3 = red


set xbrushwidth = 2

plot V(In) V(Out)


.endc

.end


Plots :

 

Case 1 : Frequency without log scale

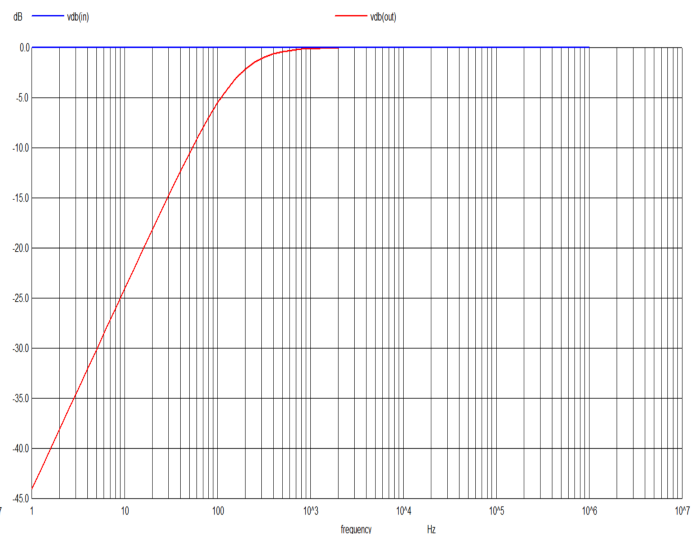

Case 2 : Frequency in log scale

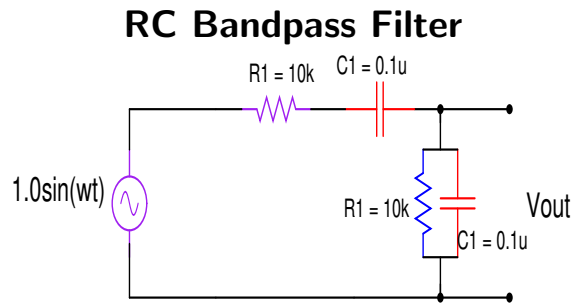

RC_Bandpass.CIR :

RC Bandpass Filter Circuit [Mayur Ware, 19D070070]

*Resistor connected between In and Out

R1 In Mid 10k

*Capacitor connected between Out and GND

C1 Mid Out 0.1u

*Parallel RC Components

R2 Out GND 10k

C2 Out GND 0.1u

*Voltage Source between In and GND

Vin In GND dc 0 ac 1

.ac DEC 10 1 10e5

*Control Commands

.control

run

set color0 = white

set color1 = black

set color2 = blue

set color3 = red

set xbrushwidth = 2

plot Vdb(In) Vdb(Out)

meas ac peak MAX vmag(Out)

meas ac fpeak WHEN vmag(Out)=peak

let f3db = peak/sqrt(2)


meas ac f1 WHEN vmag(Out)=f3db RISE=1

meas ac f2 WHEN vmag(Out)=f3db FALL=1

.endc

.end

Plots :

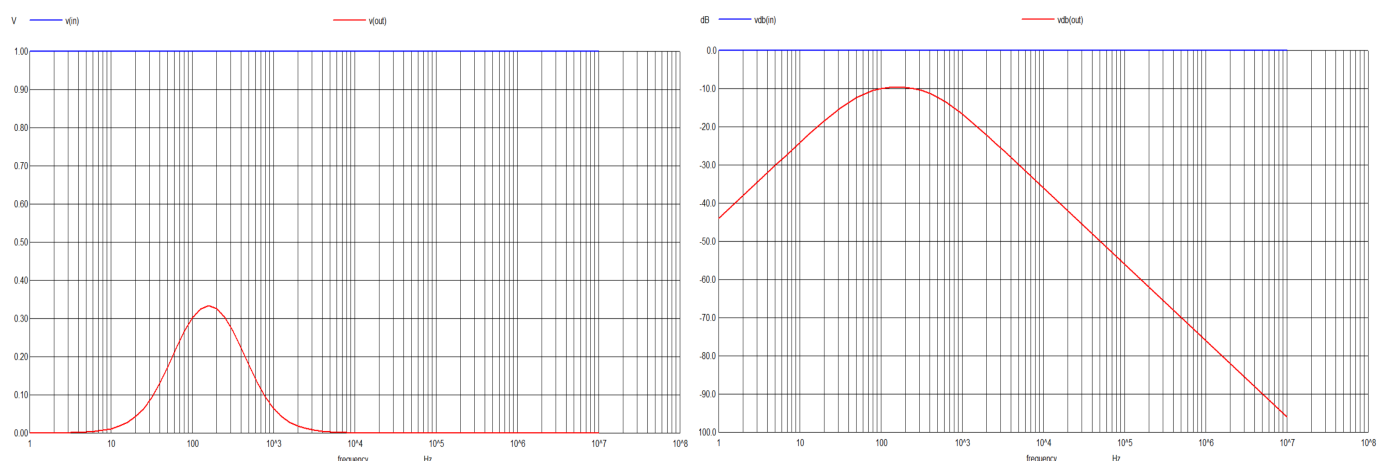

Case 1 : Frequency without log scale

Case 2 : Frequency in log scale


Transfer Function for this circuit is $\frac{1000s}{s^2 + 3000s + 10^6}$. By comparing it with $\frac{a_1 s}{s^2 + \frac{\omega_0}{Q}s + \omega^2}$ where Upper and Lower -3dB frequencies

$= \omega_1, \omega_2 = \omega_0 \sqrt{1 + \frac{1}{4Q^2}} \pm \frac{\omega_0}{2Q}$ and Center-frequency gain $= \frac{a_1 Q}{\omega_0}$

Theoretical Results : Centre Frequency (f_0) = 159.15 Hz, Lower Frequency (f_L) = 47.74 Hz and Upper Frequency (f_H) = 525.51 Hz

Simulation Results : = Centre Frequency (f_0) = 1.584891e+02, Lower Frequency (f_L) = 4.838534e+01 and Upper Frequency (f_H) = 5.276607e+02

RLC Bandpass Filter

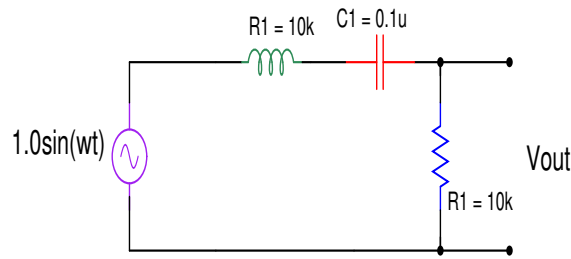

RLC_Bandpass.CIR :

RLC Bandpass Filter Circuit [Mayur Ware, 19D070070]

*Resistor connected between In and Mid

L1 In Mid 10m

*Capacitor connected between Out and GND

C1 Mid Out 0.1u

*Resistor connected between Out and GND

R1 Out GND 1k

*Voltage Source between In and GND

Vin In GND dc 0 ac 1

.ac DEC 10 1 10e7

*Control Commands

.control

run

set color0 = white

set color1 = black

set color2 = blue

set color3 = red

set xbrushwidth = 2

*plot Vdb(In) Vdb(Out)

meas ac peak MAX vmag(Out)

meas ac fpeak WHEN vmag(Out)=peak

let f3db = peak/sqrt(2)


meas ac f1 WHEN vmag(Out)=f3db RISE=1

meas ac f2 WHEN vmag(Out)=f3db FALL=1


.endc

.end

Plots :

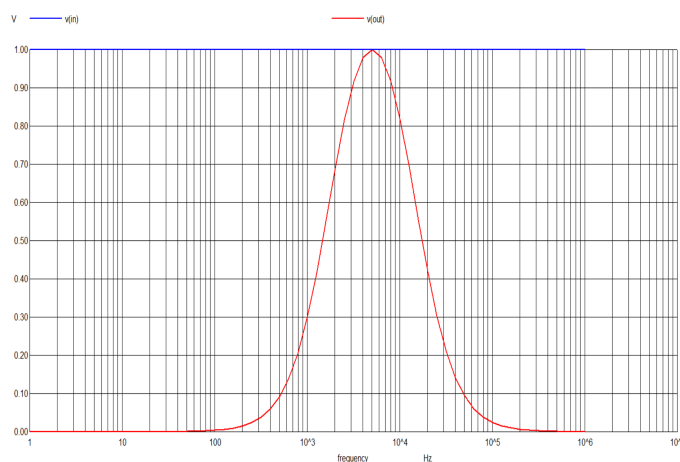

Case 1 : Frequency without log scale

 

Case 2 : Frequency in log scale

Transfer Function for this circuit is $\frac{10^5 s}{s^2 + 10000s + 10^9}$. By comparing it with $\frac{a_1 s}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$ where Upper and Lower -3dB frequencies $= \omega_1, \omega_2 = \omega_0 \sqrt{1 + \frac{1}{4Q^2}} \pm \frac{\omega_0}{2Q}$ and Center-frequency gain $= \frac{a_1 Q}{\omega_0}$

Theoretical Results : Center Frequency (f_0) = 174605.15 Hz, Lower Frequency (f_L) = 1475.98 Hz and Upper Frequency (f_H) = 17460.64 Hz

Simulation Results : Center Frequency (f_0) = 1.74611e+05, Lower Frequency (f_L) = 1.468642e+03 and Upper Frequency (f_H) = 1.745991e+04

● Major Learnings from this Experiment :

- Circuit simulations using NGSpice Software
- Introduction of Lab Equipments
- Xcircuit Software for Circuit Drawing
- Various RC and RLC Filter Circuits

● Challenges faced :

- Unfamiliarities with NGSpice Syntax
- Calculation of Center, Upper and Lower -3dB Frequencies

● Questions or Clarifications (if any) :

None

References

WEL Resources for NGSpice