

# Expt 4 - Current Source, Current Mirror, and Differential Pair

EE 230 Analog Circuits Lab


Joseph John

2021-22/I

# Summary

- Expt 3 – Frequency Response of a CE Amp
  - Common Mistakes
- Expt 4 - Current Source, Current Mirror, and Differential Pair

# Frequency Response of a CE Amp

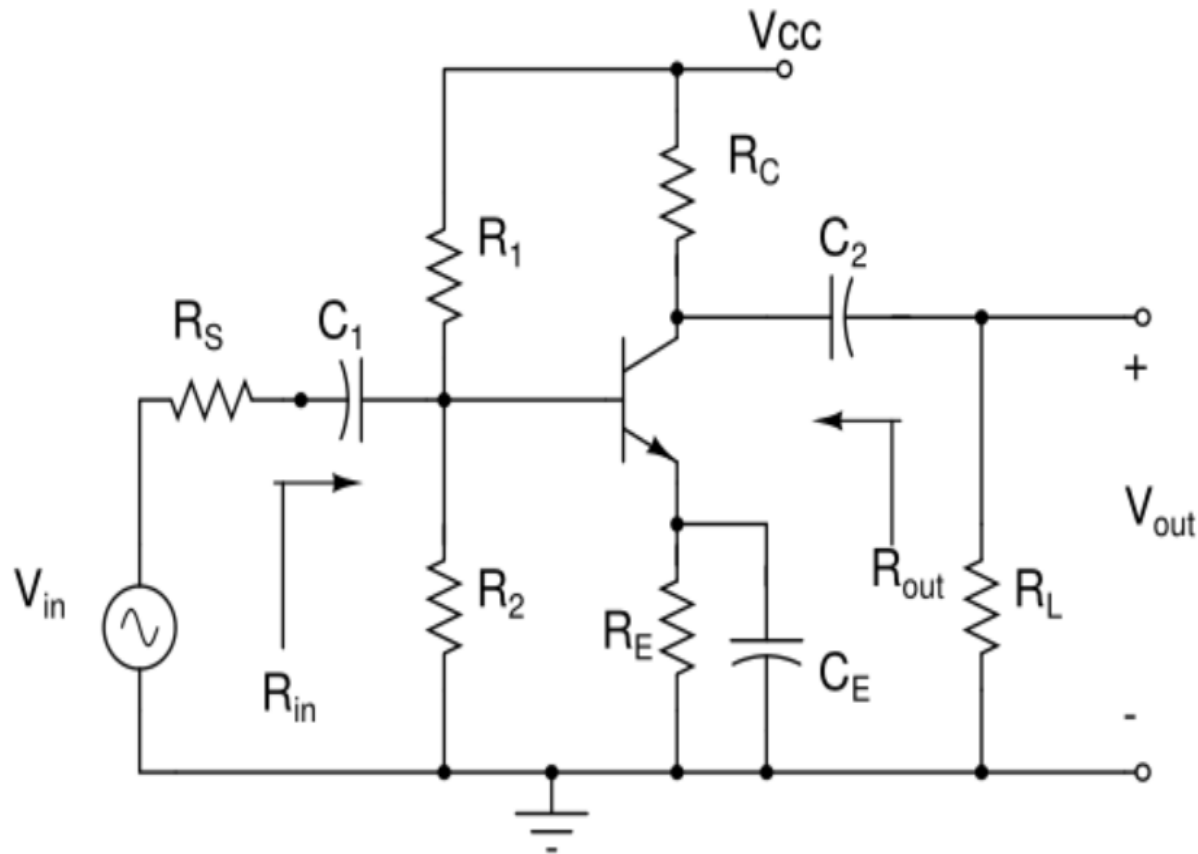


- $f_L$  – Low Freq Cut Off
- $f_H$  – High Freq Cut Off

# Expt 4

- Current Source,
- Current Mirror, and
- Differential Pair
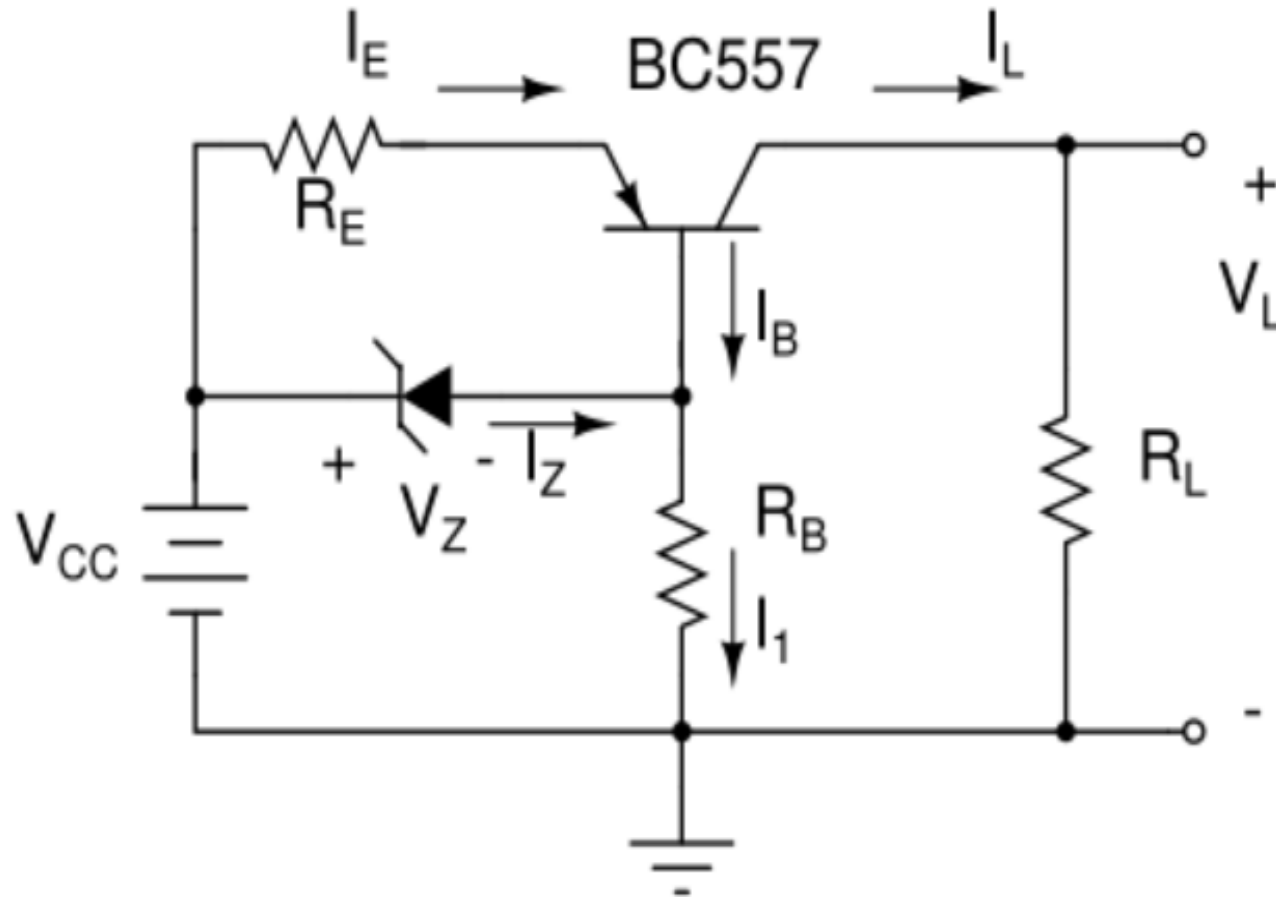
## Part A: BJT Current Source (using a Zener diode and a *pn*p transistor)




- Features
- $I_L$  can be changed by changing  $R_E$
- Works for reasonably large values of  $R_L$

# Current source Characteristics


- Voltage Sources – Ideal vs Practical
- Current Sources – Ideal vs Practical

# BJT Current Source

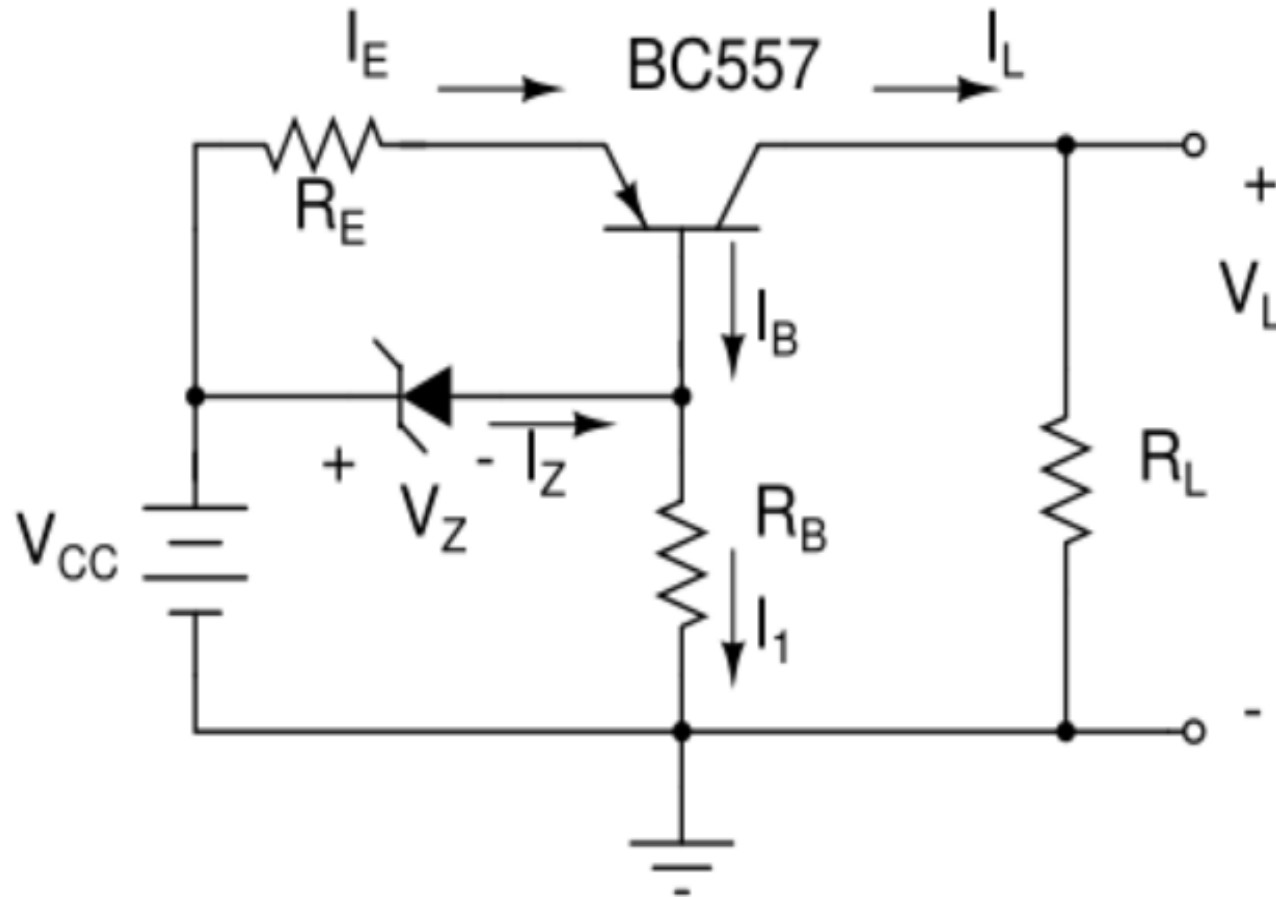

- Operation
- Ideally should work for any value of  $R_L$
- $R_L \uparrow$  ,  $V_L \uparrow$
- BJT will saturate for high  $R_L$  values
- For a given circuit there is an  $R_{Lmax}$

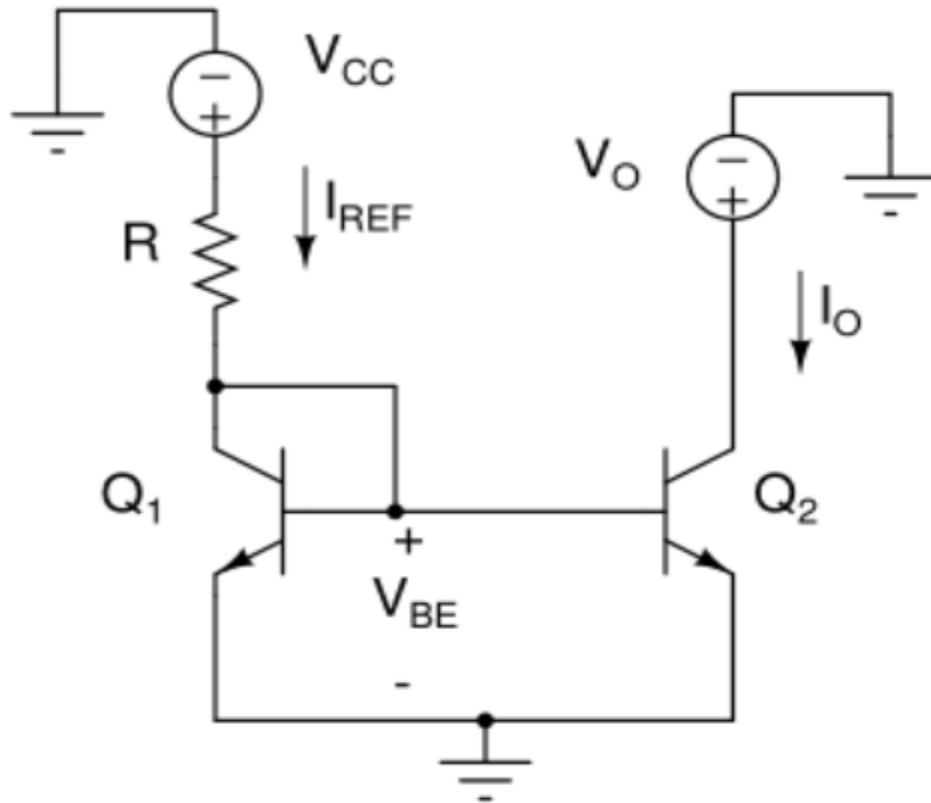
## Part B: Current Source (using a Current Mirror)



- Current sources extensively used
- IC biasing
- Active loads
- Current Sources made of BJT arrays (ICs)
- Advantage
  - Monolithic
  - Better matching of  $V_{BE}$




# LM 3046 *npn* Arrays

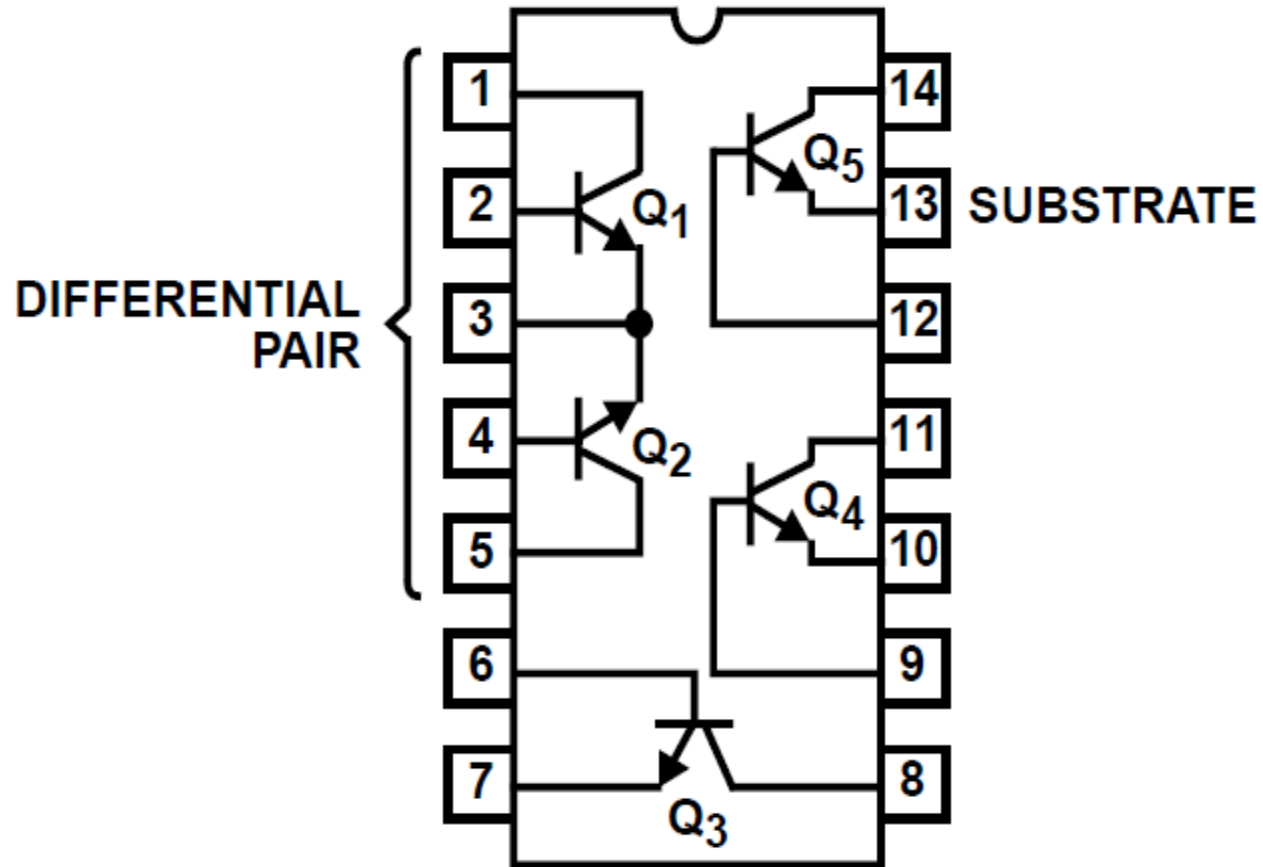

- 5 npn BJTs
- DC to 120 MHz
- One diff pair
- Monolithic design
  - $V_{BE}$  match (+/- 5 mV)
- $I_C$  up to 10 mA
- $V_{CE}$  up to 10V
- Max Power Diss: 300 mW (single BJT)

# Measured Results

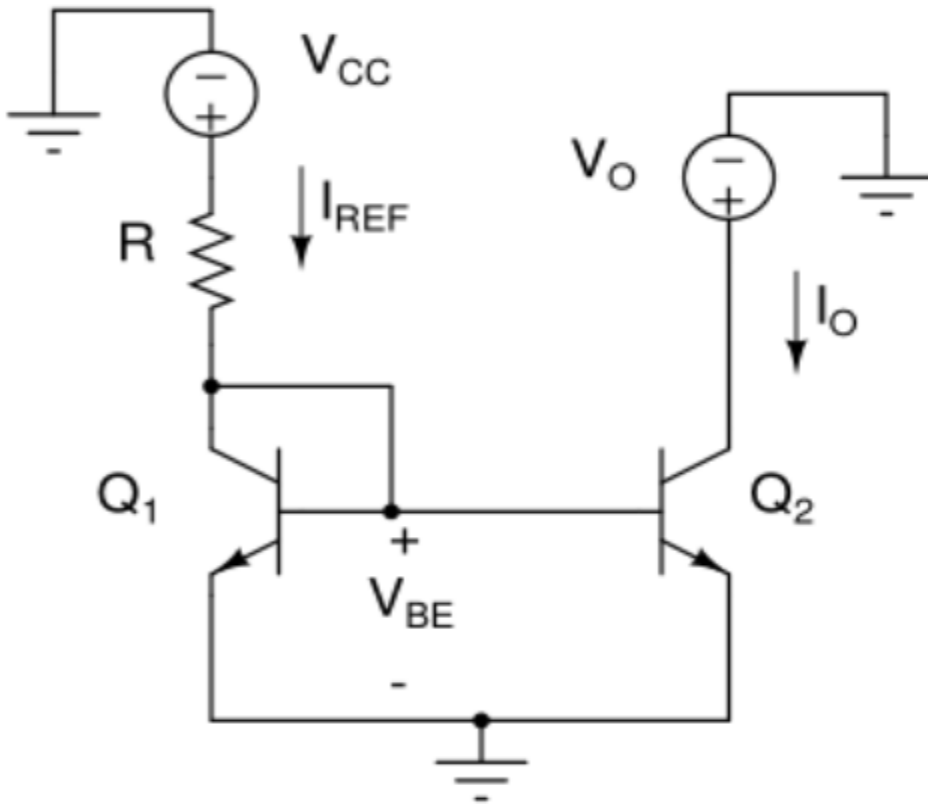


- $V_{CC} = 12\text{ V}$ ,  $R = 10\text{ k}\Omega$ ,  $V_{BE} = 0.7\text{ V}$

- $V_O : 1\text{ V}$  ,  $I_O = 1.125\text{ mA}$


- $V_O : 5\text{ V}$  ,  $I_O = 1.2\text{ mA}$

## Part C: Differential Pair

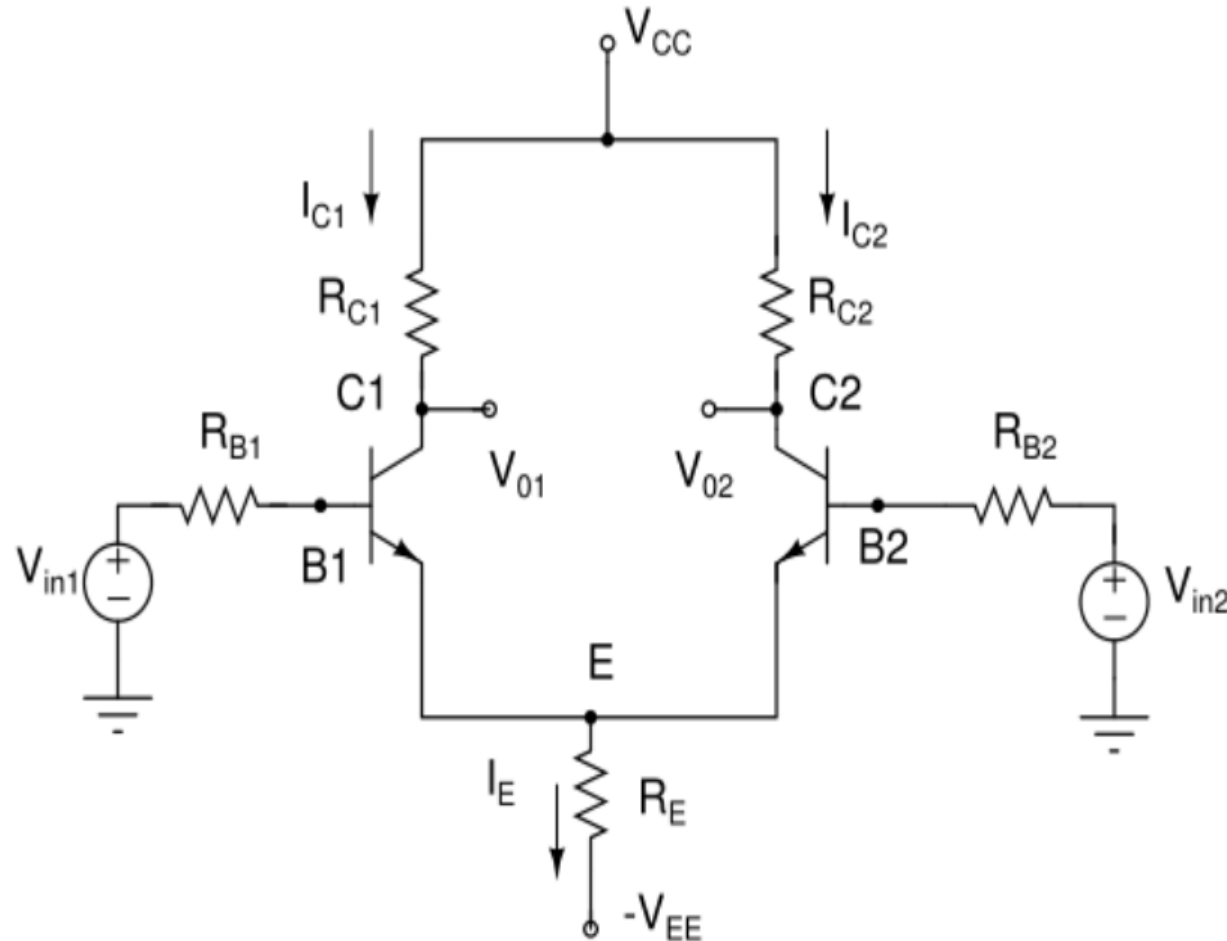


- Identical BJTs (hence IC BJT arrays preferred)
- Circuit symmetric
- Current switching
- $R_E$  for simple Diff pair
- $R_E$  may be replaced with a current source

# Single-ended Gain

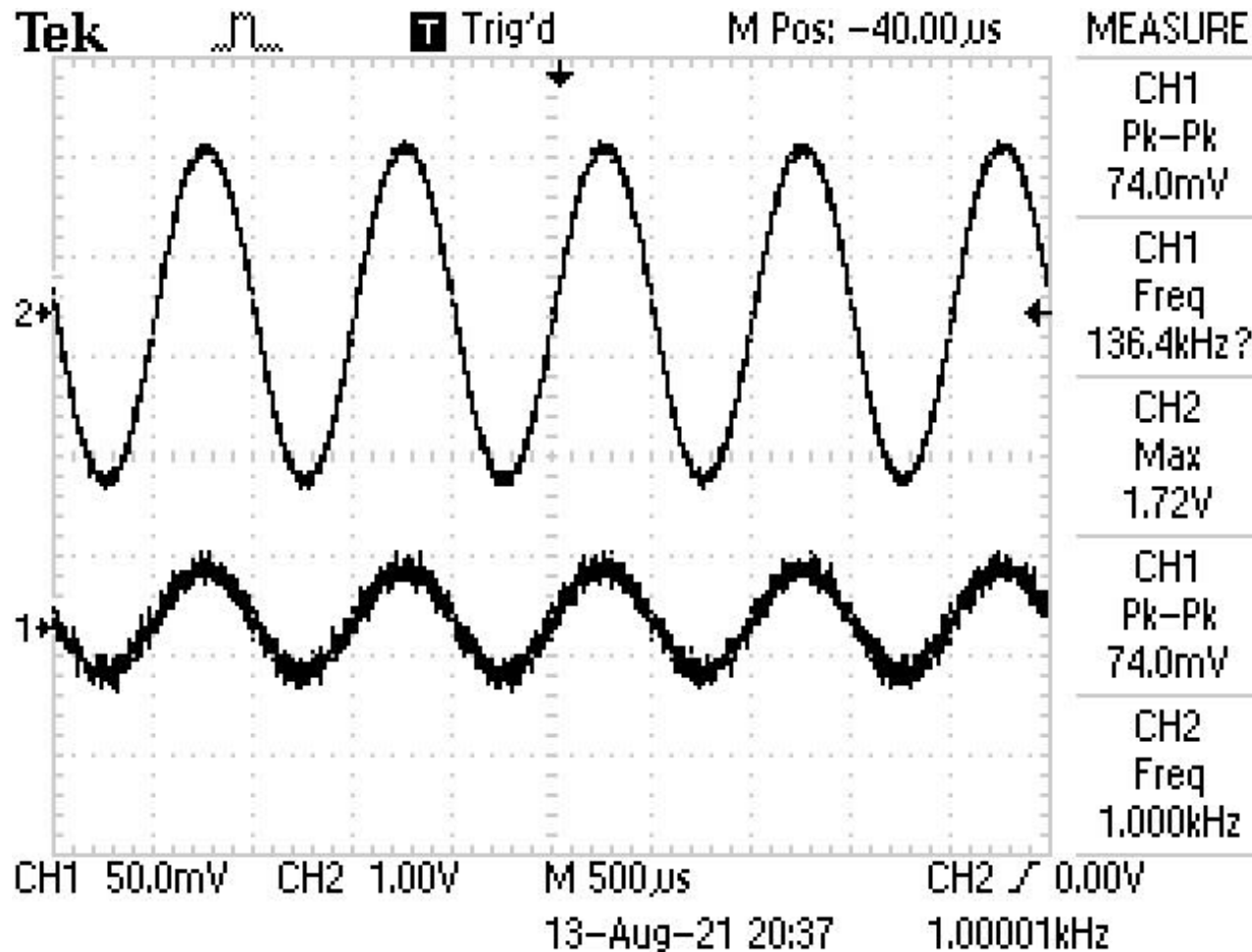


- $V_{in1} - 50\text{mVp-p}$
- 1 kHz
- $V_{O2} - 3.6 \text{ Vp-p}$
- Voltage Gain: 72 V/V

# Both Outputs

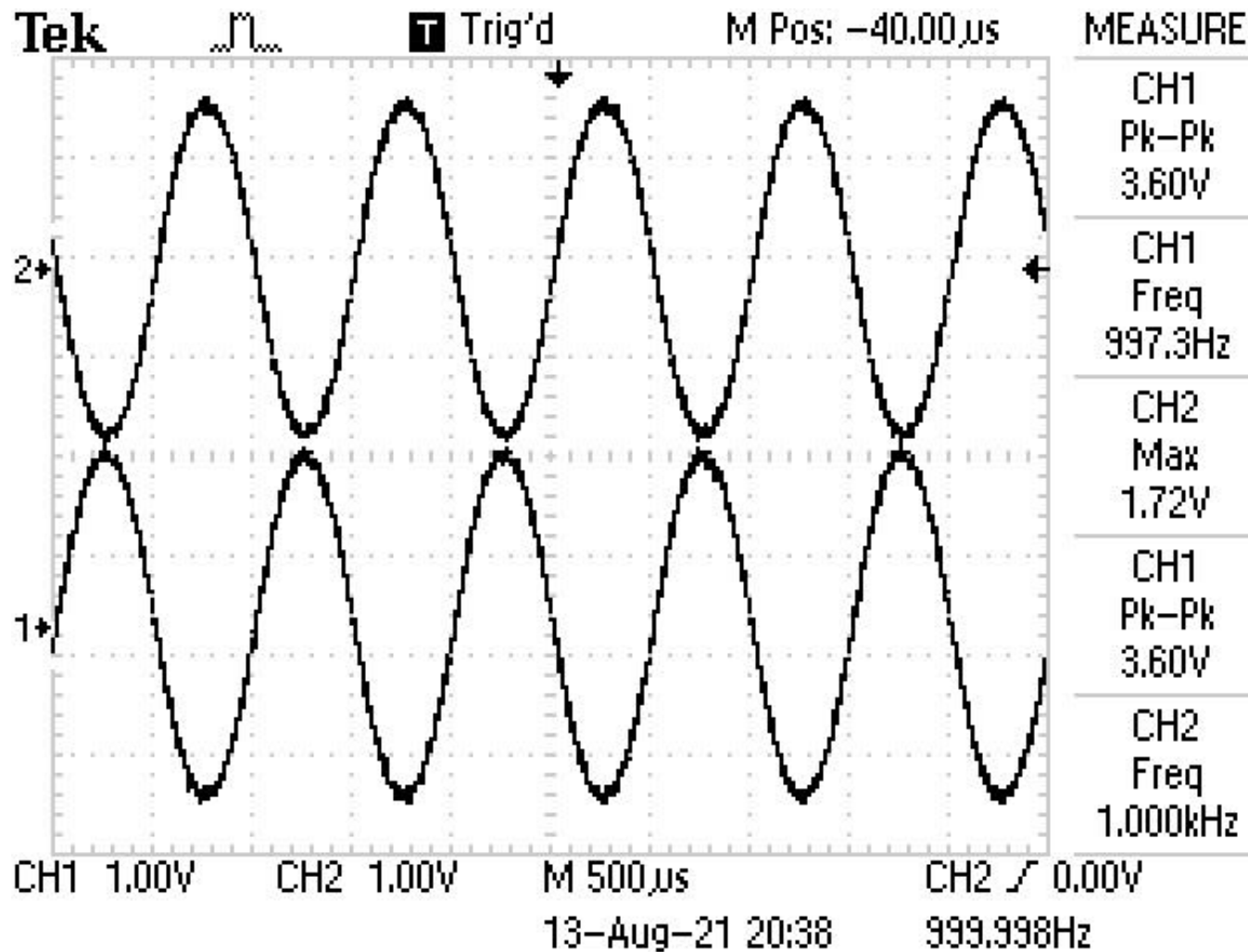


- $V_{in1} - 50\text{mVp-p}$
- 1 kHz
- $V_{O1}$  and  $V_{O2} - 3.6\text{ Vp-p}$
- Voltage Gain: 68 V/V
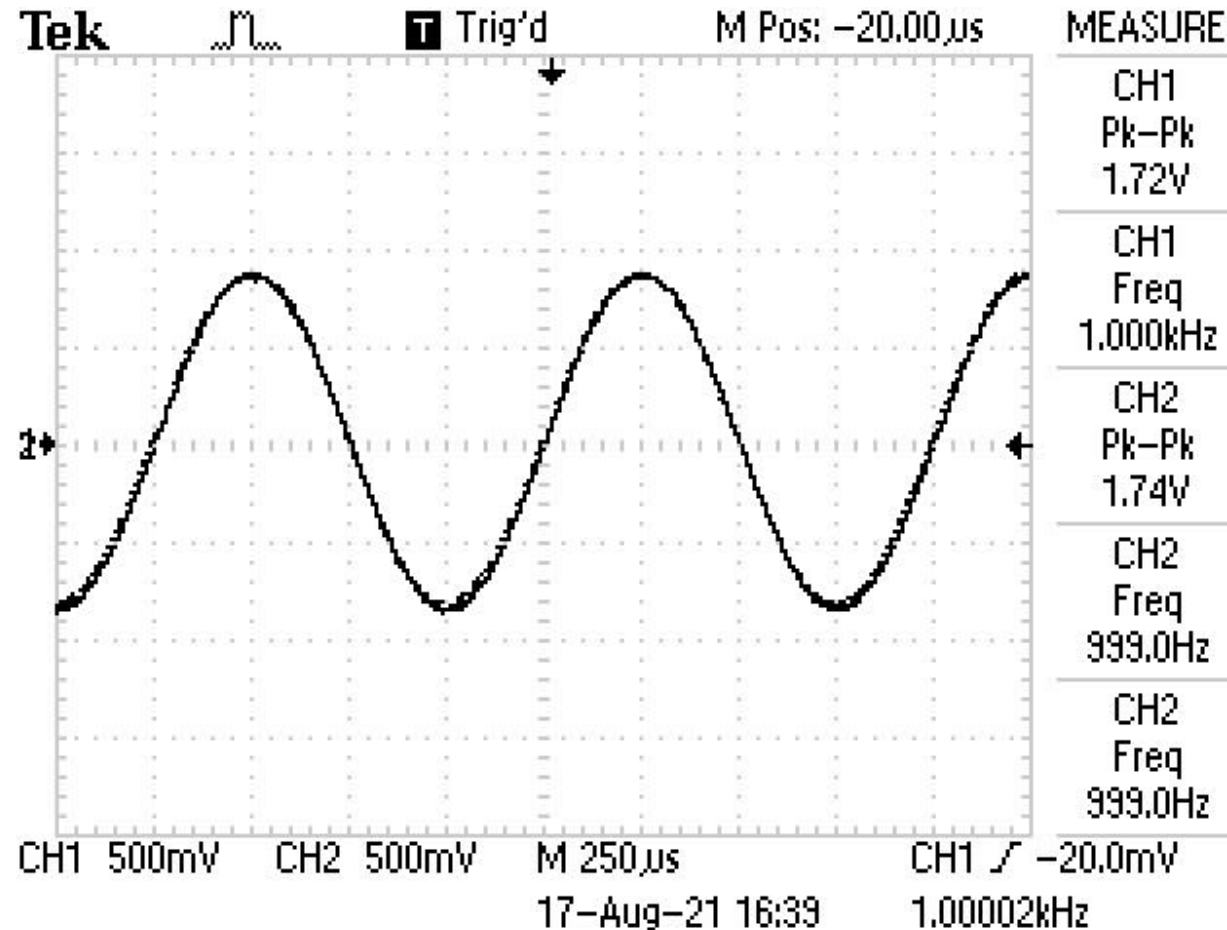
# Both Outputs (Overlapped) – $V_{O2}$ inverted



- $V_{O1}$  and  $V_{O2}$  together

# Common-mode Operation

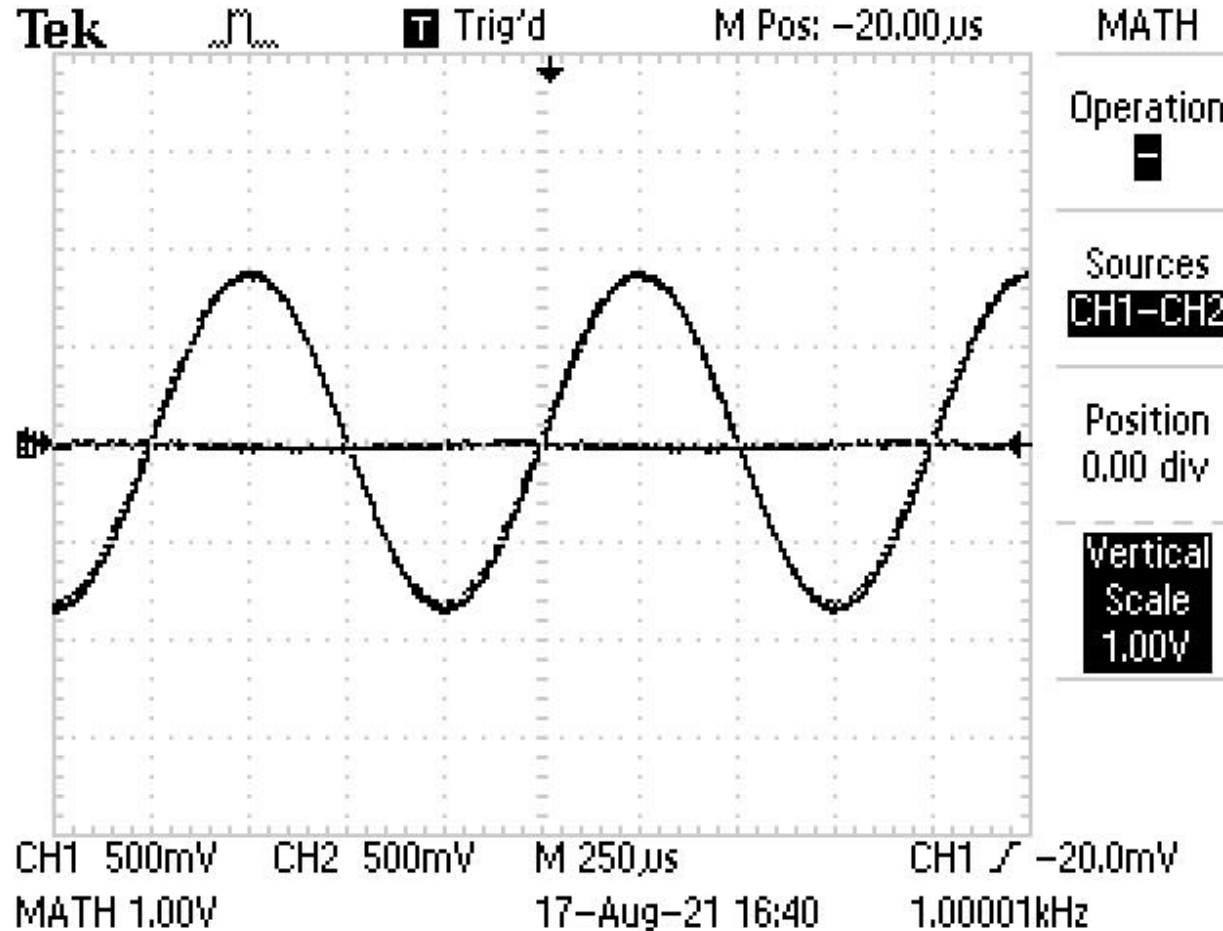

- $V_{in1} = V_{in2} = 5 \sin \omega t$
- Differential Output (Through DSO Math Operation)