


EE230 : Analog Circuits Lab

Mayur Ware | 19D070070, **Section 6**

Experiment 4 : Current Source, Current Mirror, and Differential Pair

August 21, 2021

BJT Current Source

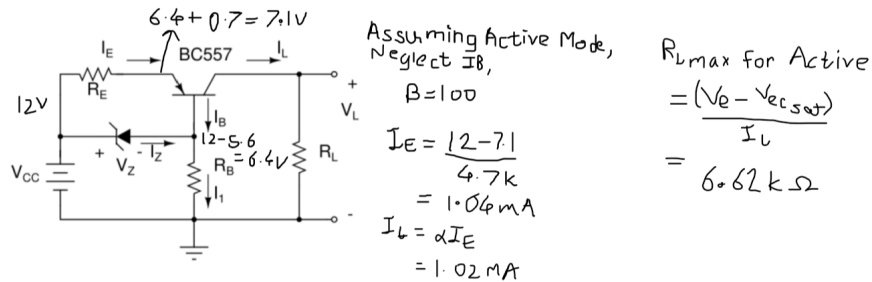

19D070070 | Mayur Ware

*Common-Emitter Amplifier: Biasing Circuit

.model bc557a NPN IS=10f BF=200 ISE=10.3f IKF=50m NE=1.3

+ BR=9.5 VAF=80 IKR=12m ISC=47p NC=2 VAR=10 RB=280 RE=1 RC=40

+ tr=0.3u tf=0.5n cje=12p vje=0.48 mje=0.5 cjc=6p vjc=0.7 mjc=0.33 kf=2f

Q1 4 3 2 bc557a

*Voltage Sources

Vin 1 GND 12

VI 5 GND dc 0

Ve 6 2 dc 0

Vb 3 7 dc 0

X1 3 1 DI_1N4734A

*Resistors

Re 1 6 4.7k

Rb 7 GND 2.2k

RI 4 5 1k

*Control Commands

.op

.control

run


print i(V2) i(V1) V(2) V(3) V(5)

.endc

.end


Simulation Results (Operating Point) :

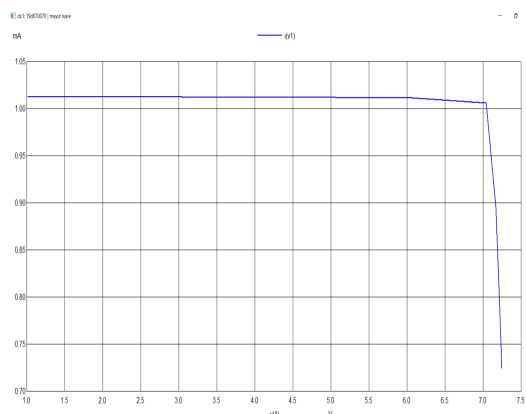$i(v_e) = 1.026180e-03$ $i(v_b) = 2.961952e-03$ $i(v_l) = 1.012825e-03$ $v(e) = 7.176954e+00$ $v(b) = 6.516294e+00$ $v(c) = 1.012825e+00$



I learned use and benefits of Zener diode in pnp transistor circuit.

BJT Current Mirror based Current Source

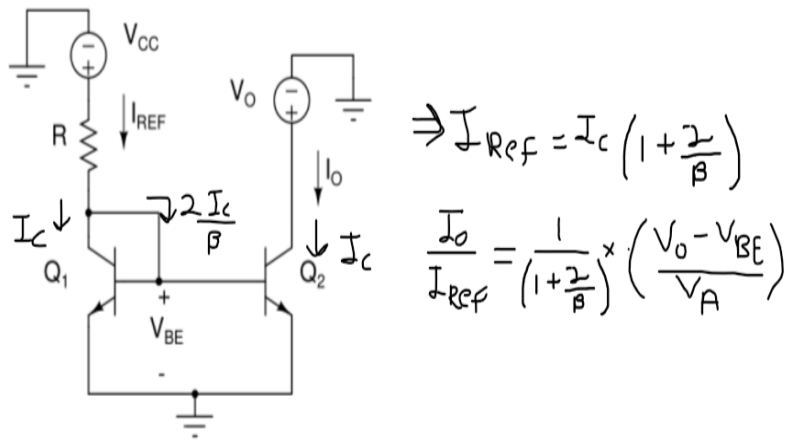

19D070070 | Mayur Ware

*BJT Current Mirror Circuit

.model bc547a NPN IS=10f BF=100 ISE=10.3f IKF=50m NE=1.3

+ BR=9.5 VAF=200 IKR=12m ISC=47p NC=2 VAR=10 RB=280 RE=1 RC=40

+ tr=0.3u tf=0.5n cje=12p vje=0.48 mje=0.5 cjc=6p vjc=0.7 mjc=0.33 kf=2f

*BJT

Q1 2 3 GND bc547a

Q2 5 3 GND bc547a

*Voltage Sources

Vcc 1 GND 12

Vo 4 GND 1

V1 4 5 dc 0

V2 2 3 dc 0

*Resistors

R 1 2 10k

*Control Commands

.dc Vo 1 5 0.5

.control


run

plot i(V1)


.endc

.end

Plots :

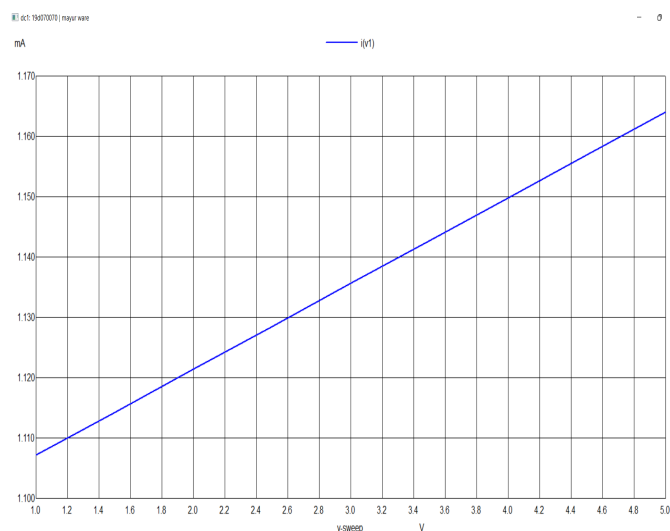

$V_A = 80V$

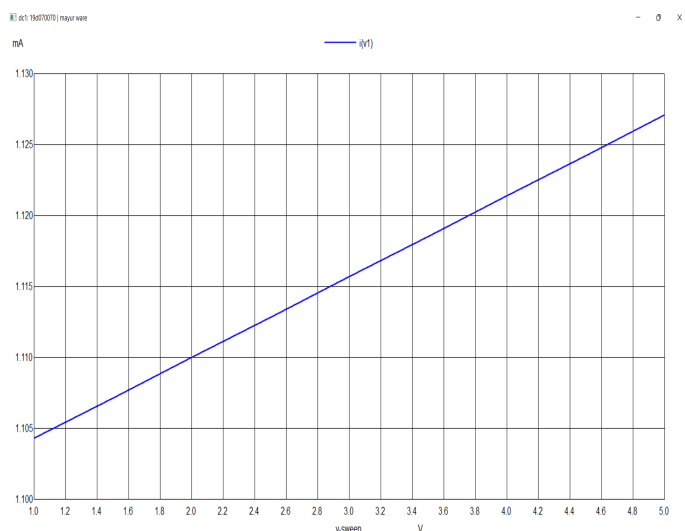

$V_A = 100V$

Observations :


For both cases, plot of I_O is a straight line. But, for $V_A = 100V$, I_O values are slightly less than $V_A = 80V$

Learning :

I learned how to change V_A value in a transistor model.

Differential Pair

DC Operating Values

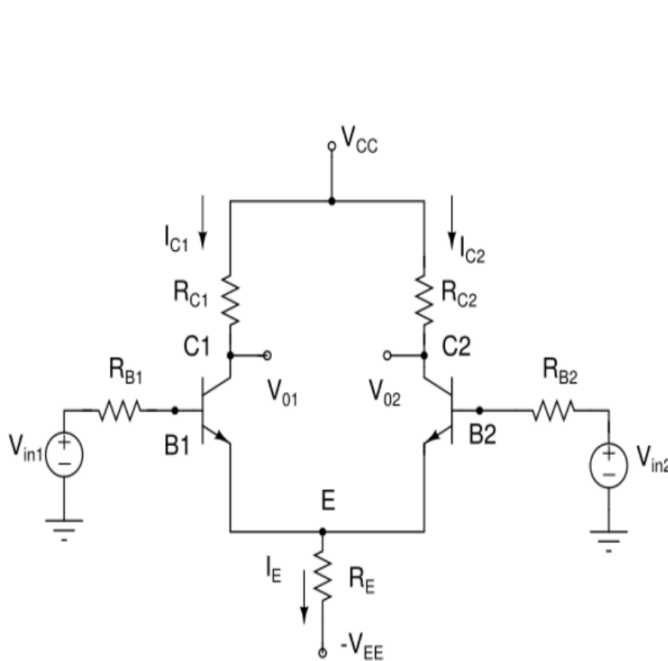

Assuming Active Mode,
Neglect I_B

$$\Rightarrow I_E = \frac{12 - 0.7}{20k} = 0.565 \text{ mA}$$

$$2R_E = 20k \quad I_{E_{\text{Diff}}} = 2 \times I_E = 1.13 \text{ mA}$$

By symmetry,

$$I_{C1} = I_{C2} = I_{E_{\text{Diff}}} \times \frac{1}{2} = 0.565 \text{ mA}$$

$$V_{01} = V_{02} = 12 - 6.8k \times 0.565 \text{ mA} = 8.17 \text{ V}$$

19D070070 | Mayur Ware

*BJT Differential Pair Circuit

.model bc547a NPN BF=400 NE=1.3 ISE=10.3F IKF=50M IS=10F VAF=80 ikr=12m

+ BR=9.5 NC=2 VAR=10 RB=280 RE=1 RC=40 VJE=.48 tr=.3u tf=.5n

+cje=12p vje=.48 mje=.5 cjc=6p vjc=.7 mjc=.33 isc=47p kf=2f

*BJT

Q1 C1 B1 E bc547a

Q2 C2 B2 E bc547a

*Voltage Sources

Vcc CC GND 12

V1 CC 1 dc 0

V2 CC 2 dc 0

Vee GND EE 12

*Resistors

Rc1 1 C1 6.8k

Rc2 2 C2 6.8k

Re E EE 10k

Rb1 B1 GND 1k

Rb2 B2 GND 1k

*Control Commands

.op

.control

run

set color0 = white

set color1 = black

set color2 = blue

set color3 = red

set xbrushwidth = 2

print -i(Vee) i(V1) i(V2) V(E) V(C1) V(C2)

.endc

.end

Simulation Results (Operating Point) :

-i(v1) = 1.135562e-03

i(v2) = 5.645243e-04

v(c1) = 8.161234e+00

i(v1) = 5.645243e-04

v(e) = -6.44385e-01

v(c2) = 8.161234e+00

Learning :

Equal I_{C1} and I_{C2} , V_{C1} and V_{C2} due to circuit symmetry

Differential Amplifier

```


19D070070 | Mayur Ware
*BJT Differential Pair VTC Circuit
V 3 GND sin(0 10m 1k 0 0)
*Control Commands
.tran 0.1m 2m
.control
run
meas tran a pp V(C1)
meas tran b pp V(3)
print a/b
plot V(3) V(C1) V(C2)
.endc
.end

```

$a = 1.196783e+00$

$b = 1.993003e-02$

Gain = $a/b = 6.004923e+01$

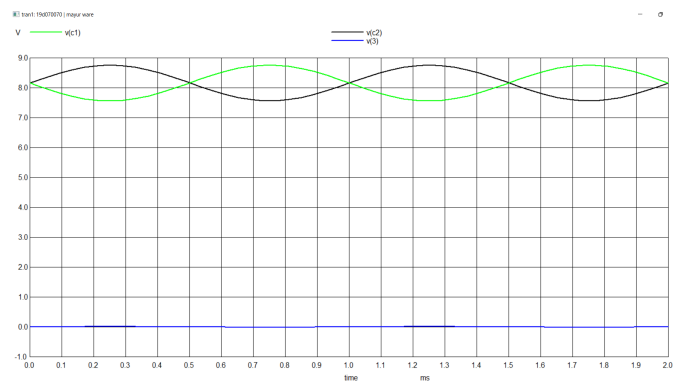


Large-Signal Characteristics (Voltage-Transfer Characteristics - VTC)

```


19D070070 | Mayur Ware
*BJT Differential Pair VTC Circuit
*Control Commands
.dc V3 -1 1 0.01
.control
run
plot V(C1) vs V(3)
plot V(C2) vs V(3)
.endc
.end

```

Plots :

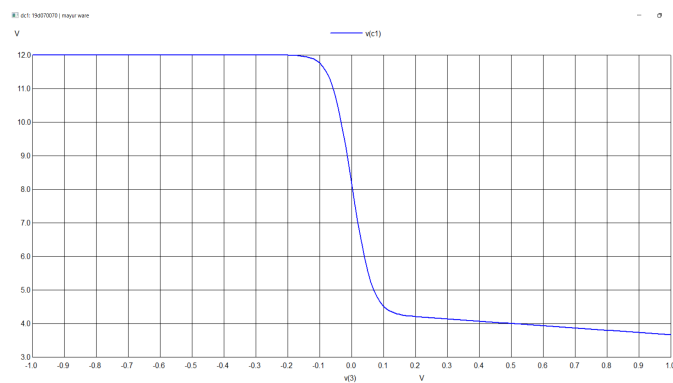

V_{C1} vs V_{in1}

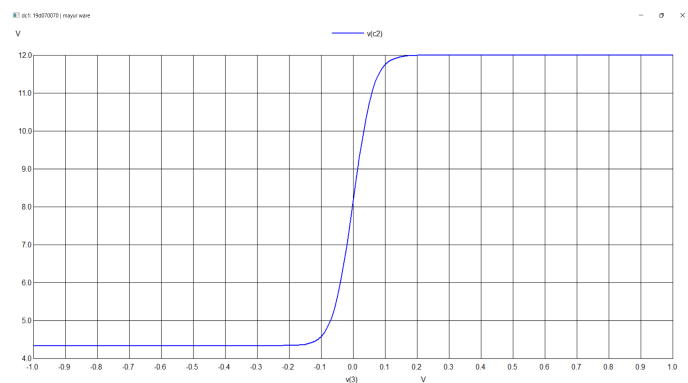

V_{C2} vs V_{in1}

Observations :

V_{C1} decreases as V_{in1} goes from it's negative peak to it's positive peak

V_{C2} increases as V_{in1} goes from it's negative peak to it's positive peak