

# Expt 6 – Opamp Amplifiers

EE 230 Analog Circuits Lab

Joseph John

2021-22/I

# Summary

- Part A - Intro to General Purpose Opamps and LM 741
- Part B – Inverting Amplifier Configuration
- Part C – Non-inverting Amplifier Configuration
- Part D – Single-Opamp Difference Amplifier

# Part A - Intro to General Purpose Opamps and LM 741


DC Open-loop gain : $2 \times 10^5$ V/V
Open-loop input resistance: 2 M $\Omega$
Slew rate : 0.5 V/ $\mu$ s

Open-loop cut-off frequency : 5 Hz
Open-loop Output resistance : 75 $\Omega$
CMRR ( $= A_d/A_{cm}$ ) : 90 dB

Typical Parameters of 741 General Purpose Opamp


## Part B – Inverting Amplifier Configuration
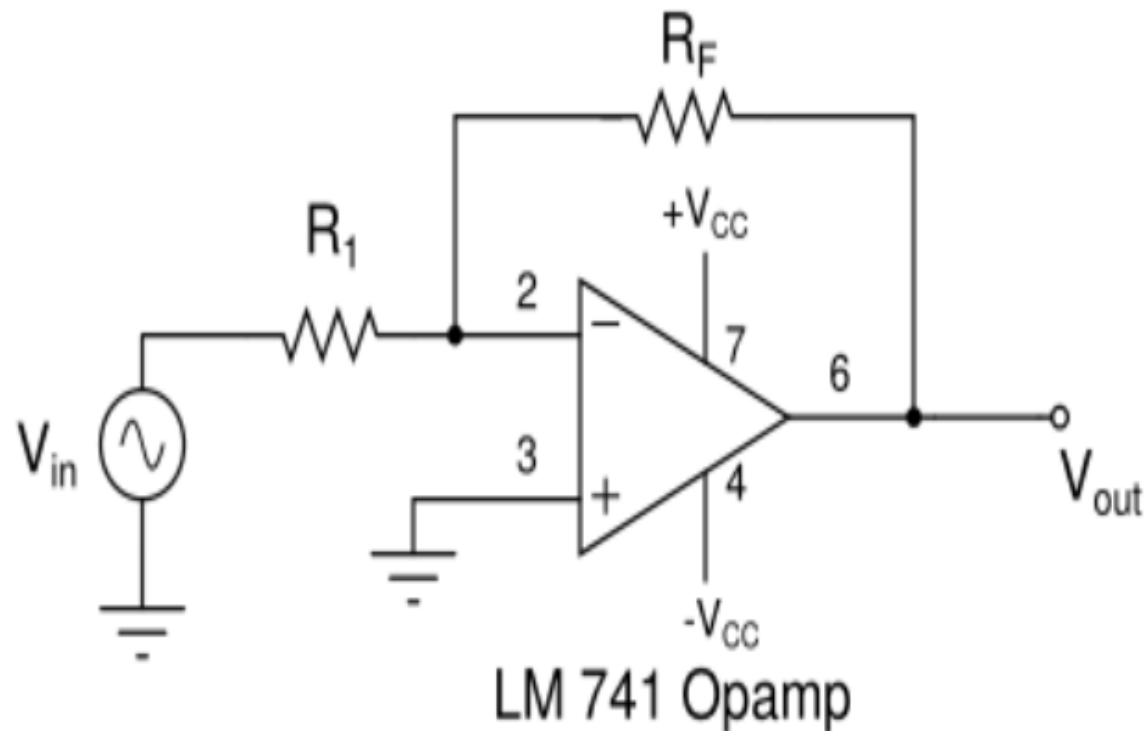
## Part B – Inverting Amplifier Configuration



- Major features (as a Voltage Amplifiers)
- $R_{in} = R_1$
- $R_{out}$  very low
- Not a good Voltage Amp (due to lower  $R_{in}$ )
- Limited Voltage gain due to limitation on  $R_1$
- Phase inversion between  $V_{in}$  and  $V_{out}$

# A Special Inverting Amplifier

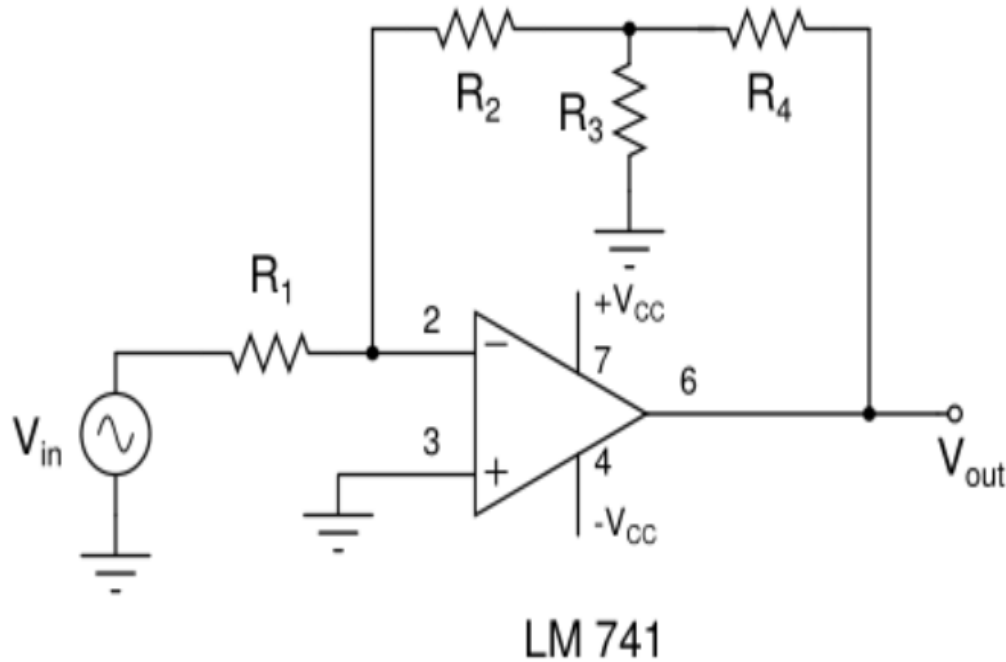


$$\frac{V_{out}}{V_{in}} = \frac{-R_2}{R_1} \left( 1 + \frac{R_4}{R_2} + \frac{R_4}{R_3} \right)$$

- Expt 6 circuit values:
- $R_1 = R_2 = R_4 = 1 \text{ M}\Omega$ ,  $R_3 = 120 \text{ k}\Omega$
- $R_1 = R_2 = R_4 = 1 \text{ M}\Omega$ 
  - $R_1$  chosen high to take care of the  $R_{in}$  issue of the standard inverting amplifier
- High voltage gain possible
  - Expt 6:  $|A_v| = 10.3$
- A good choice as a voltage amp

# Opamp based Weighted Summer


# Resistive Summer Circuit

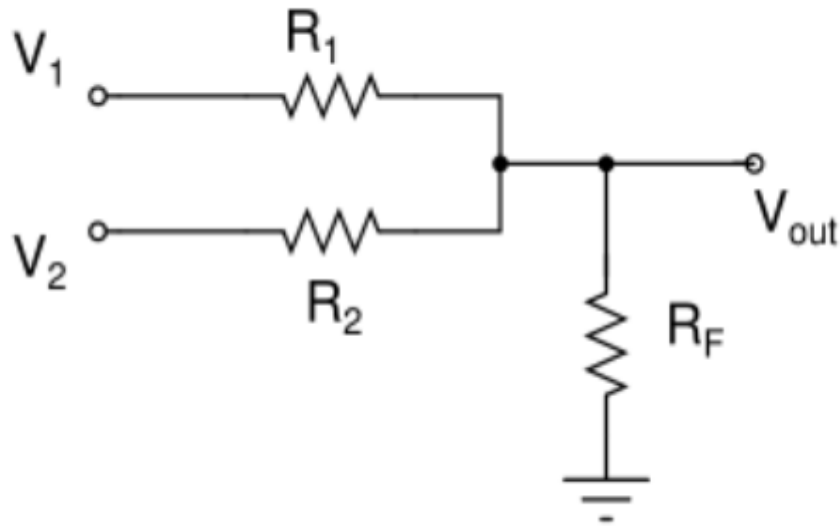



- Problems
- Weights are coupled
  - Contribution of  $V_1$  affected by weightage of  $V_2$
- Quite cumbersome to design
  - For more than 2 inputs
- No possibility of gain



# Opamp based Weighted Summer

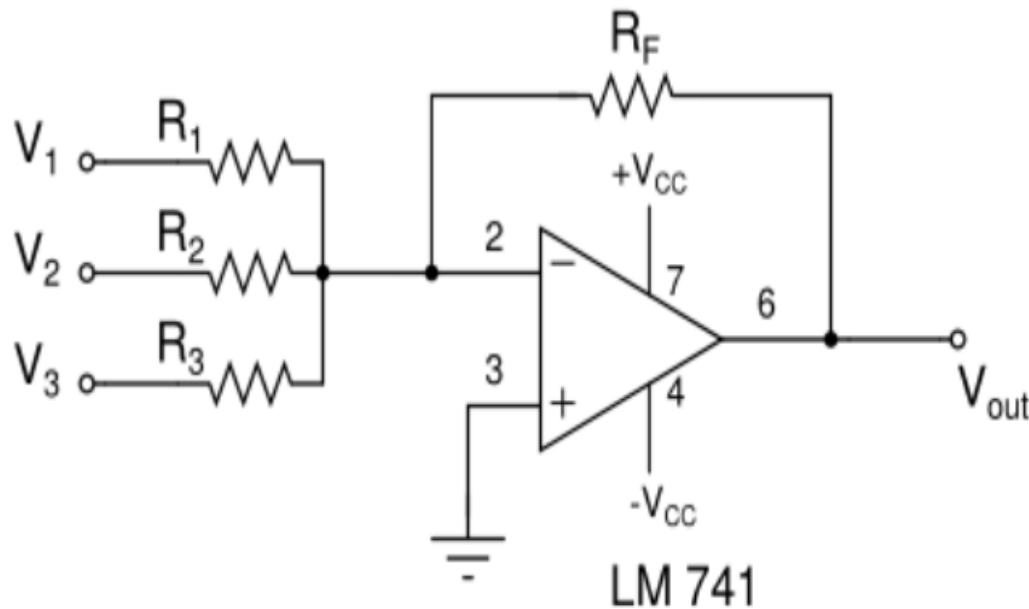

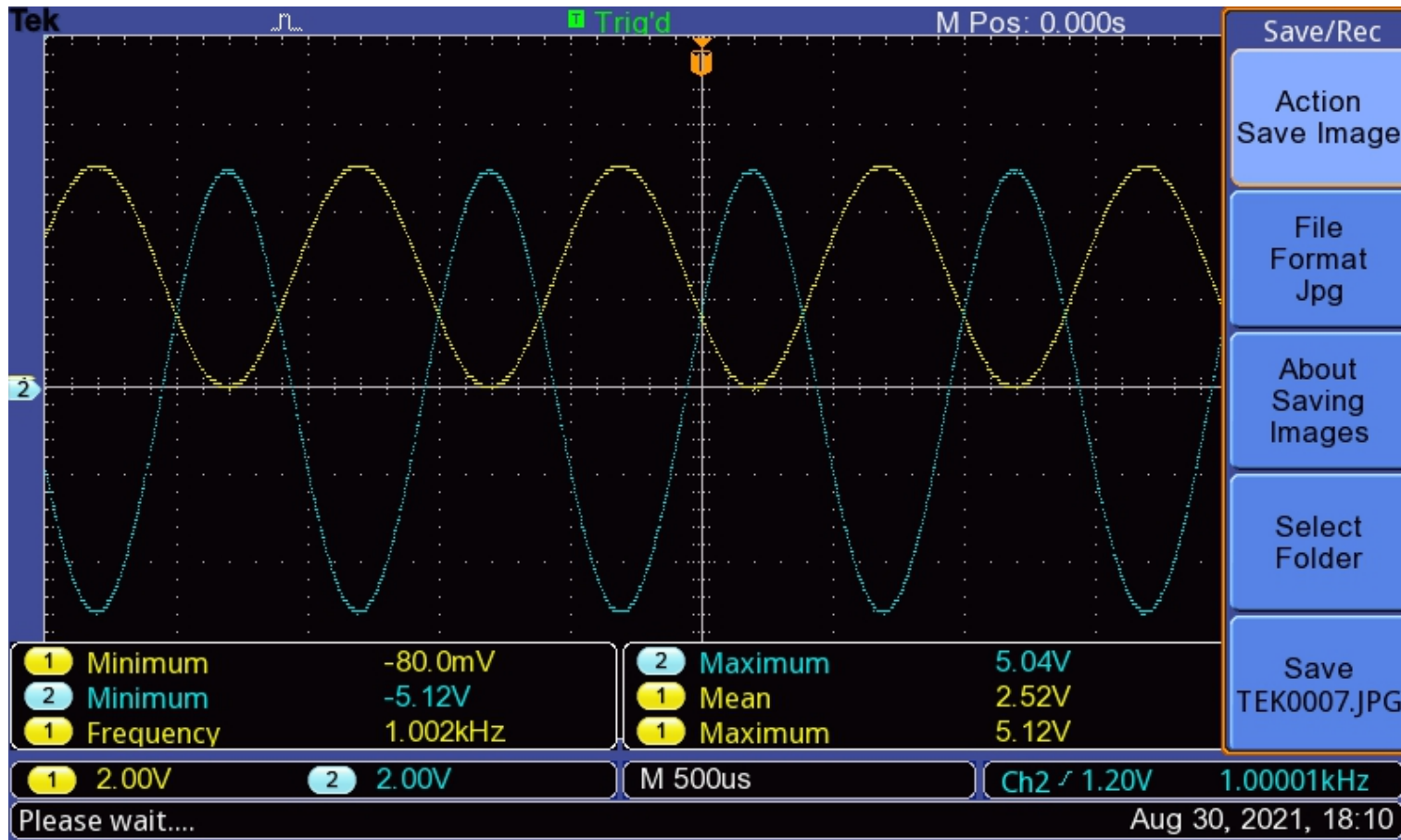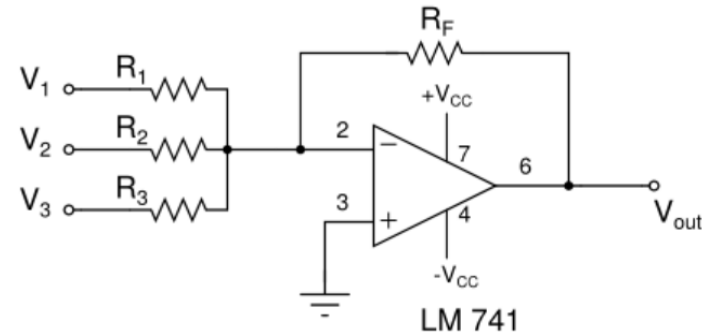
- Problems
- Weights are independent
  - Contribution of  $V_1$  depends only on its weightage
- Very easy to design
  - For any number of inputs
- Voltage gain possible



- Experiment
- $R_1 = R_2 = 6.8 \text{ k}\Omega$ ,
- $R_F = (6.8 \text{ k}\Omega + 6.8 \text{ k}\Omega)$
- $V_1$  = a unipolar sinewave (Max 5 V and Min 0 V);
- $V_2 = -2.5 \text{ V dc}$
- $V_{out} : 5 \sin \omega t$



## Part C – Non-inverting Amplifier

# Non-inverting Amplifier

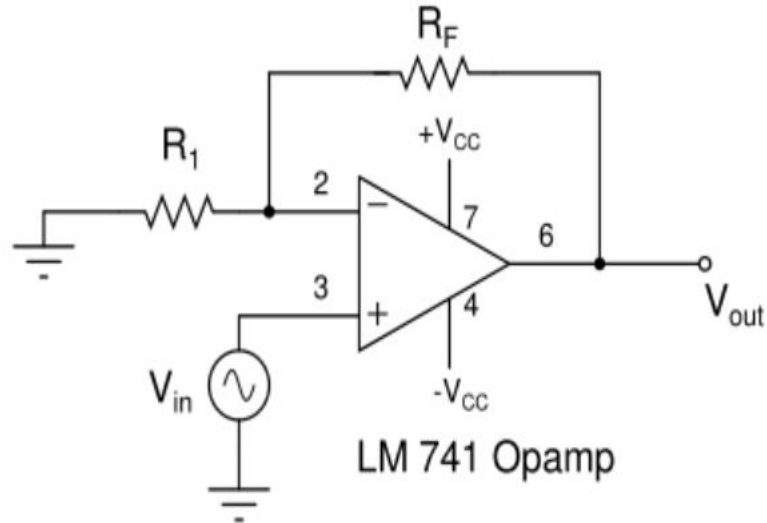

- Major features (as a Voltage Amplifiers)
- $R_{in}$  very high
- $R_{out}$  very low
- Choice of  $R_1$  and  $R_F$ 
  - Based on input bias current
- Excellent voltage amplifier

# Closed-loop Gain, $A_f$

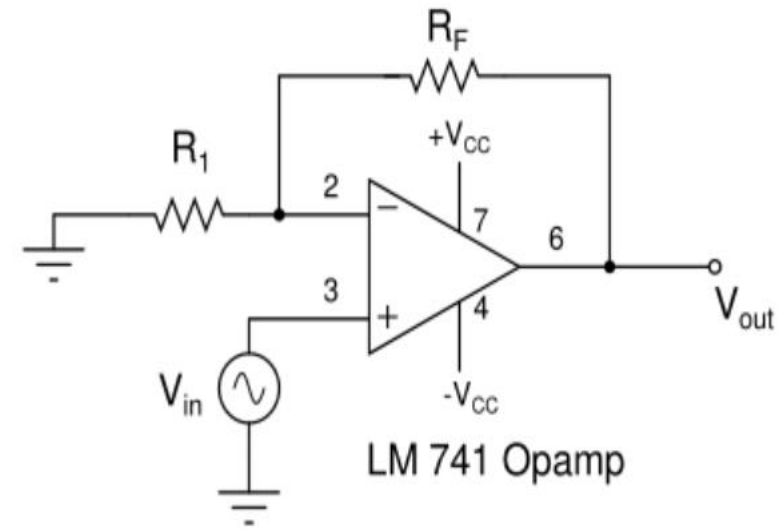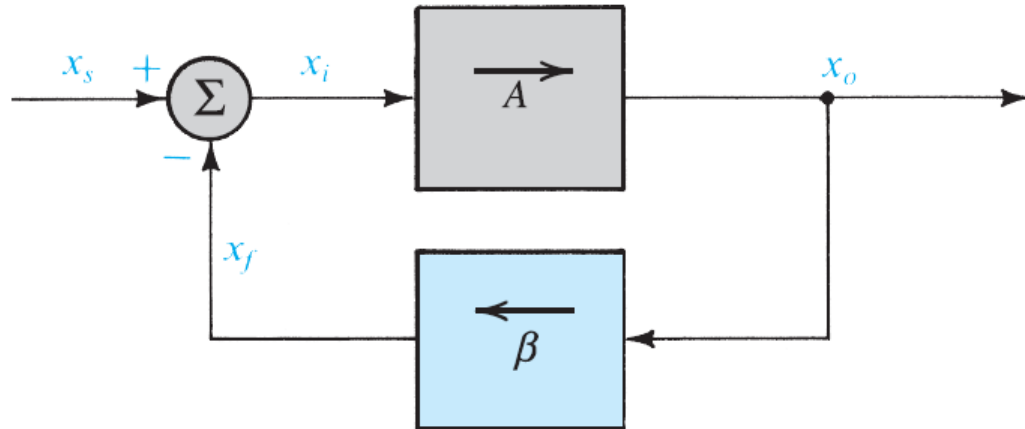


$$A_f = \frac{A}{1 + A\beta}$$

- $A_f$  of an Non-inv amp


## Part D – Difference Amplifier

# Difference Amplifier

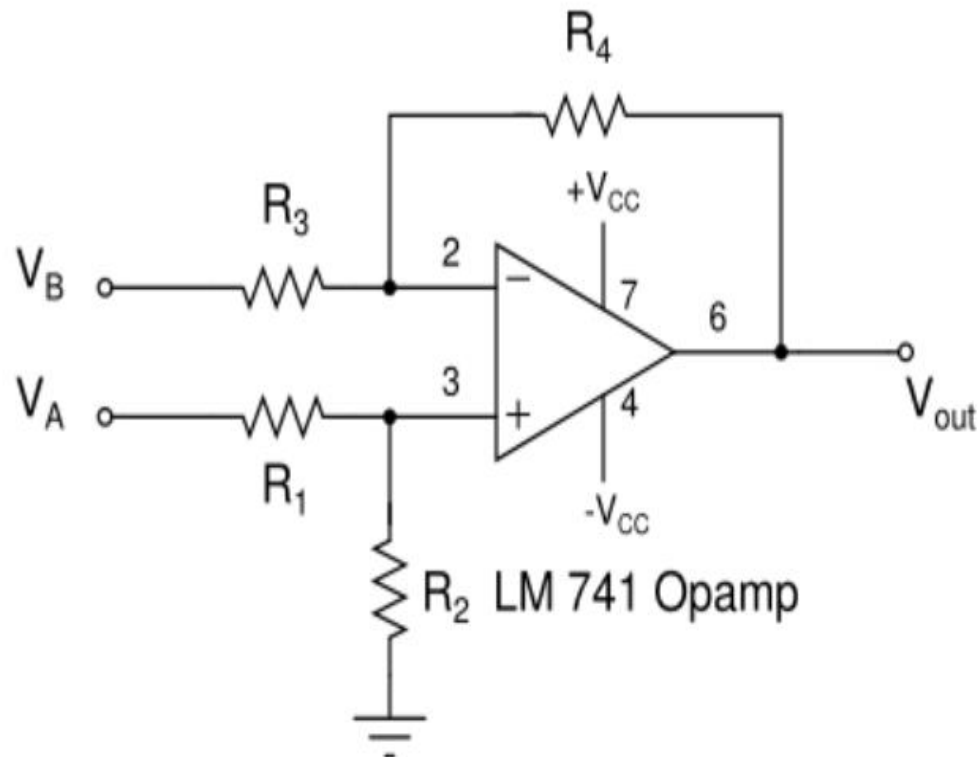



- Major Features
- Uses differential input signals
  - Inv and Non-inv used single-ended inputs
- Works as a difference amp if  $(R_4/R_3 = R_2/R_1)$
- $A_d = R_4/R_3$
- $A_{cm} = 0$  ideally
- $CMRR = A_d/A_{cm}$  (ideally  $\infty$ )
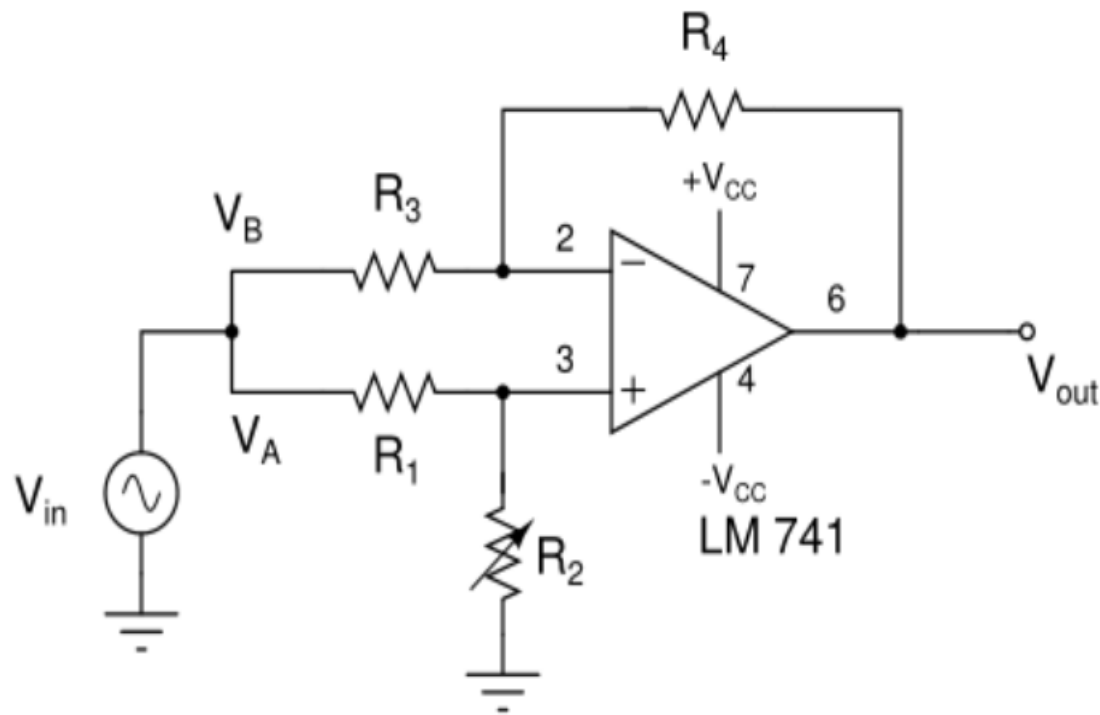
# Measurement of Common-mode Gain $A_{cm}$



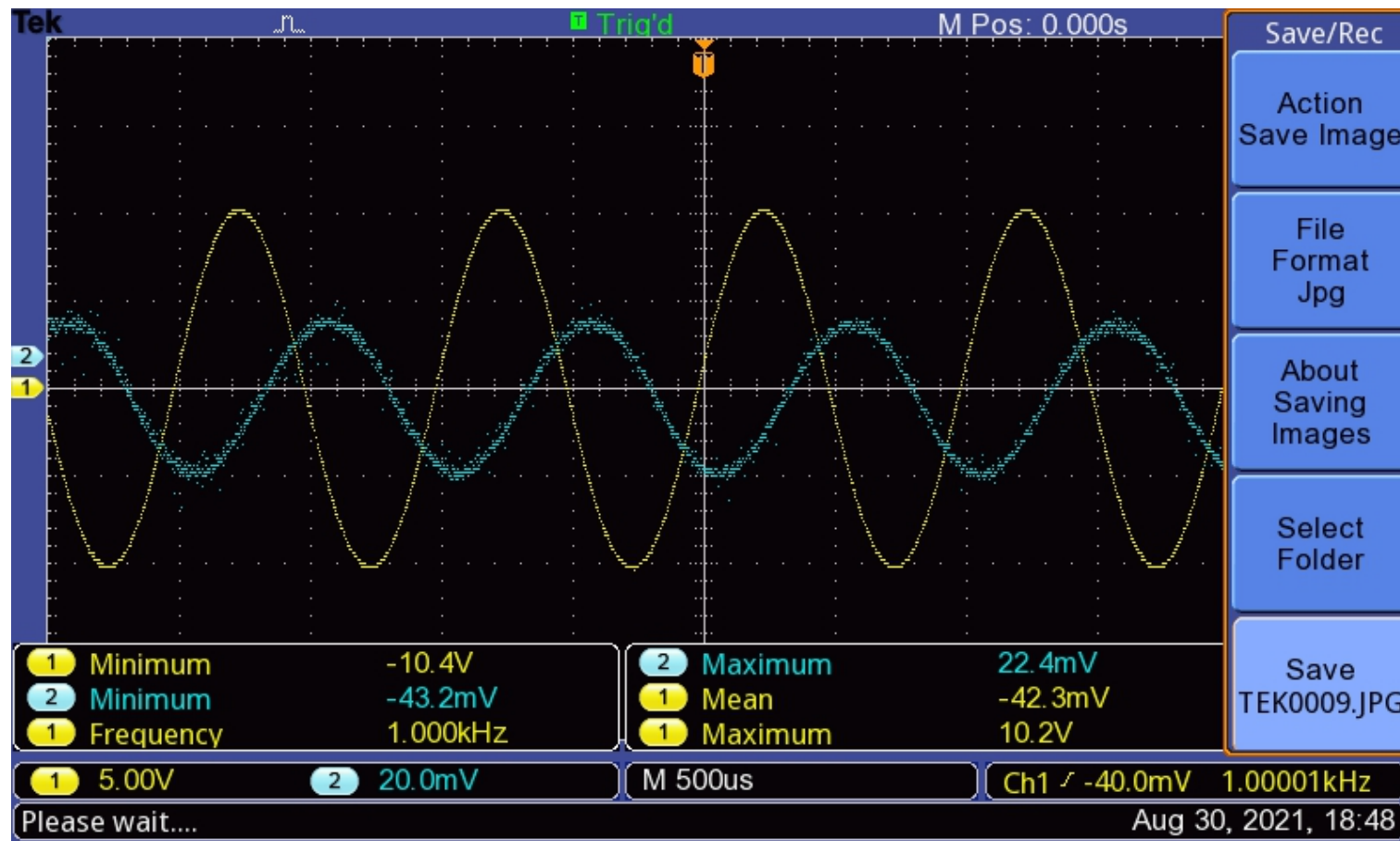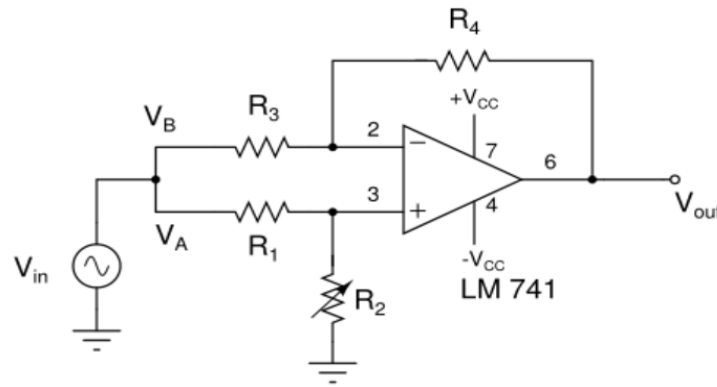- $A_{cm}$  is a very small quantity ( $10^{-3}$  or  $10^{-4}$  typ)
- Difficult to measure
- Need to do a careful measurement to minimize measurement errors
- $A_{cm} = V_{out}/V_{in}$






## Procedure


- $V_A = V_B = V_{in}$
- $V_{in} = 10 \sin \omega t$  (1 kHz)
- Adjust  $R_2$  (to satisfy the condition,  $R_2/R_1 = R_4/R_3$ )
- Adjust  $R_2$  to get the minimum possible  $V_{out}$
- $A_{cm} = V_{out}/V_{in}$
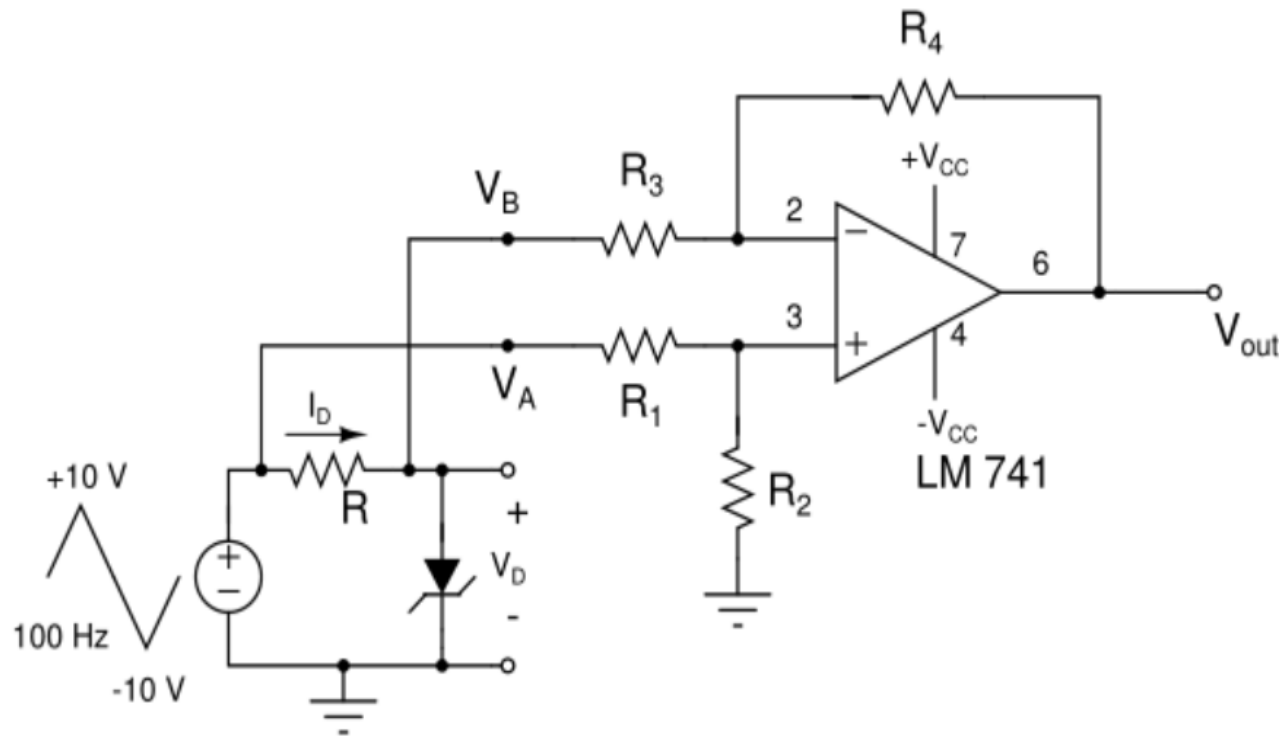
# I-V Characteristics of a Zener and other Diodes




- Very useful circuit
- $R_1 = R_2 = R_3 = R_4 = 10 \text{ k}\Omega$ ,
- $R = 1 \text{ k}\Omega$ .
- $V_{out} = (V_A - V_B) = I_D \cdot R$
- Magnitude of  $V_{out}$  (in volts) will be the same as magnitude of  $I_D$  (in mA)
- Choice of  $V_{in}$ 
  - Must be a triangular waveform
  - Must be low frequency (100 Hz to 1 kHz)

# Application 1 – I-V Characteristics of a Zener Diodes

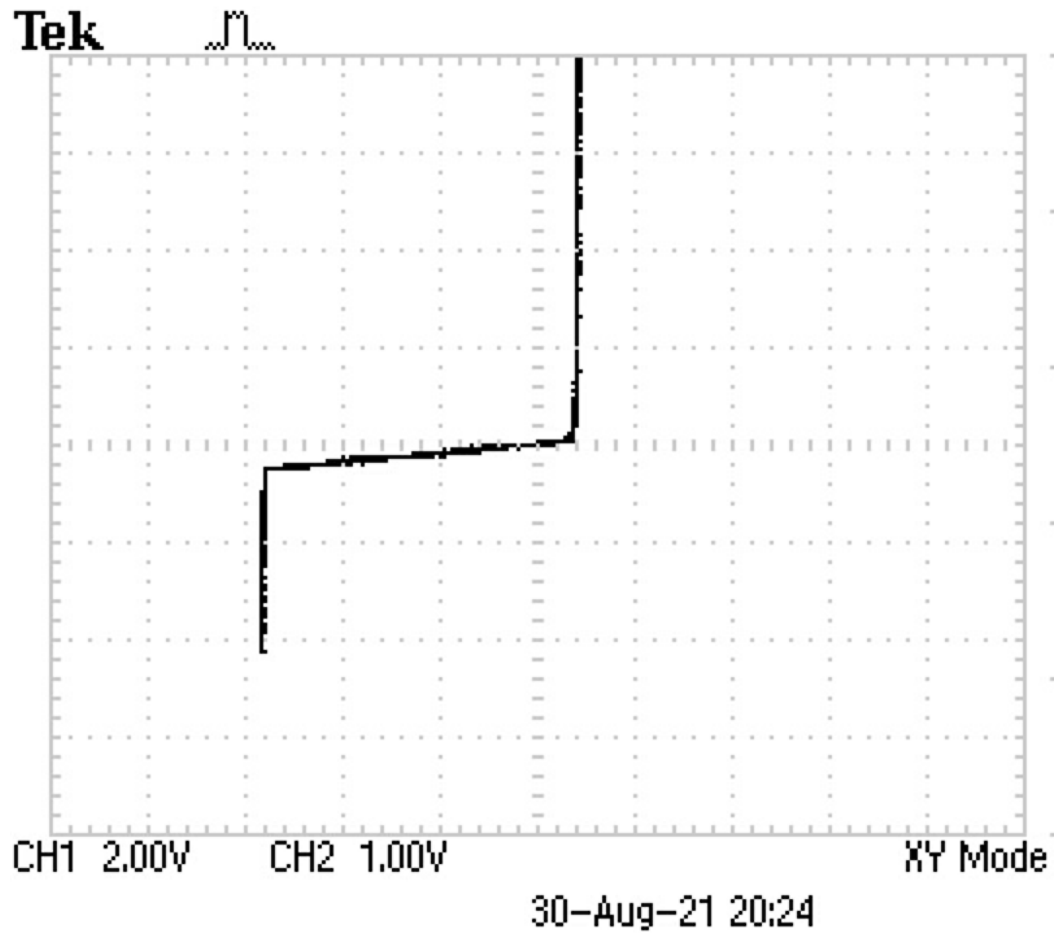


Zener 5.6 V, 1 kHz

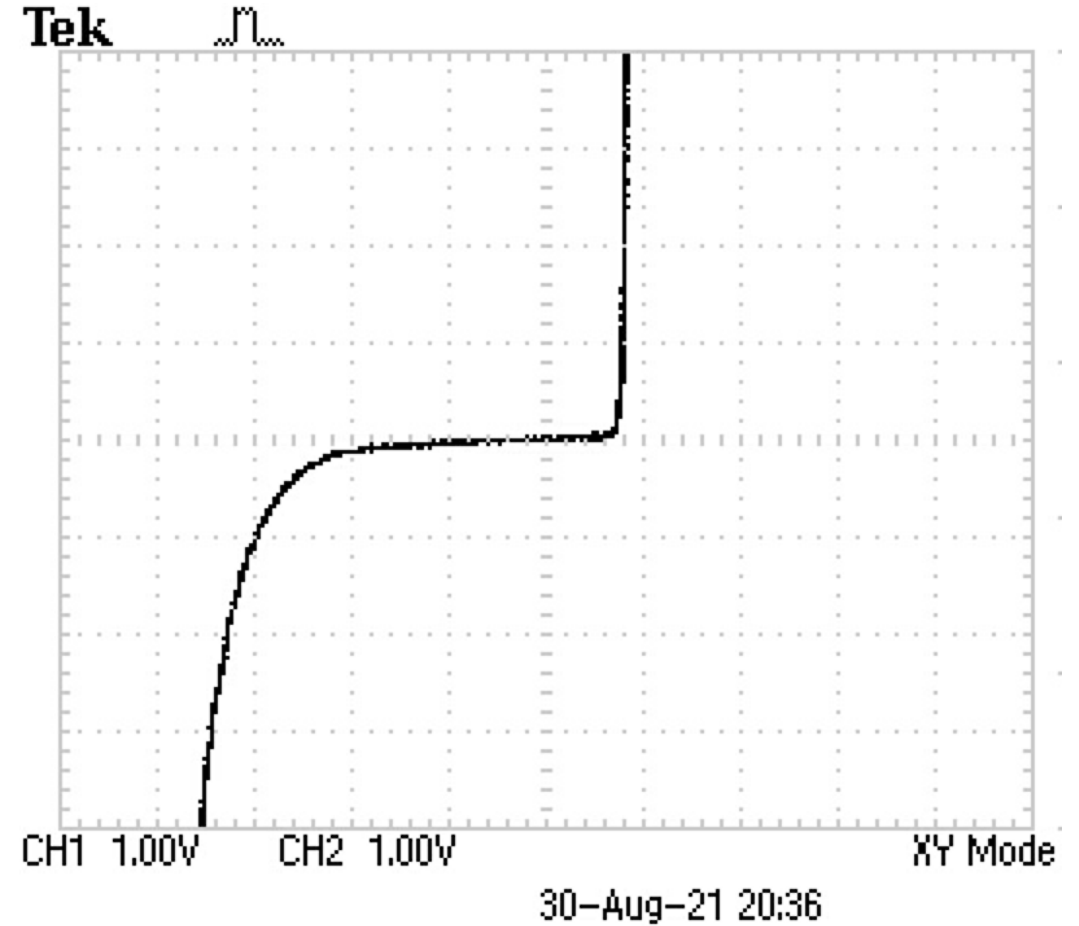


Zener 3.6 V, 1 kHz

# Application 2 – I-V Characteristics of Silicon and Ge Diodes

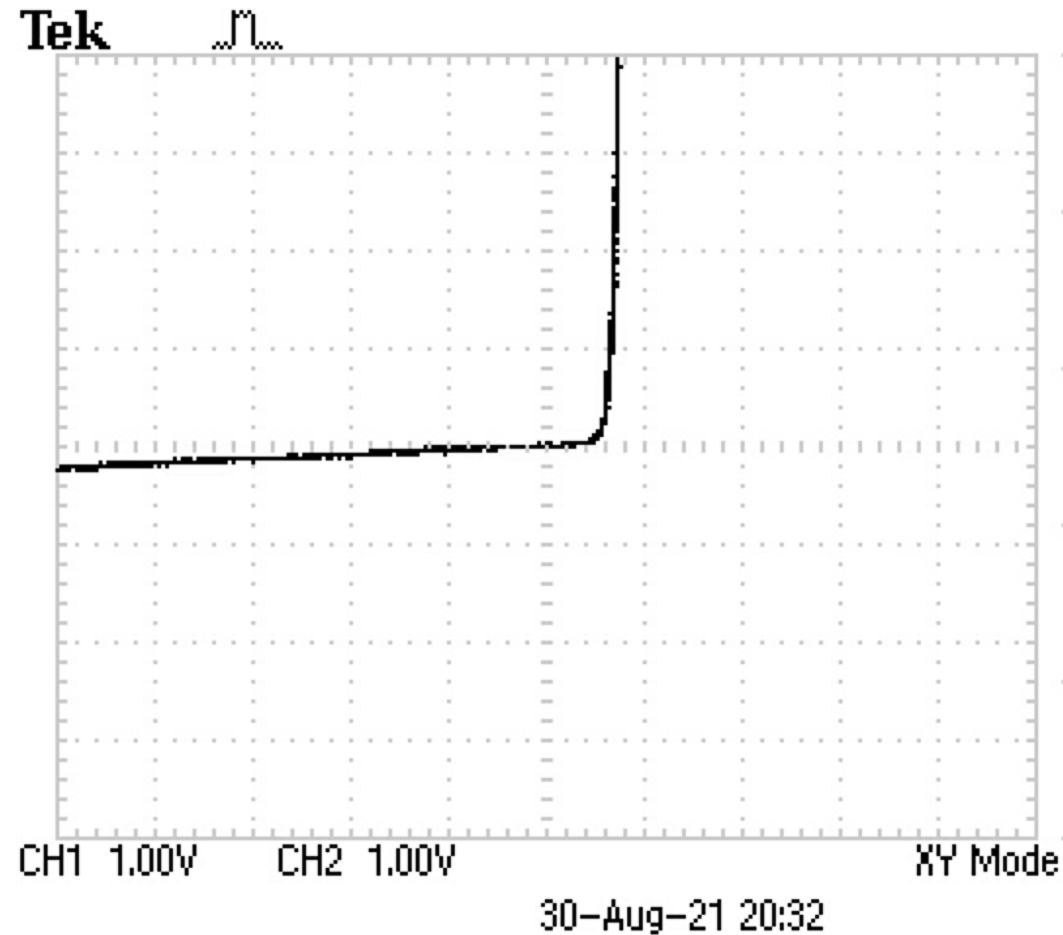


IN914 – Signal diode, 1 kHz

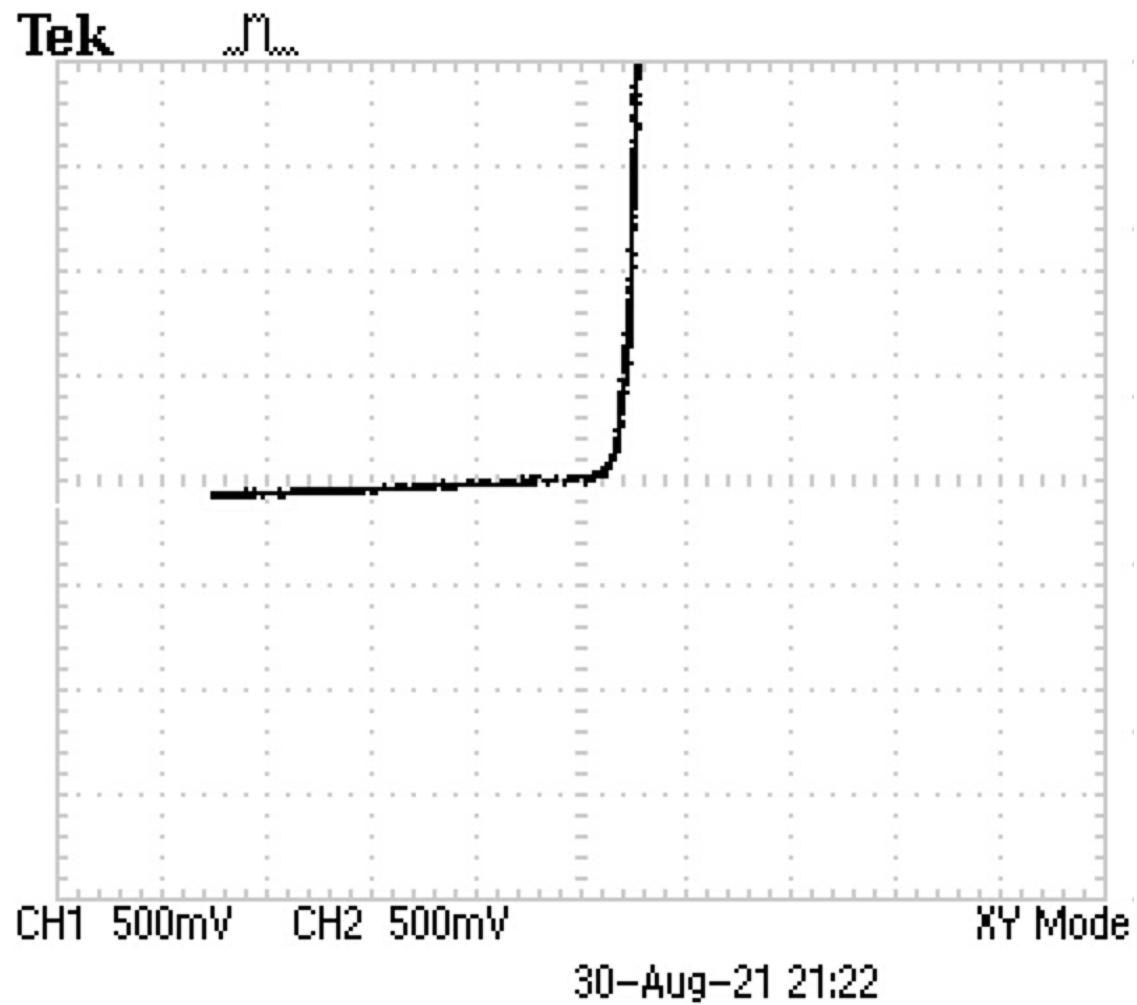



Ge diode, 100 Hz

10 kHz

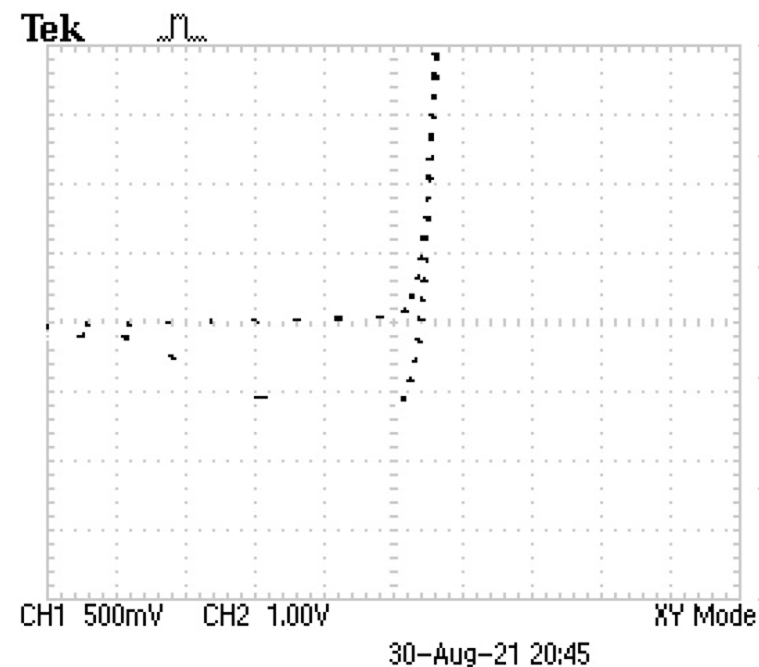


1 kHz

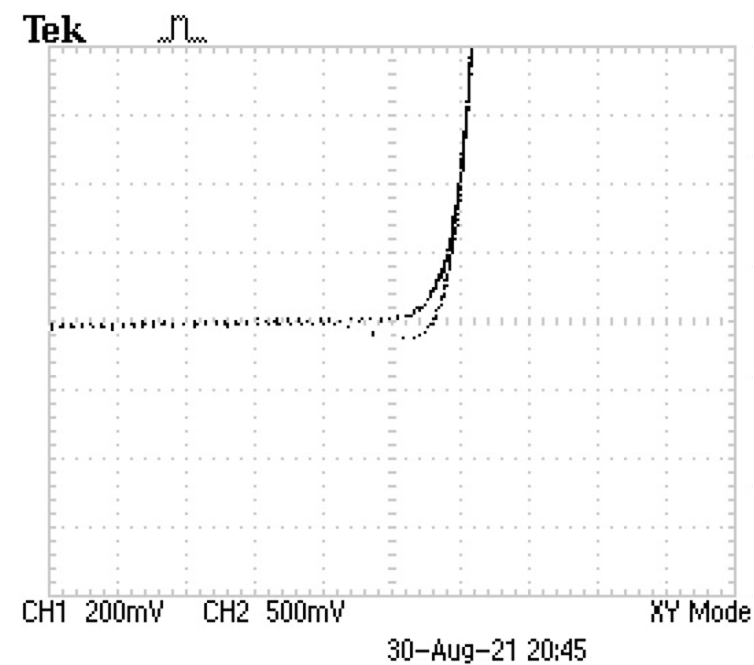

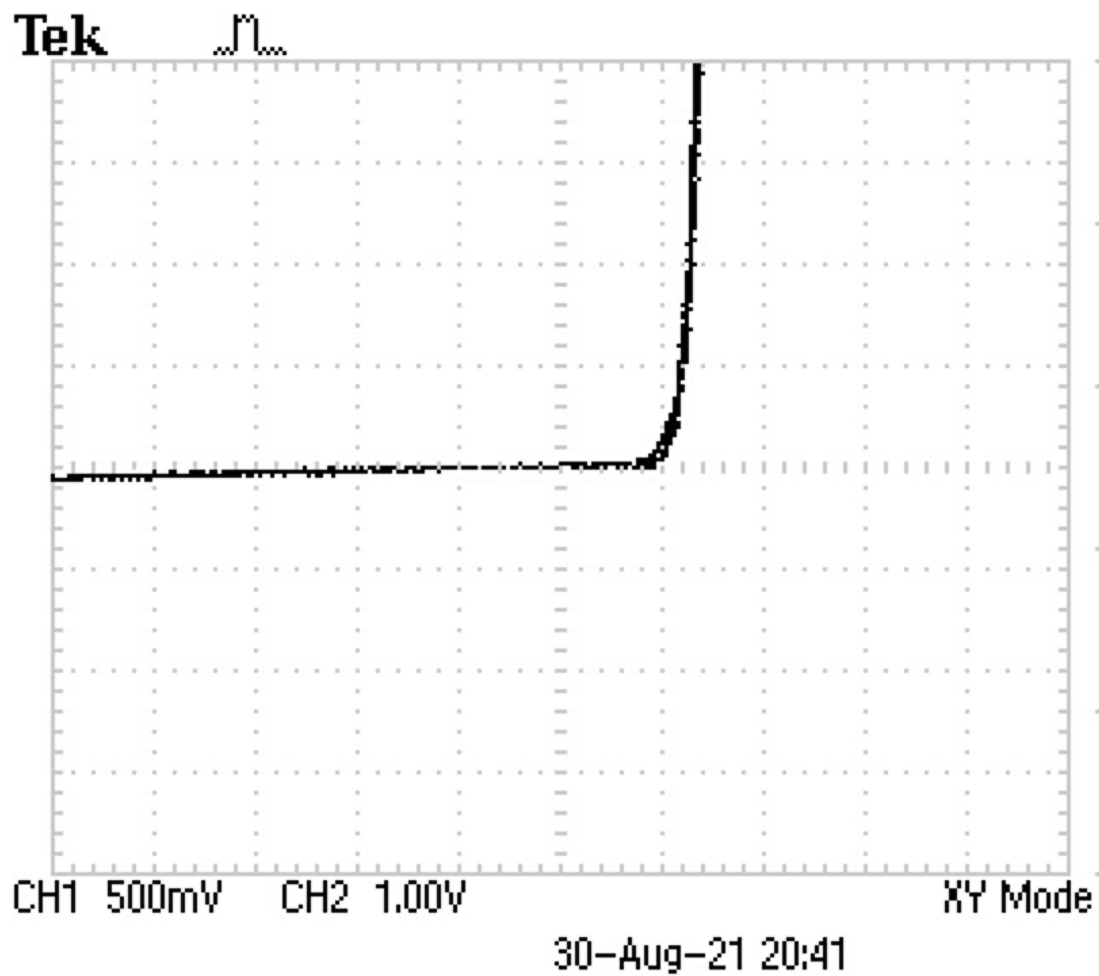


IN4007 1 kHz

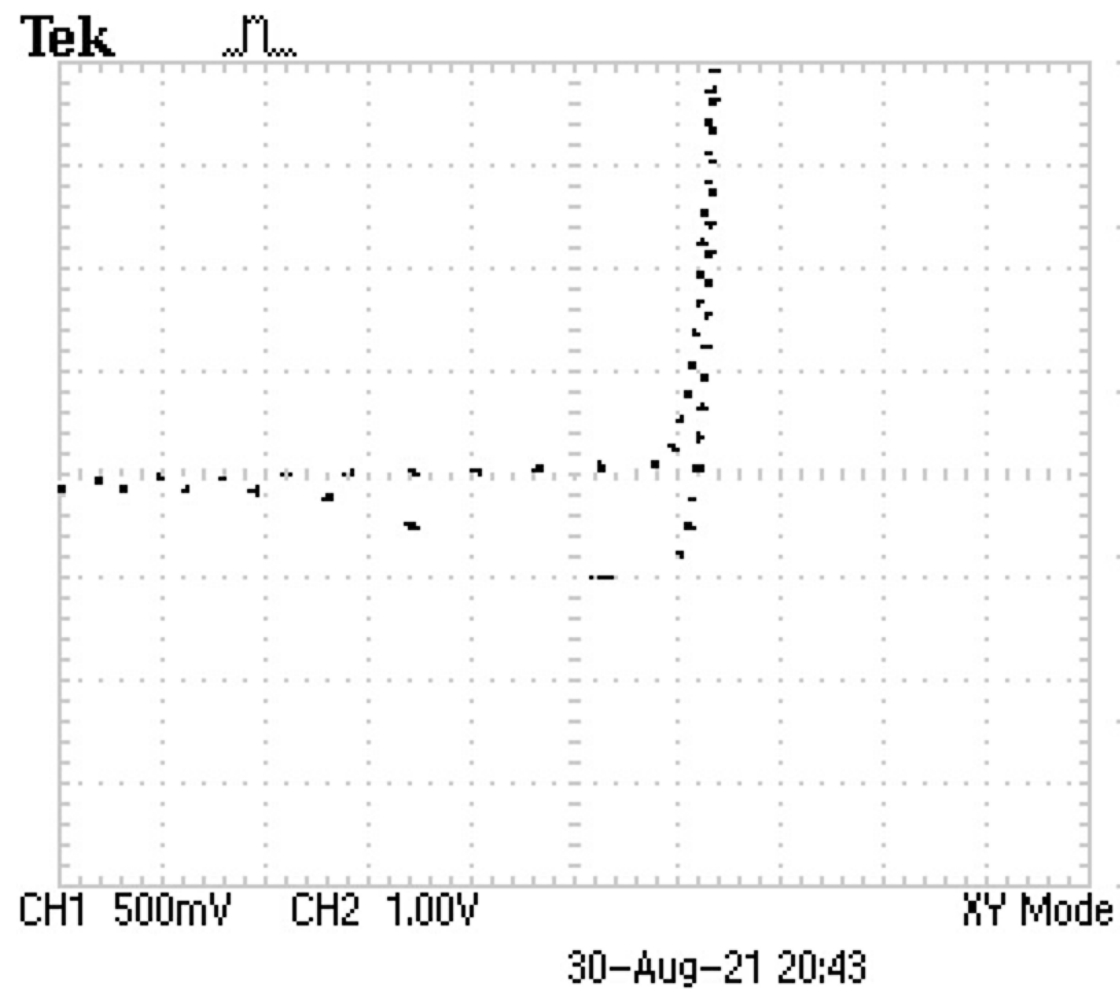


IN4007 10 kHz
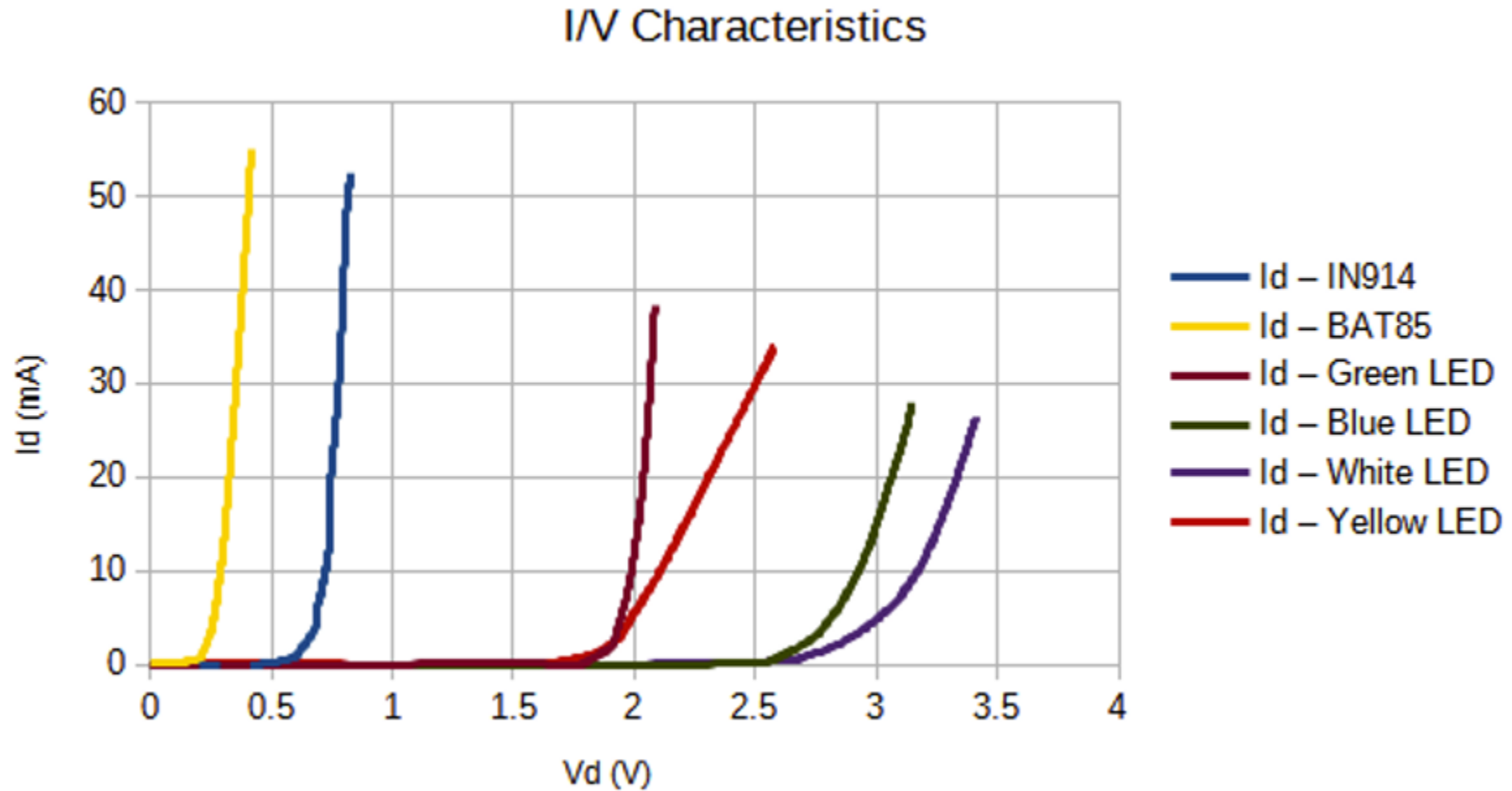
## Application 3 – I-V Characteristics of LEDs




Measured in WEL Lab using a newly developed Data Acq Board
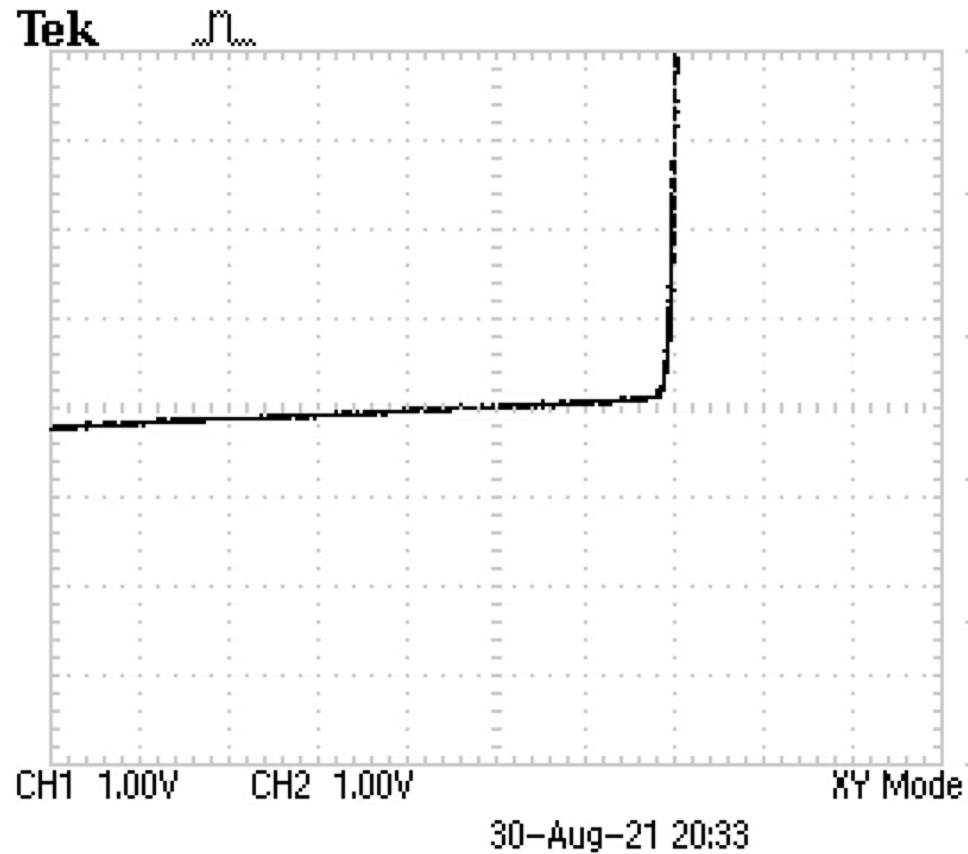
# I-V Characteristics of LEDs – measured using our Difference Amplifier




Green LED (1.8 V), 1 kHz

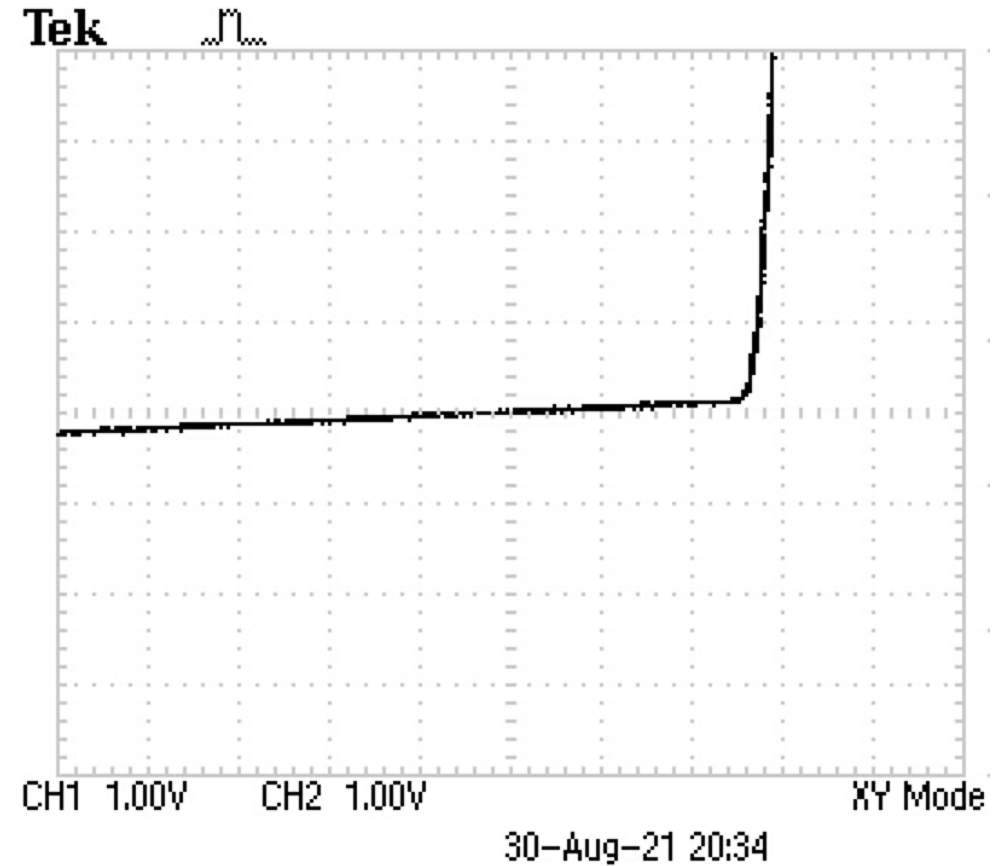


Blue LED (2.6 V), 1 kHz



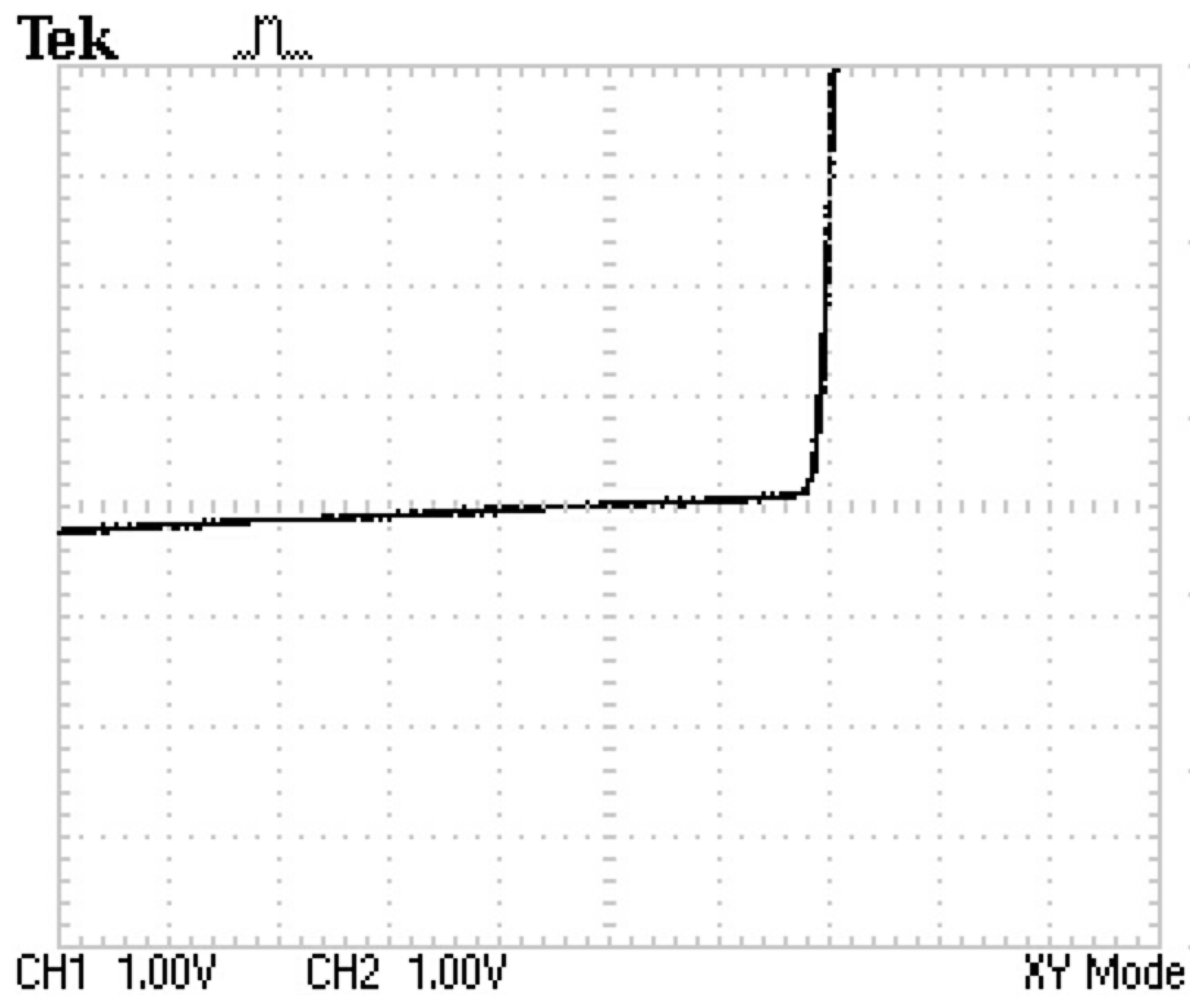


30-Aug-21 20:38

White LED (1.8 V), 1 kHz

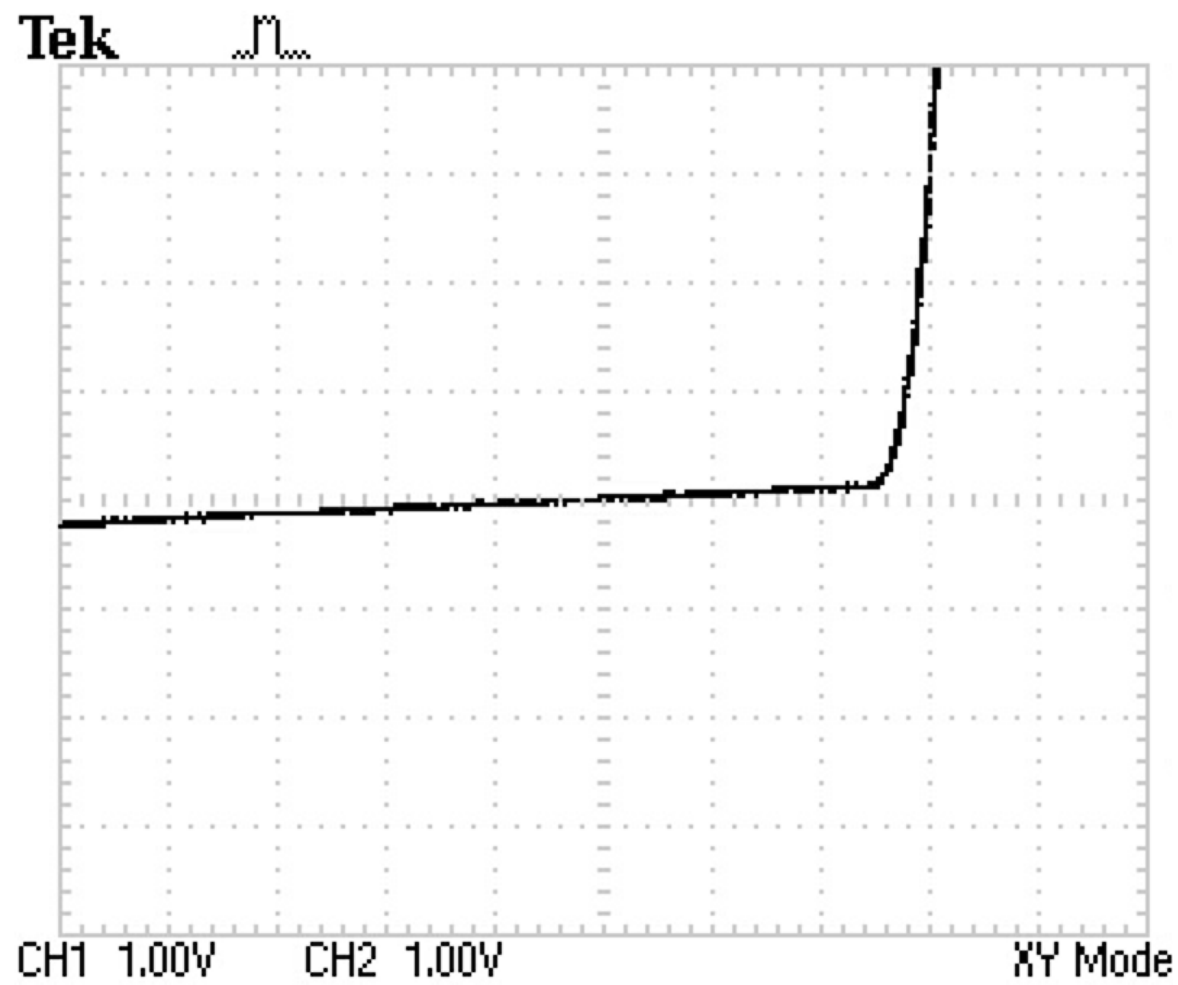


30-Aug-21 20:39

White LED (2.6 V), 1 kHz

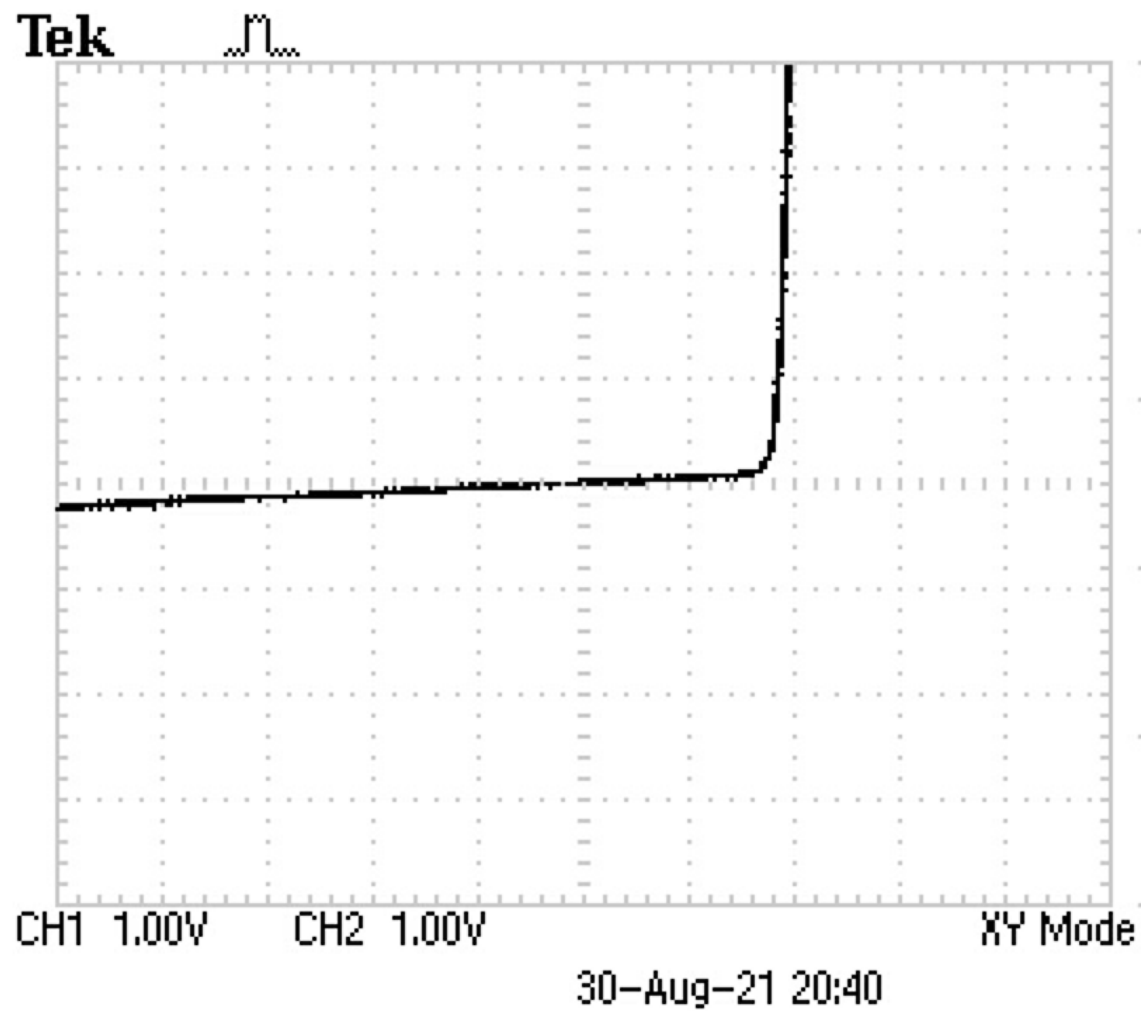


Red LED (1.8 V), 1 kHz

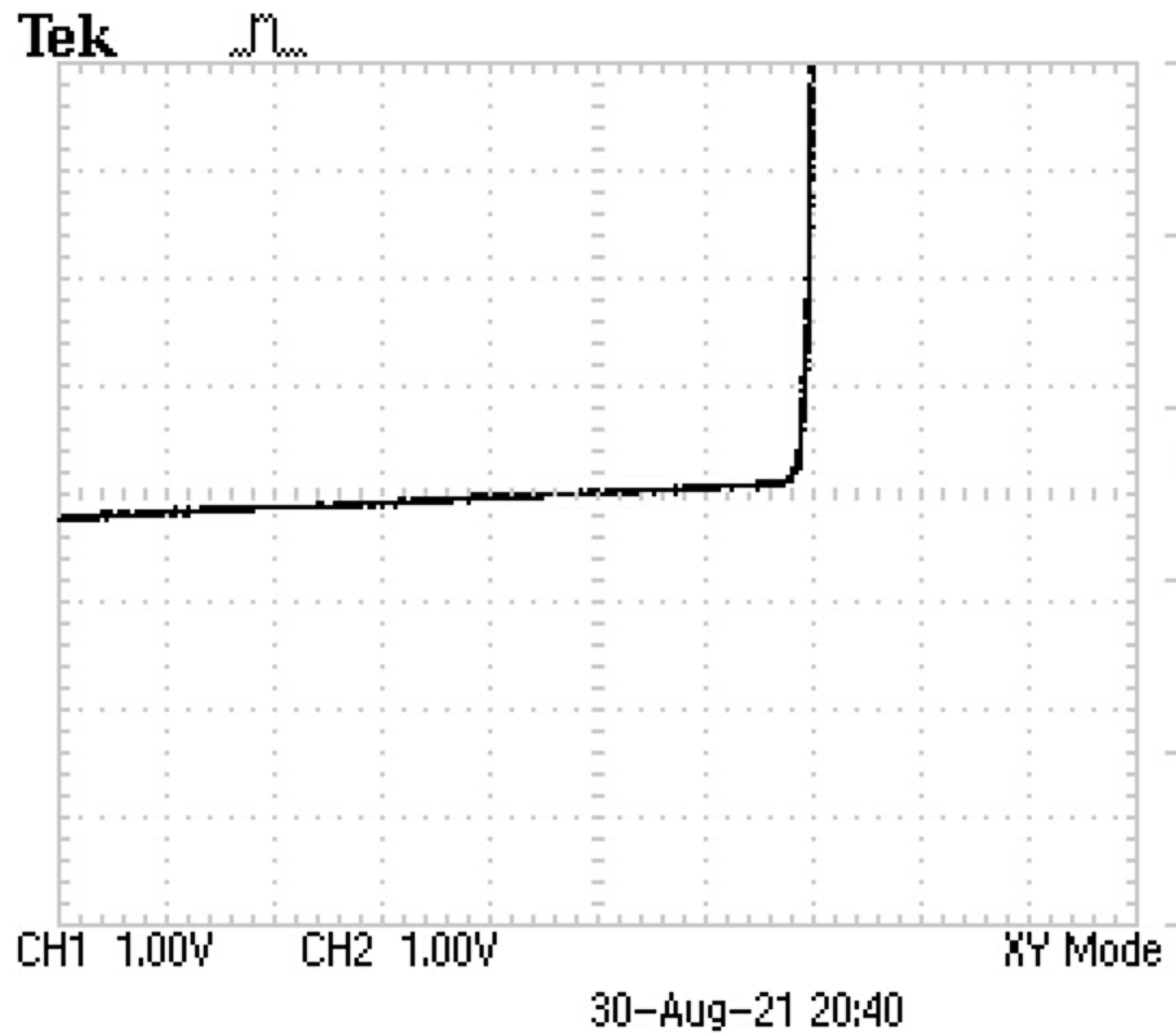

Yellow LED (1.9 V), 1 kHz

# Interfacing LM35
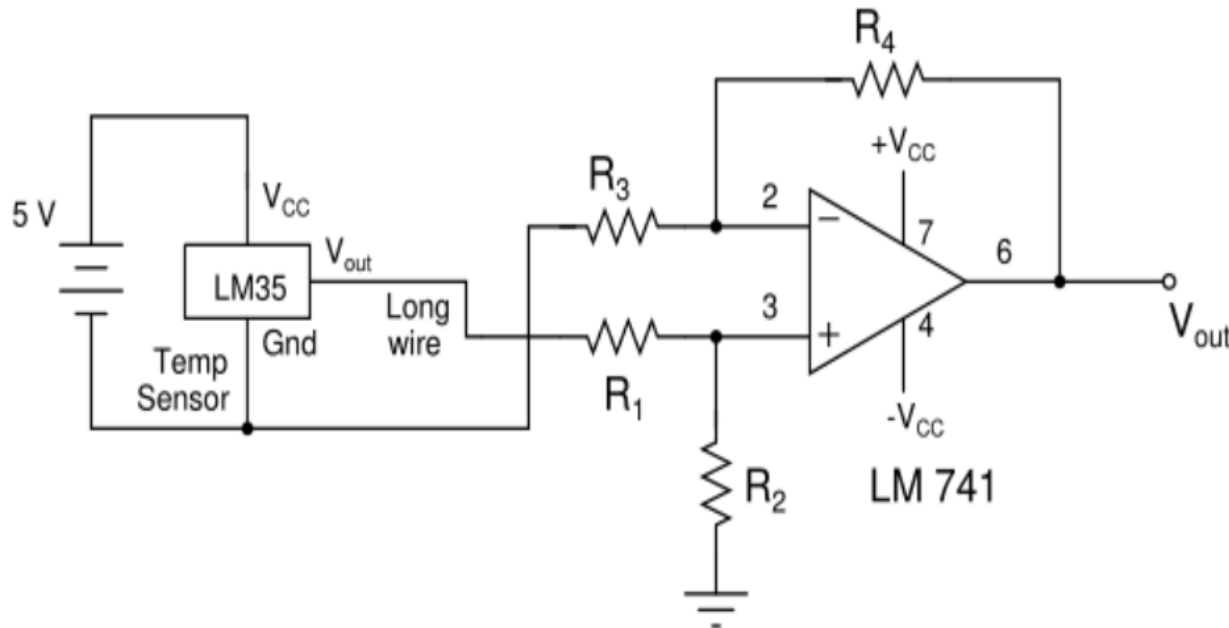
# Interfacing Circuit 3: Difference Amplifier (with $A_d = 10$ )



- Problem of noise
- Difference amplifier preferred
- No conclusive results

# Announcements

- Midsem Exam – Sep 24 (Friday) – 2:00 – 3:15pm (Weightage 18%)
  - Expts 1 to 6
  - SAFE/Codetantra
- No Quiz on Sep 24 Fri
- Quiz 7 and Quiz 8 on Oct 1 Friday

# Quiz instructions

- Mobile Calculators NOT allowed
- No formula sheets
- Video Proctoring – Full view of your workspace