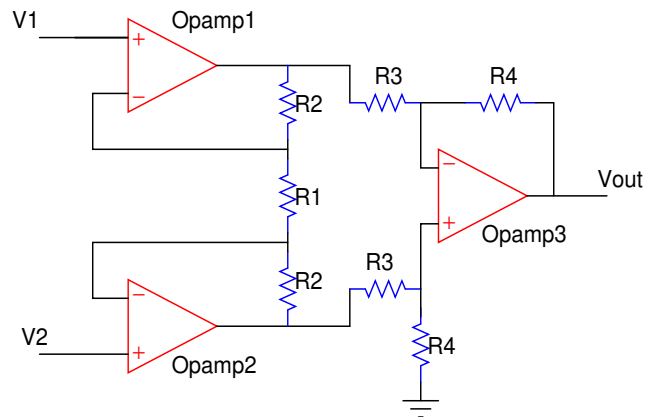


EE230 : Analog Circuits Lab

Mayur Ware | 19D070070, **Section 6**
Experiment 7 : Instrumentation Amplifiers

September 26, 2021

Three-Opamp Instrumentation Amplifier using TL084




The differential voltage gain of the above amplifier,

$$A_d = \frac{V_{out}}{(V_2 - V_1)} = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1} \right)$$

where the second term $[1 + (2R_2/R_1)]$ is the A_d of the first difference amplifier, while (R_4/R_3) is the A_d of the second one.

INA128 Instrumentation Amplifier

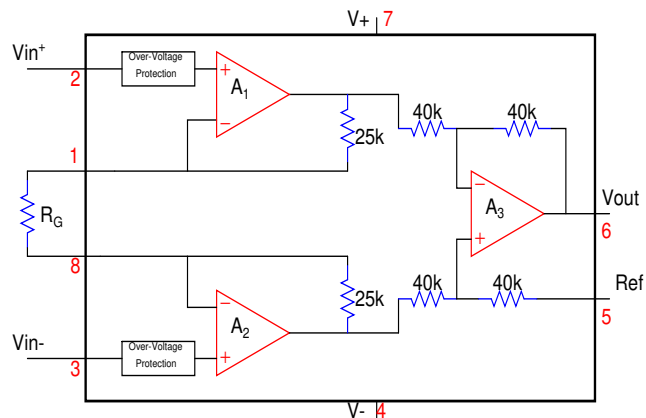

The differential voltage gain of the above amplifier is also,

$$A_d = \frac{V_{out}}{(V_2 - V_1)} = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_G} \right)$$

INA 128 is a low cost, general purpose instrumentation amplifier employing the standard three-Opamp instrumentation amplifier design

Learnings

- 1) INA128 Instrumentation Amplifier has a slight beneficial edge over Three-Opamp Instrumentation Amplifier using TL084 due to its adjustability. One can have more control over the gain in INA128 Instrumentation Amplifier as compared to Three-Opamp Instrumentation Amplifier due to adjustable resistor R_G .
- 2) Over-Voltage Protector in INA128 Instrumentation Amplifier is also its another benefit.
- 3) Three-Opamp Instrumentation Amplifier can be built on the bread board but not INA128 Instrumentation Amplifier.

Answer to the questions

Q1) In Sec 3.2 and 3.3, even under no-load conditions V_{out} was found to be non-zero. Give one or two reasons for this.

Answer :

- 1) V_{out} is non-zero due to the offset voltage even for no load condition.
- 2) There is more offset in the V_{out} in Instrumentation Amplifier using TL084 as compared to INA128 Instrumentation Amplifier because offset voltage in INA128 as compared to TL084.

Q2) Give two or three major advantages of the three-Opamp instrumentation amplifier as compared to the single-Opamp difference amplifier of Experiment 6.

Answer :

- 1) Input resistance (R_{in}) for Three-Opamp Instrumentation Amplifier is ideally infinity which is very high as compared to Single-Opamp Instrumentation Amplifier.
- 2) It is easy to change the Differential Voltage Gain (A_d) in Three-Opamp Instrumentation Amplifier by only changing a single resistor and still having the Common-mode Voltage Gain (A_{cm}) equal to zero.
- 3) For practical purposes, Three-Opamp Instrumentation Amplifier has larger Common Mode Rejection Ratio (CMRR) than Single-Opamp Instrumentation Amplifier.

Q3) Look at the data sheets of TL084 and INA 128. Identify the major differences between these two ICs – i.e. Opamp parameters crucial for difference amplifier applications, such as the Loadcell application discussed in this experiment.

Answer :

- 1) Drift is low for Three-Stage Instrumentation Amplifier.
- 2) Input bias current is low for Three-Stage Instrumentation Amplifier.
- 3) Low offset voltage for Three-Stage Instrumentation Amplifier.
- 4) High Common Mode Rejection Ratio (CMRR) for Three-Stage Instrumentation Amplifier.

Q4) Identify one or two parameters of the INA128 that makes it superior to the TL084 based instrumentation amplifier.

- 1) INA128 has low input bias current and voltage offset as compared to TL084.
- 2) Common Mode Rejection Ratio (CMRR) for INA128 is very high as compared to TL084.

References

- 1) Lecture Slides
- 2) Sedra-Smith
- 3) WEL Resources for NGSpice